

# Introduction to HVDC

## VSC HVDC


*Dr Radnya A Mukhedkar*

*Group Leader, Senior Principal Engineer  
System Design*


GRID |

**ALSTOM**


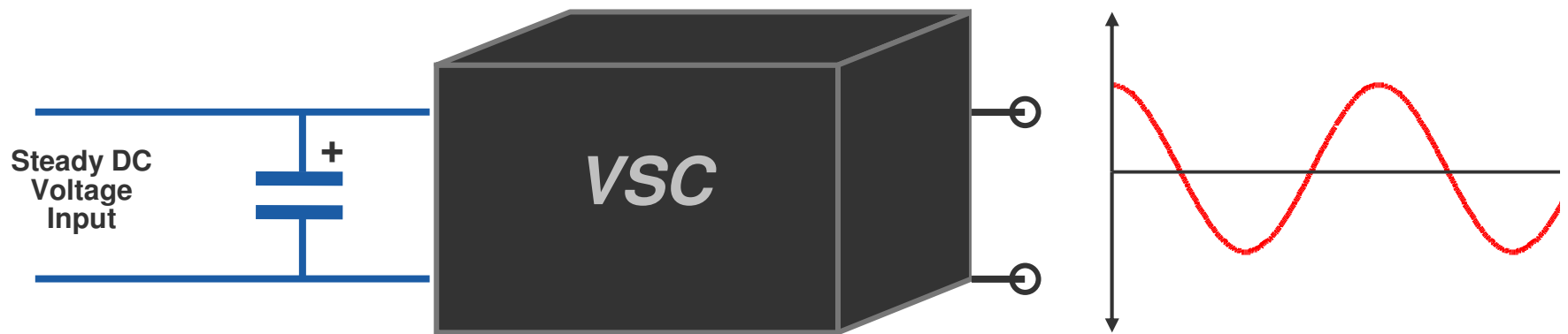
# The Voltage Sourced Converter Single Phase


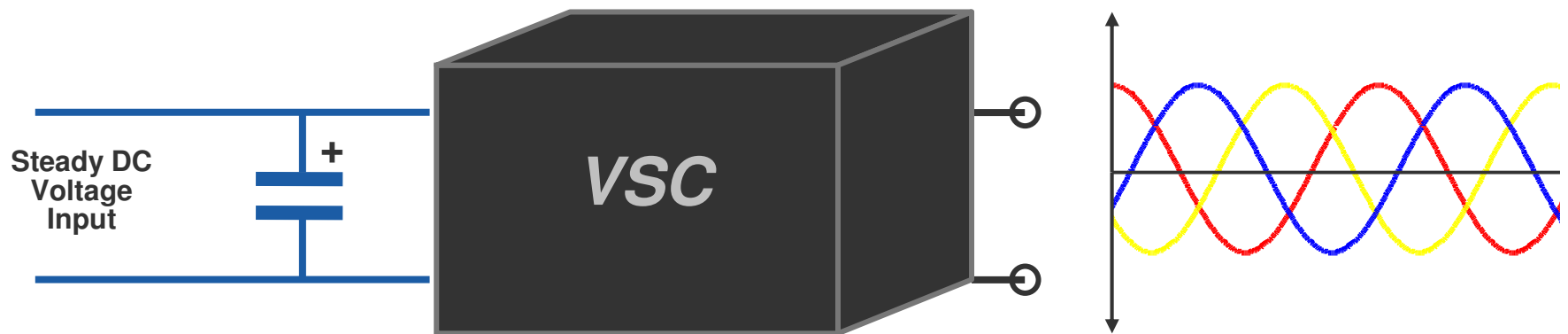
# The Voltage Sourced Converter Three Phase


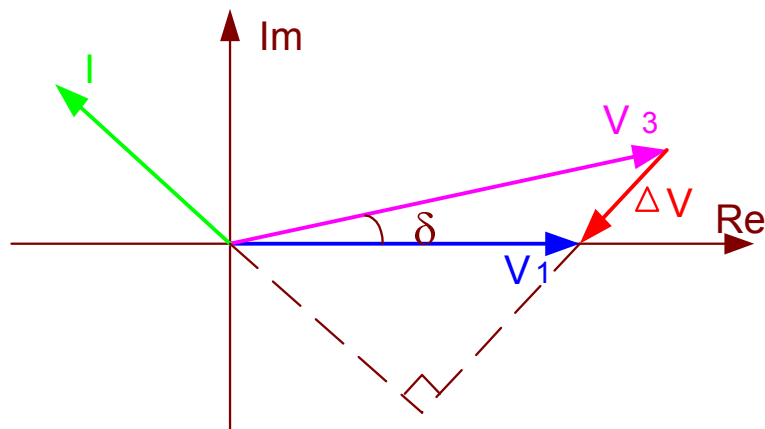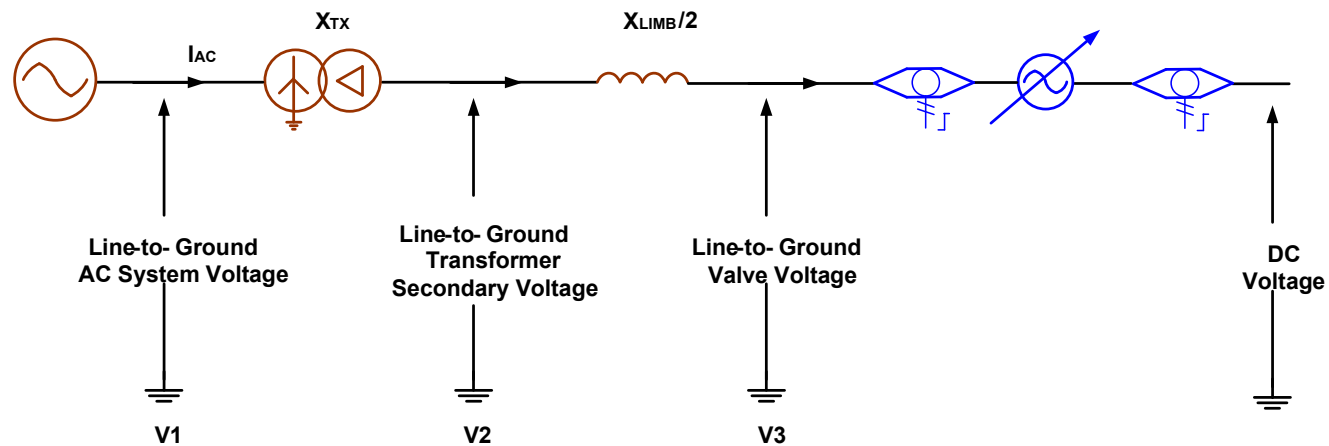
# AC/DC System Schematic – Ideal Load Flow




$$P = \frac{V_3 \cdot \sin(\delta)}{X} \cdot V_1$$

$$Q = \frac{V_3 \cdot \cos(\delta) - V_1}{X} \cdot V_1$$


# VSC

## Synthesis of a Sine Wave


### Voltage Waveforms

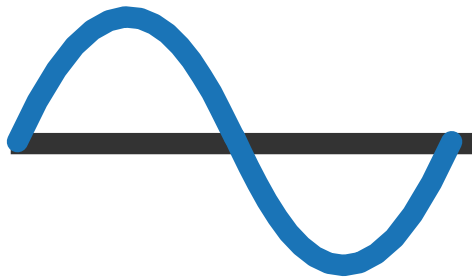

Ideal Waveform

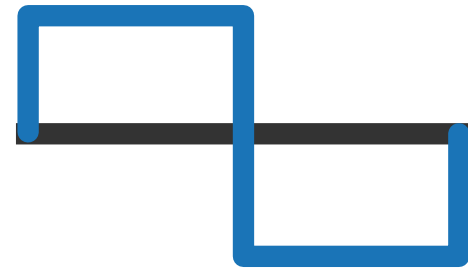


Simplest Possible Waveform

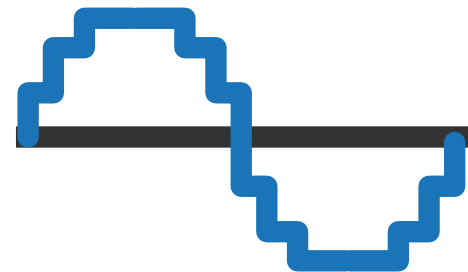


Acceptable Approximation if Sufficient Steps are Used

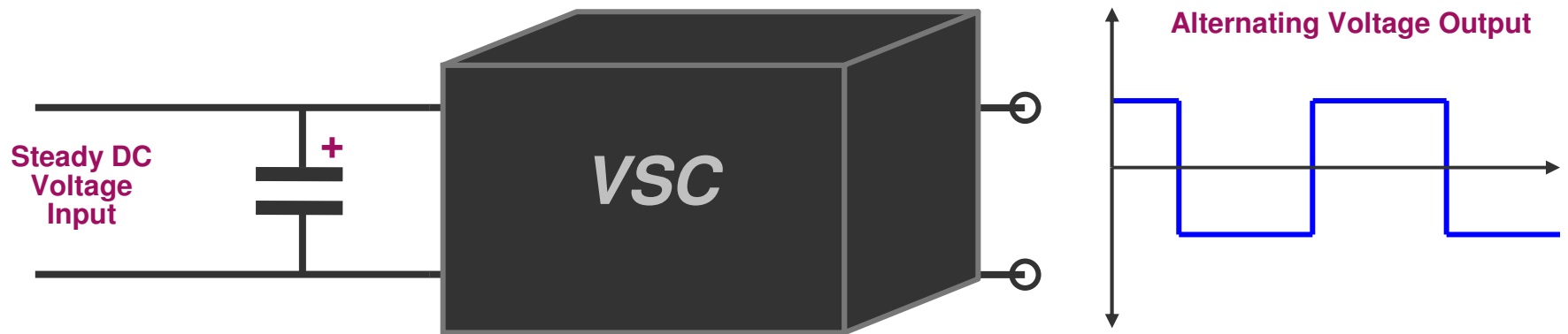
# The Voltage Sourced Converter Single Phase, 2-level



# VSC: Three Main Classes


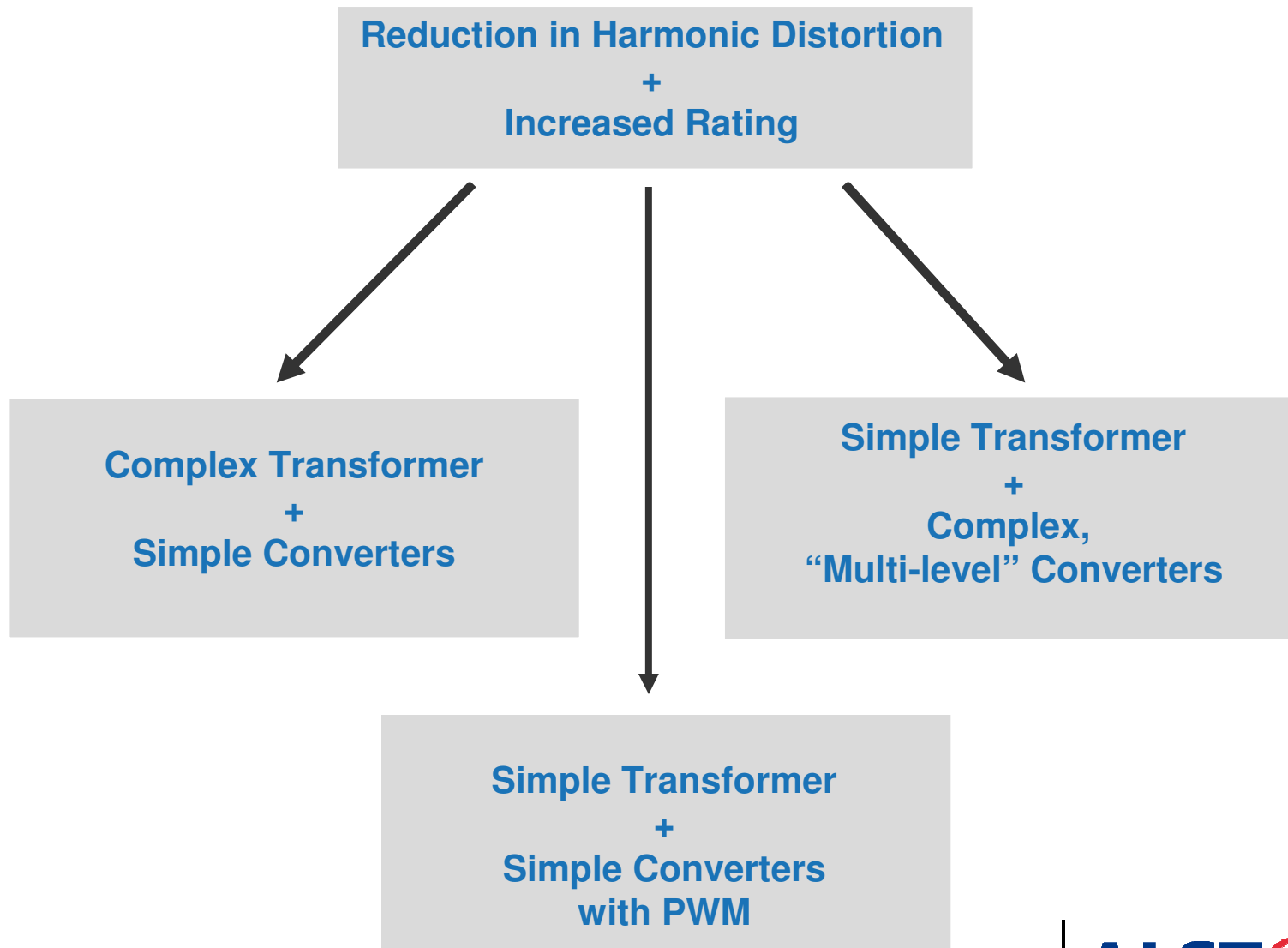

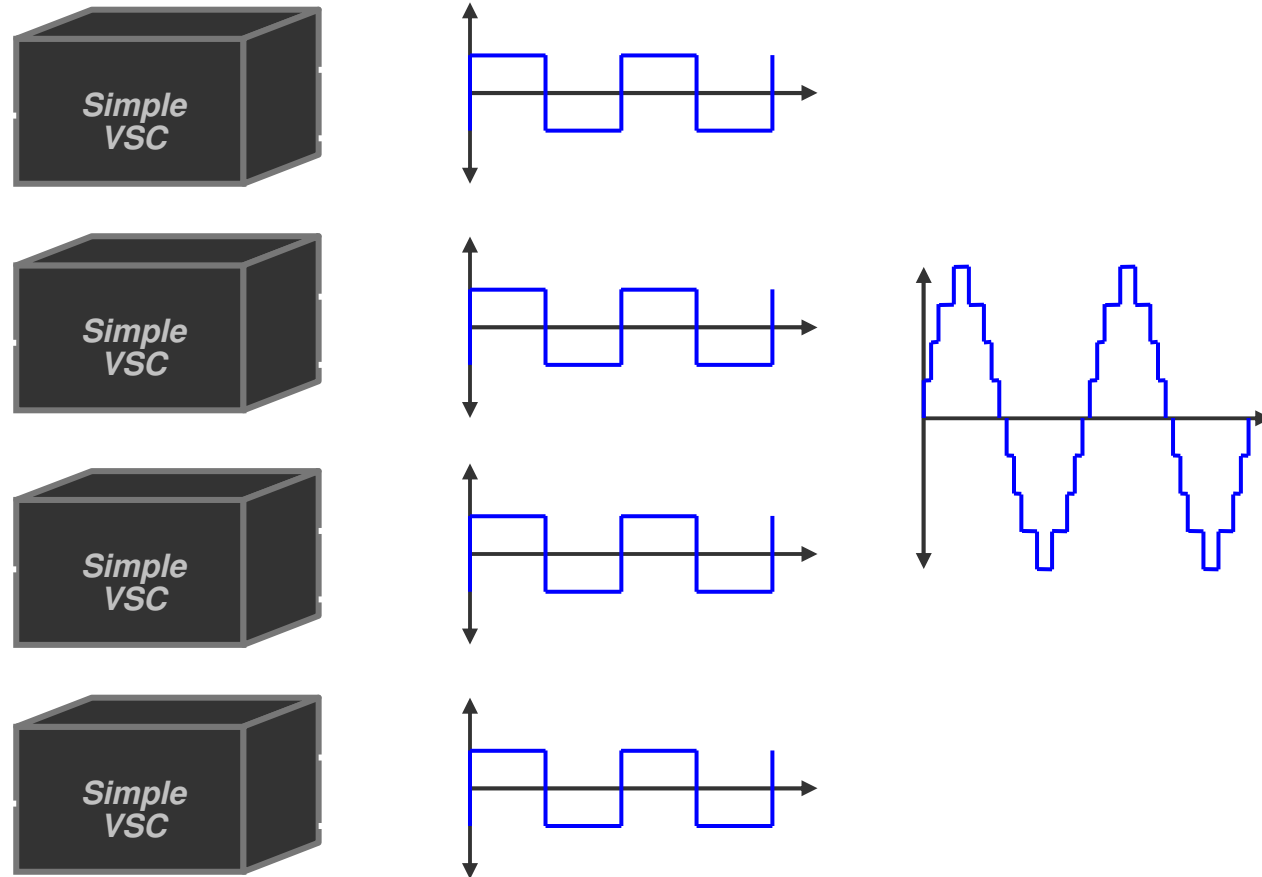
# Complex Transformer + simple converters







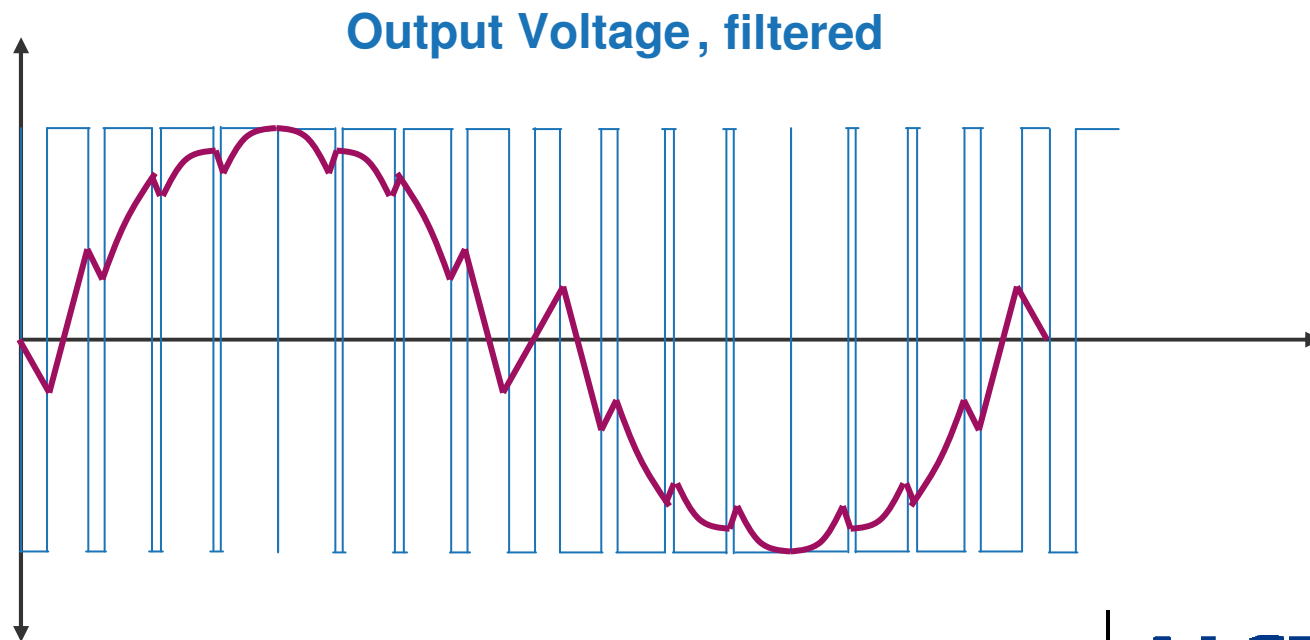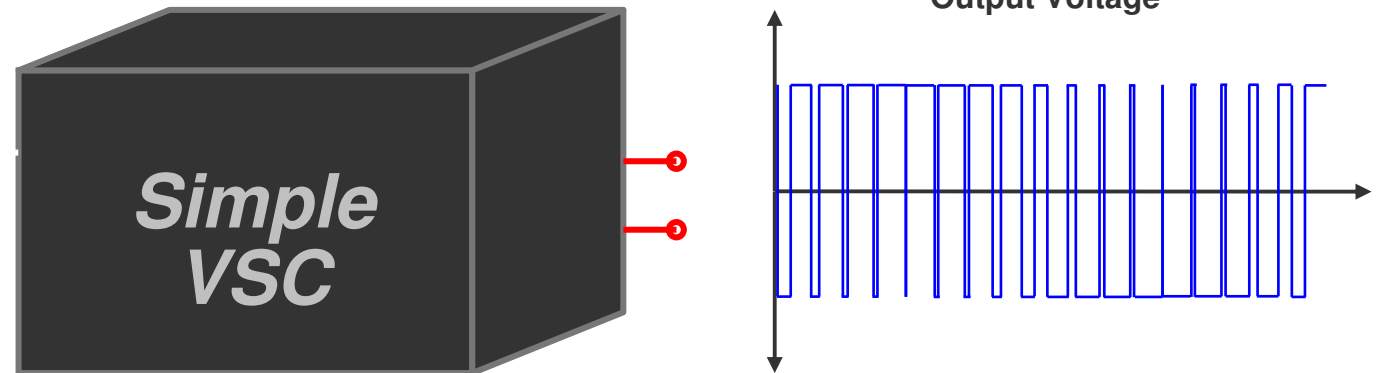
# Simple Transformer, Simple Converter + PWM



# Multi-Level Converter

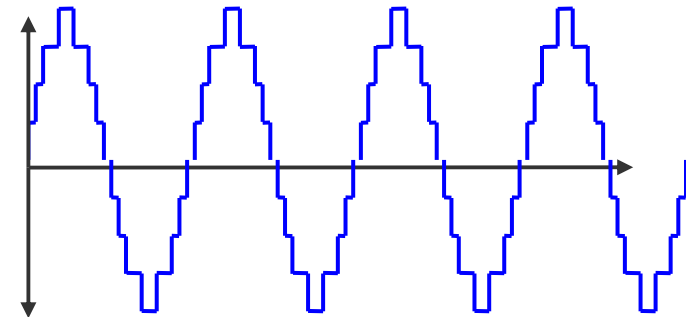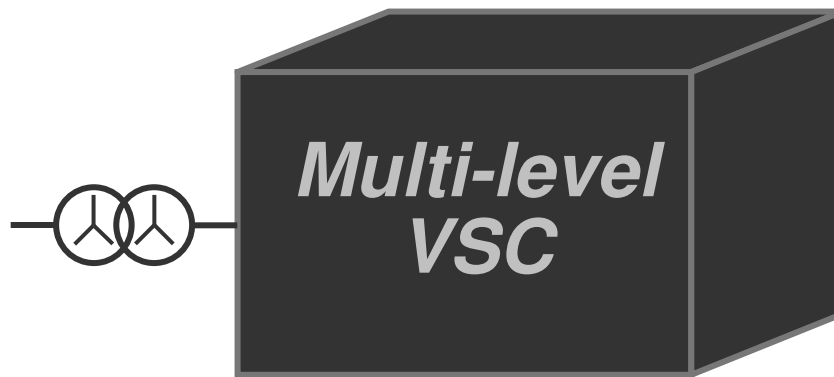


# What is a multi-level converter?

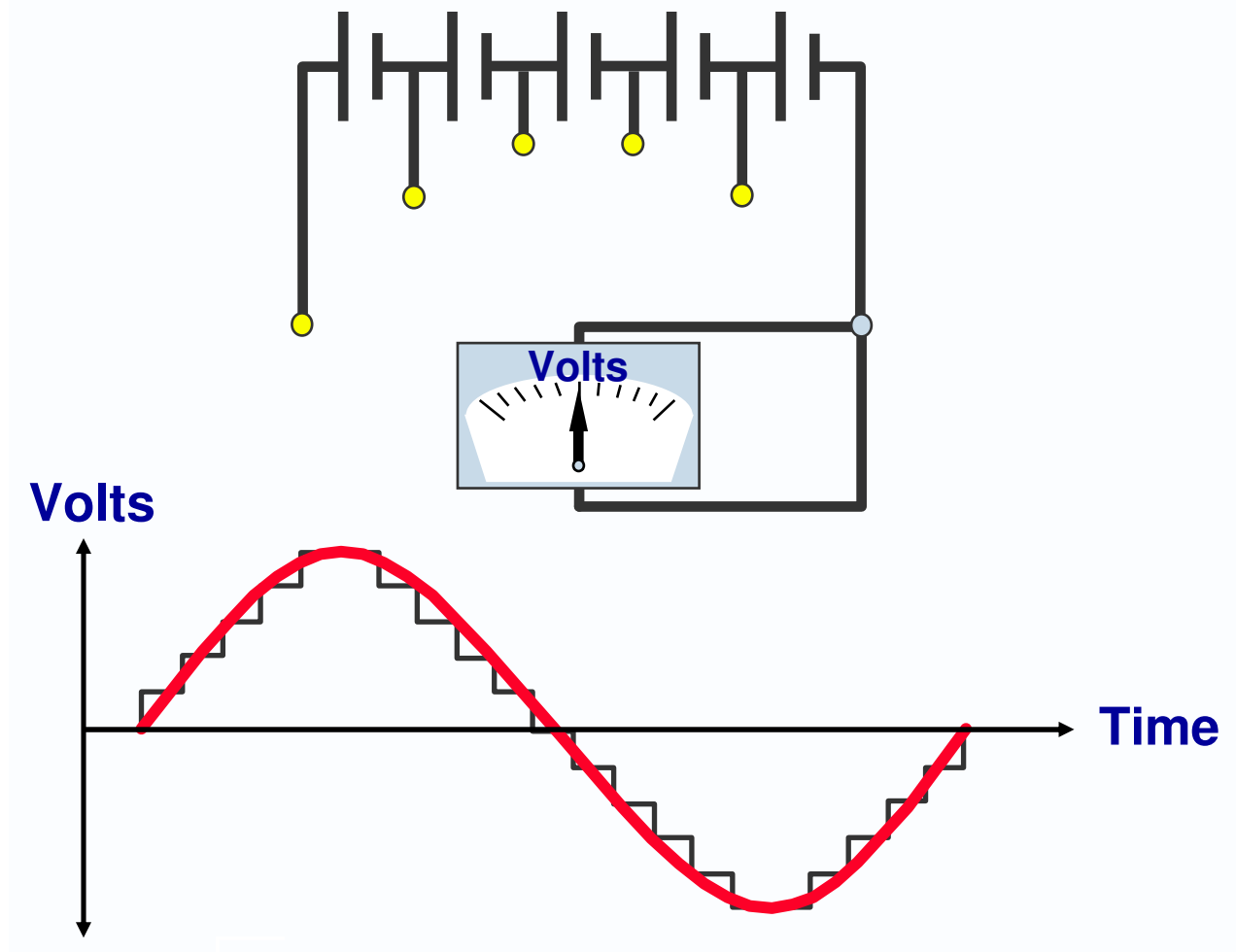

Total Flexibility

# VSC Converter: phase arm

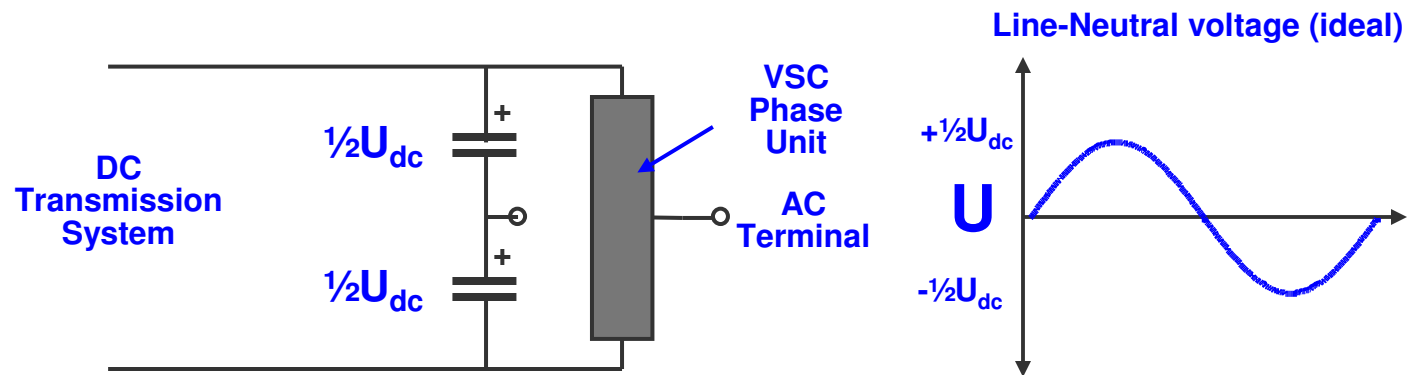

# Semiconductors for VSC

Voltage-Sourced Converters require semiconductors which can carry current in both directions and withstand voltage in the positive direction

The following types of device have the appropriate properties:

Thyristor derivatives:

- GTO: Gate Turn-Off thyristor
- GCT: Gate Commutated Thyristor (= a GTO with a better gate drive)
- IGCT: Integrated Gate Commutated Thyristor (=a GCT with the gate drive “integrated” into the semiconductor package)


Transistor derivatives:

- BJT: Bipolar Junction Transistor (only for low power and low frequency)
- MOSFET: Metal-Oxide Semiconductor Field Effect Transistor (only for low power)
- IGBT: Insulated Gate Bipolar Transistor
- IEGT: Injection Enhanced Gate Transistor – similar to an IGBT



**Do not confuse IGBT and IGCT!!**

# Basic 2-level inverter

## One phase arm

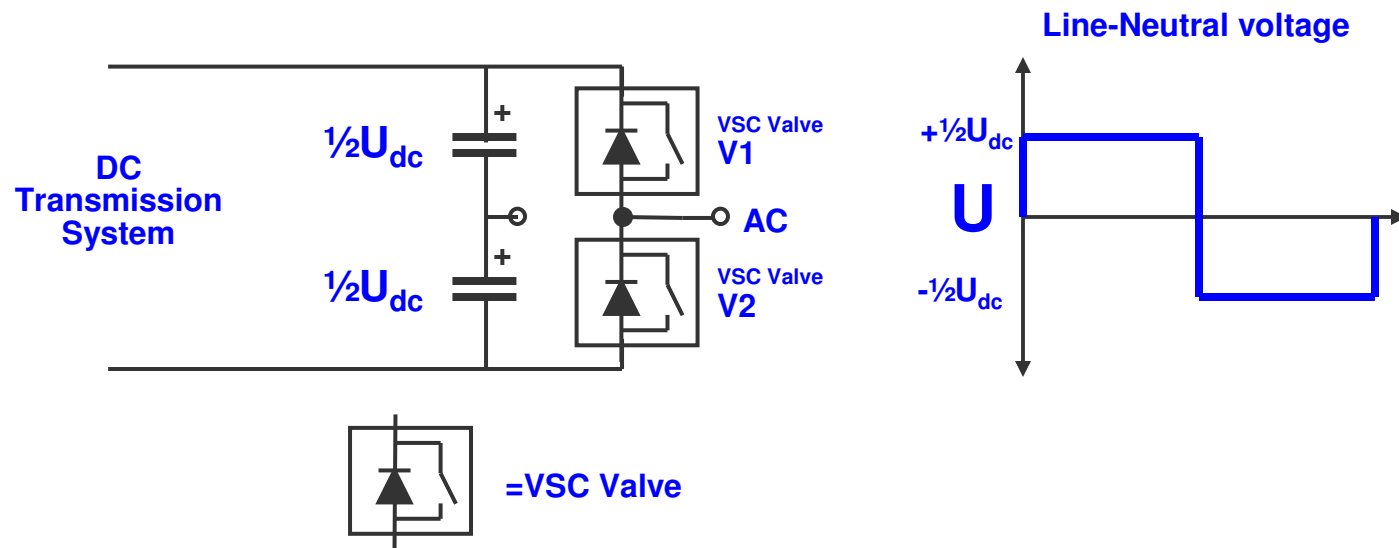
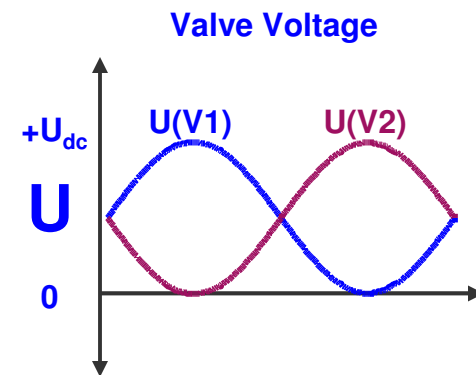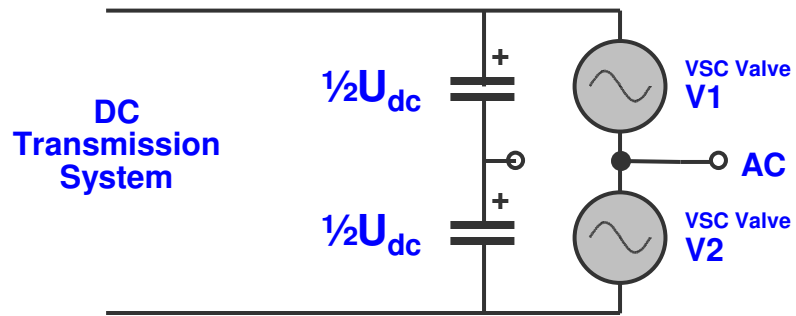
# VSC Valves of the 'Controllable Voltage Source' type




# Circuit Types

GRID |


**ALSTOM**


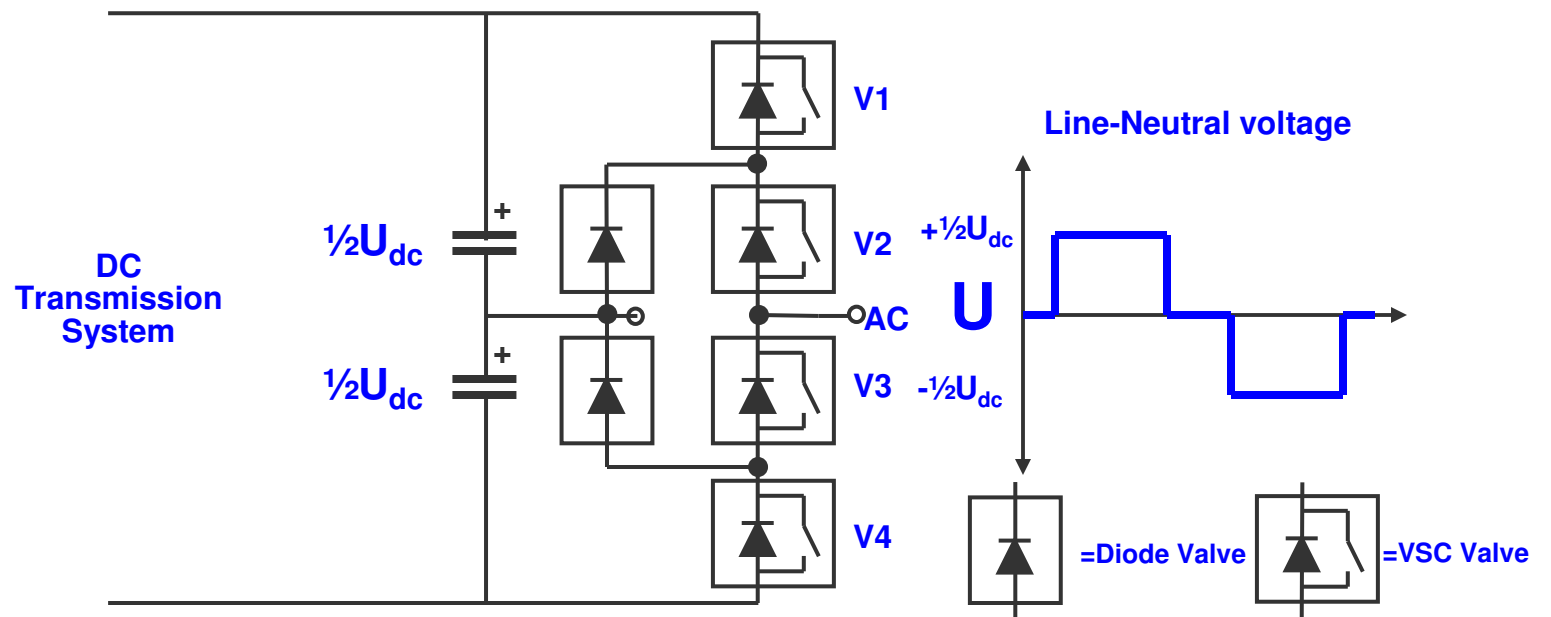
# Neutral-point clamped inverter One phase arm (3 level)



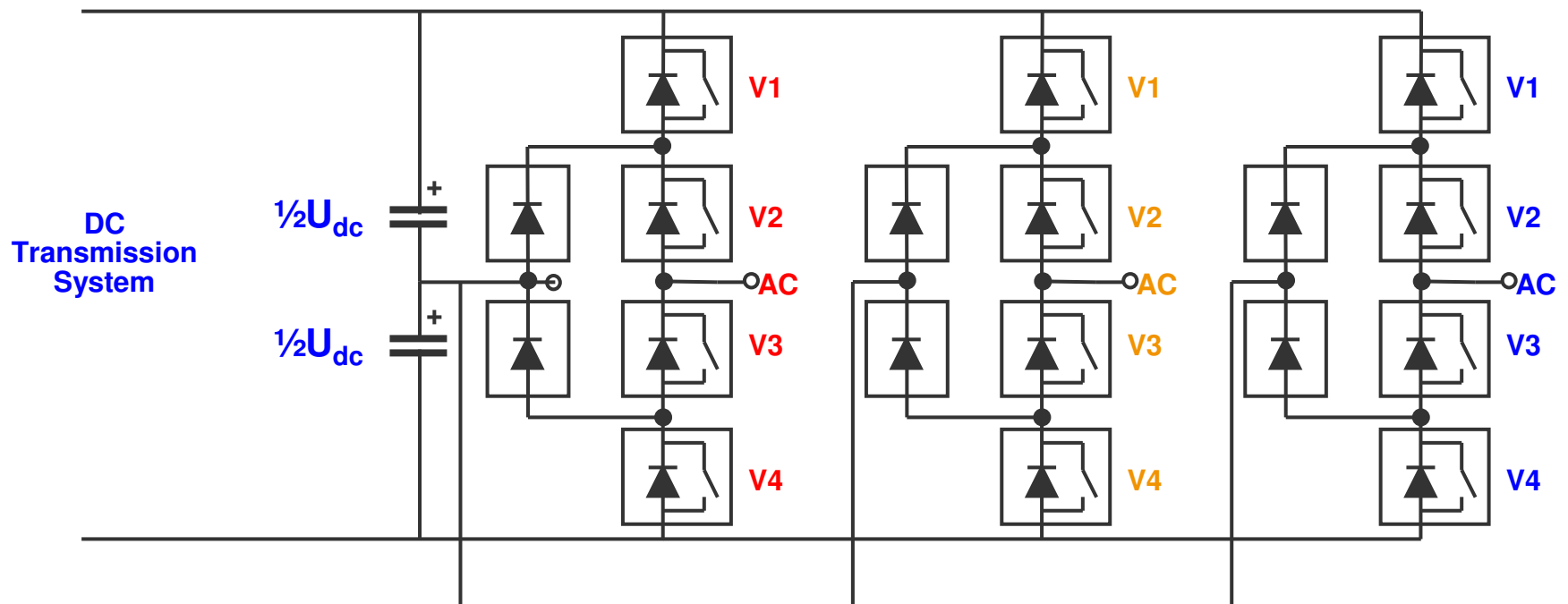
# Neutral-point clamped inverter Three-phase circuit (3 level)




# Neutral-point clamped inverter

## One phase arm (5 level)

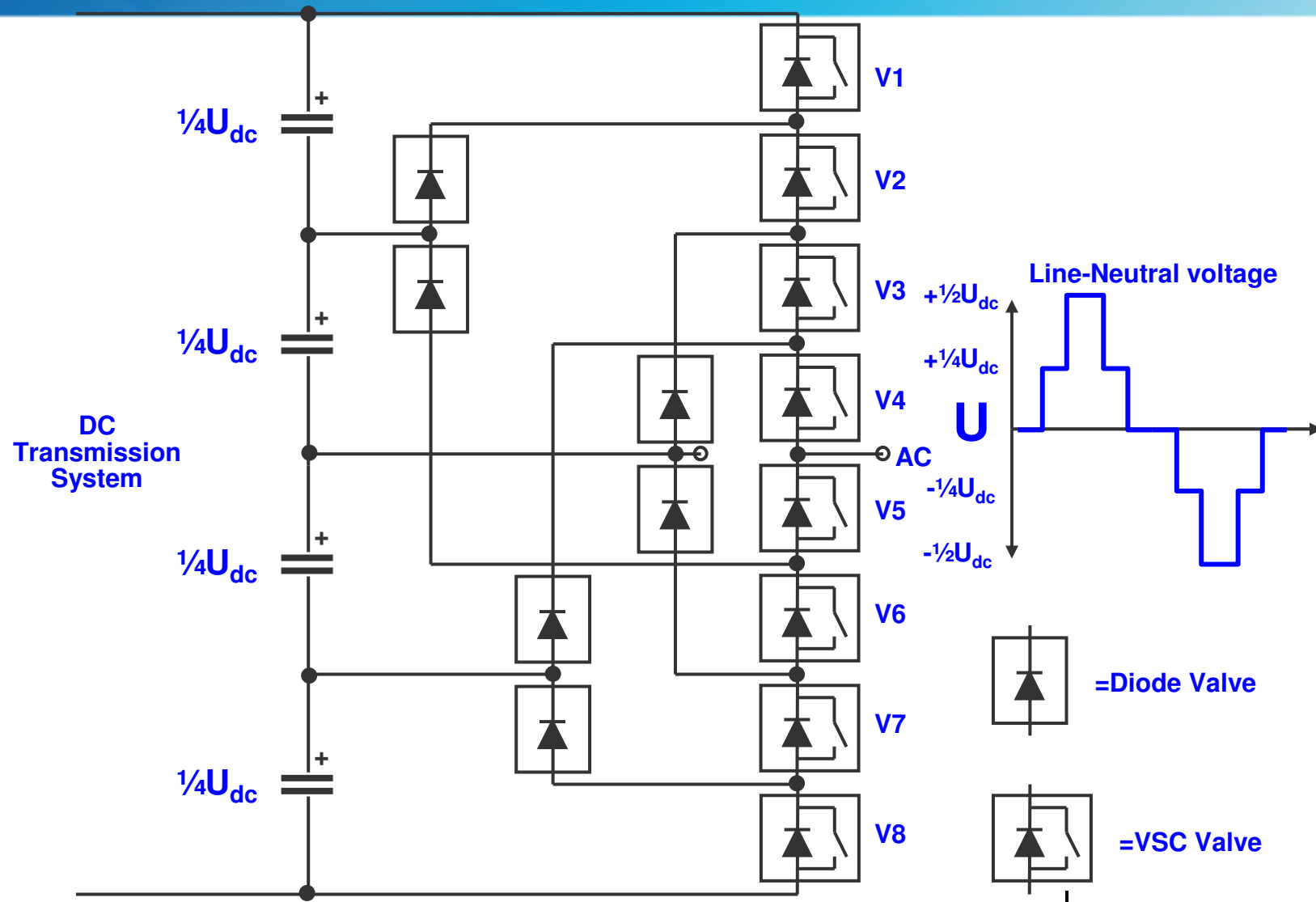


# Flying Capacitor inverter

## One phase arm (3 level)

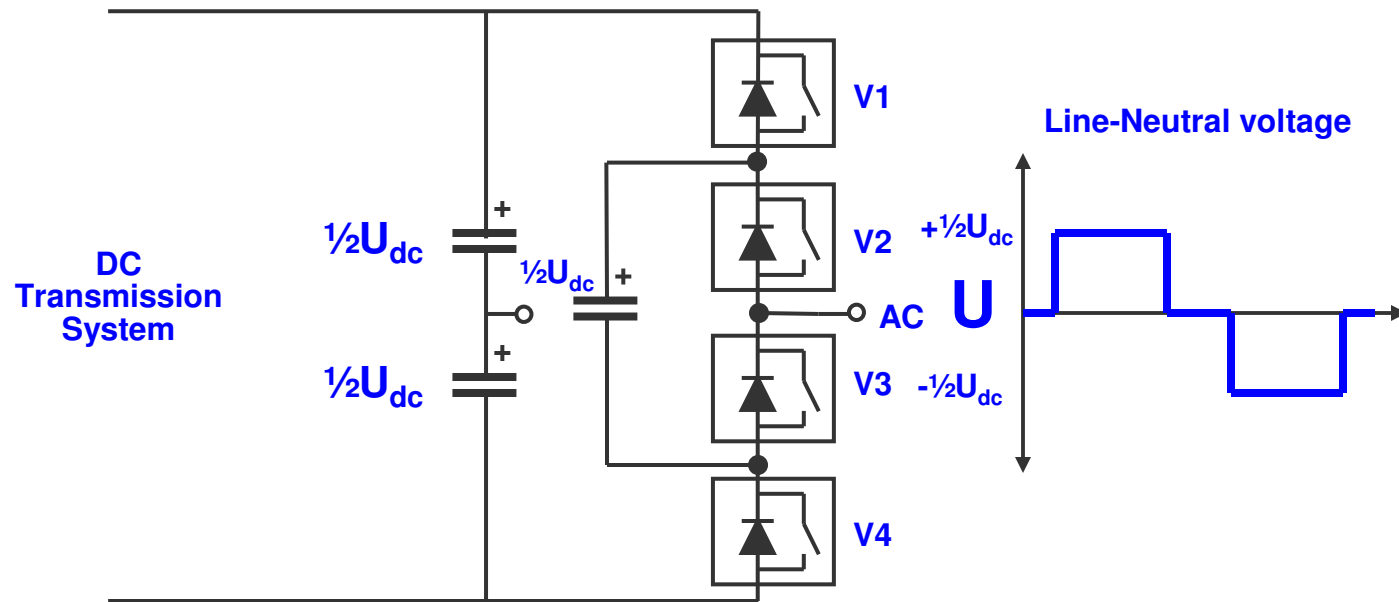

# VSC with series-connected chain link modules

a.k.a. Modular MultiLevel Converter


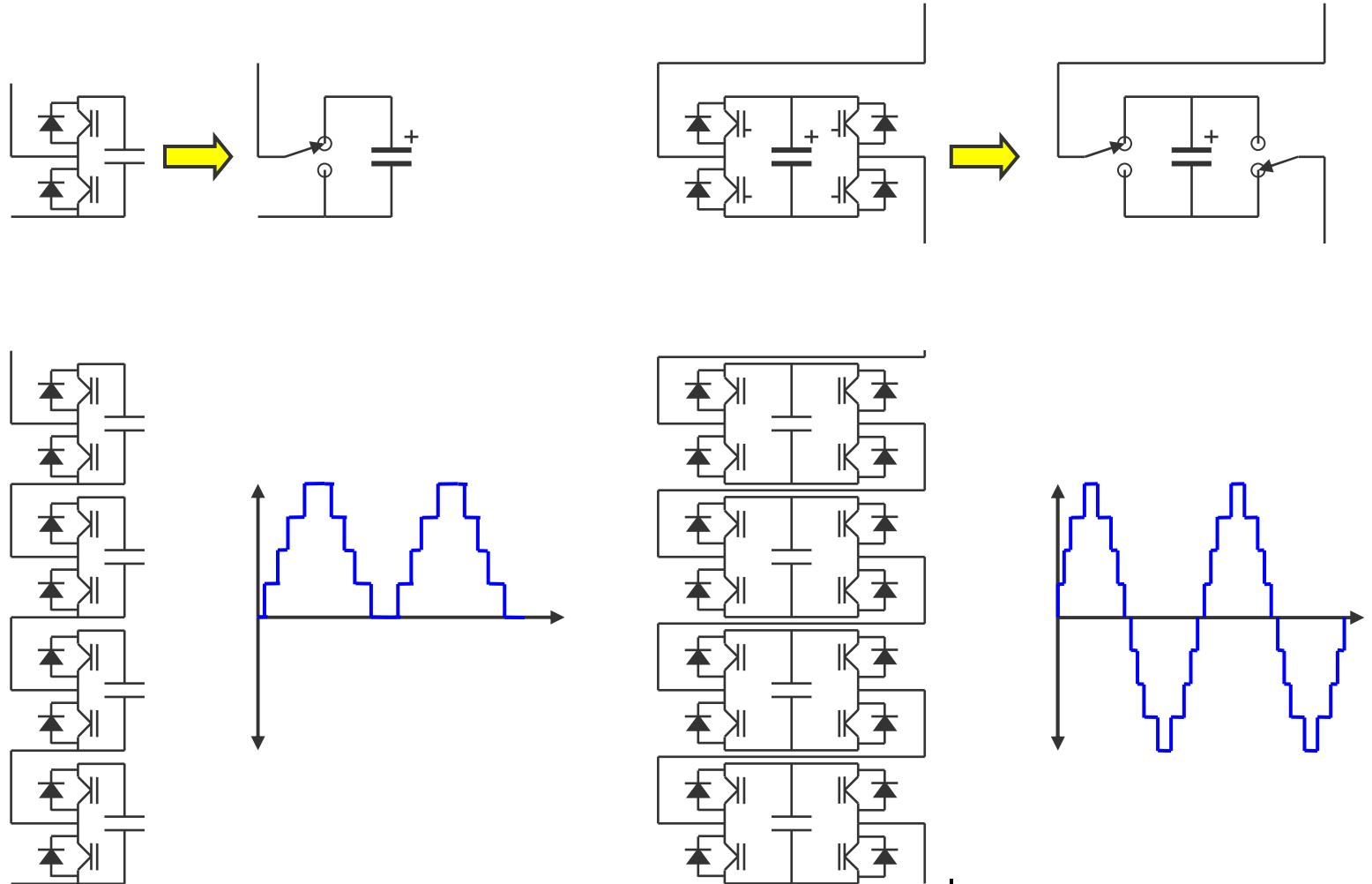


# VSC-HVDC

## 2 Basic Approaches

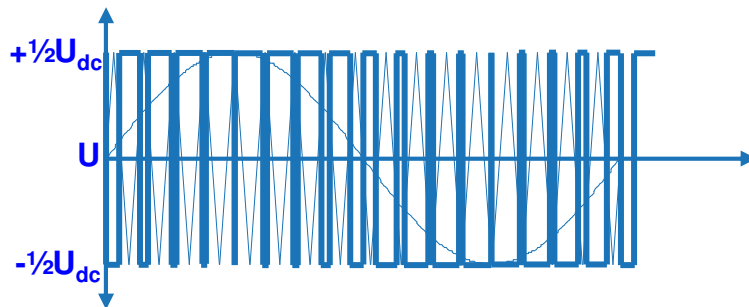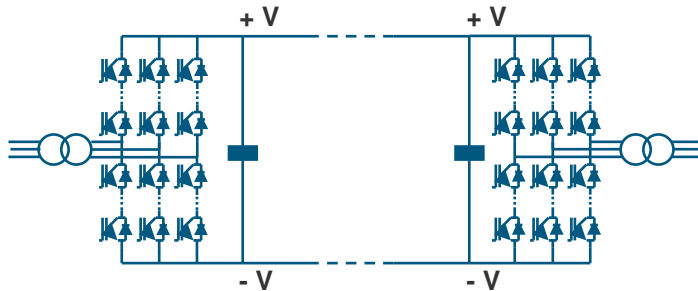
### Series-Connected IGBTs

- ✓ Conceptually simple circuit
- ✗ Requires PWM
- ✗ High switching losses
- ✗ Harmonic and EMC problems from PWM



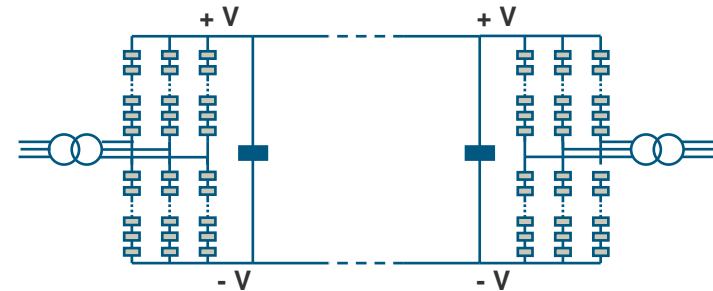
### Multi-level circuit

- ✓ Low switching losses
- ✓ Easily "scaleable"
- ✓ Virtually no harmonics
- ✗ More complex controls



□ = "Chain-Link" Module

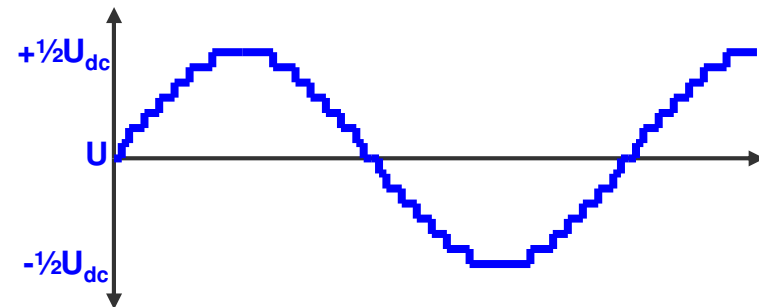


# Valve Design

GRID |

**ALSTOM**

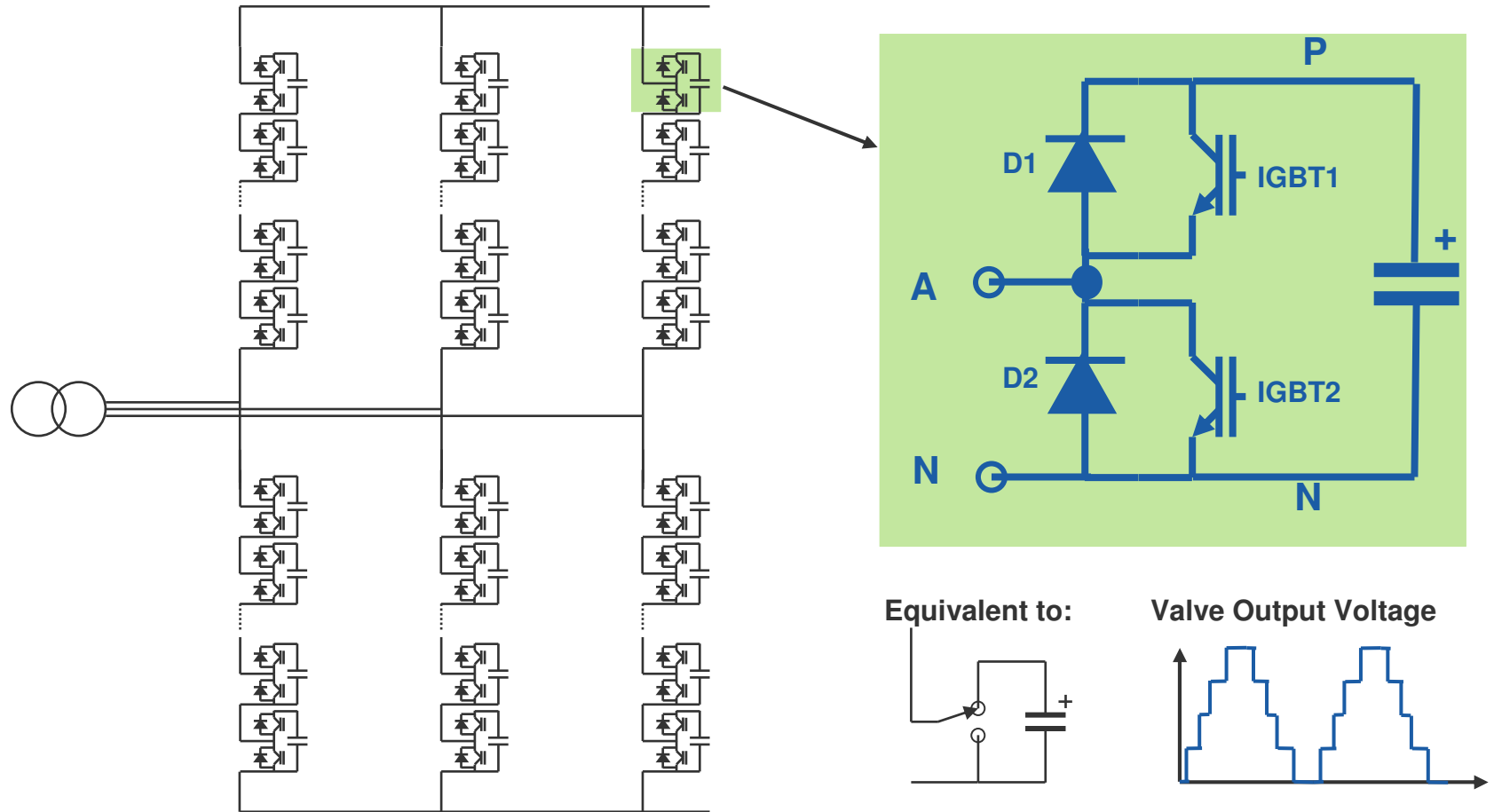
# VSC with series-connected half-chain links



**Cannot** electronically suppress faults on the DC side. Need to open the AC circuit breaker instead.




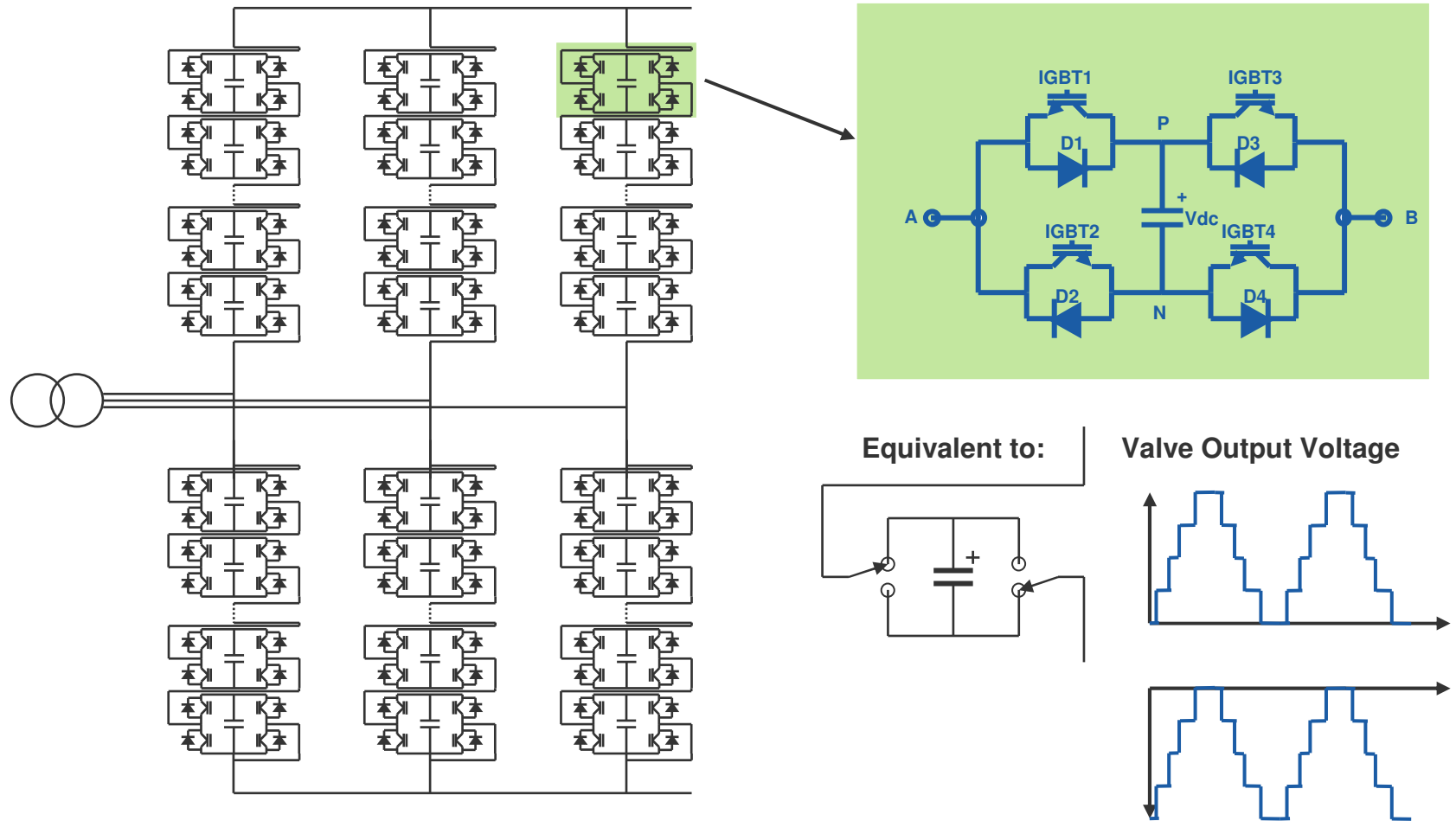
# VSC with series-connected full-chain links




Can suppress faults on the DC side by blocking the chain links (or putting them “in reverse”)

# Circuit Topology

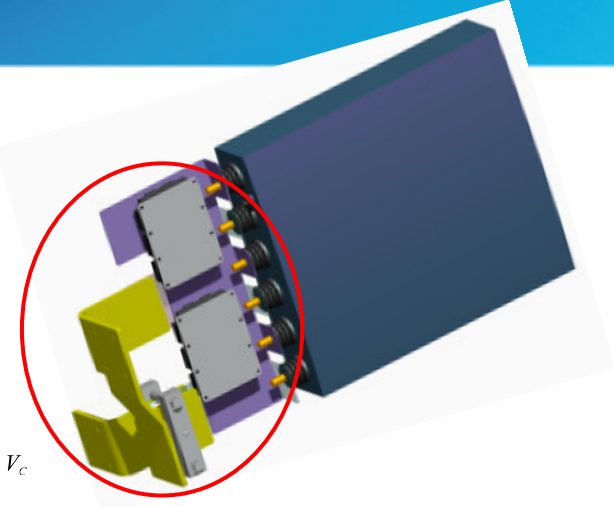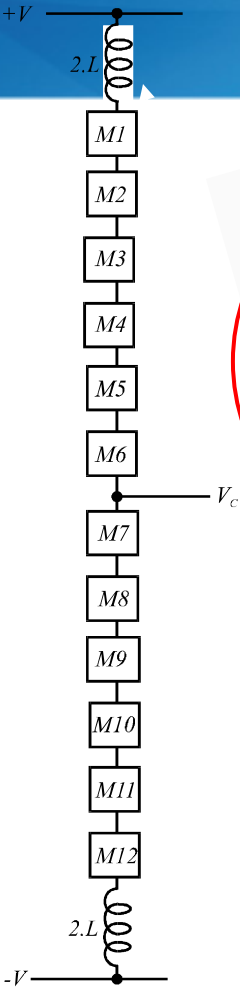


**Power Module**

**Capacitor**

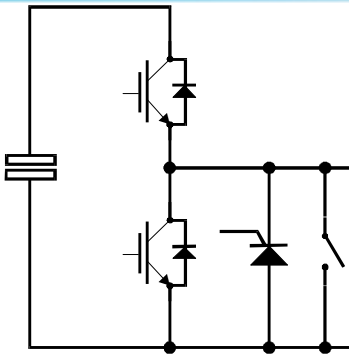

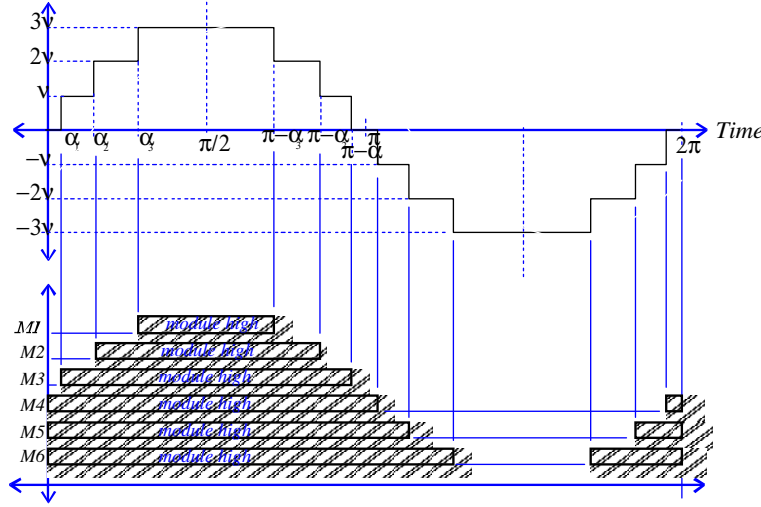**Module**

**Line reactance (L) split  
Becomes a means of  
protection**




**Stepped Waveform**

**Seven Level  
Overall Topology**

- ▶ **The number of modules = the number of devices in a conventional circuit**
- ◆ **Requires twice the number of devices**

# VSC Valves - Sub-module Components

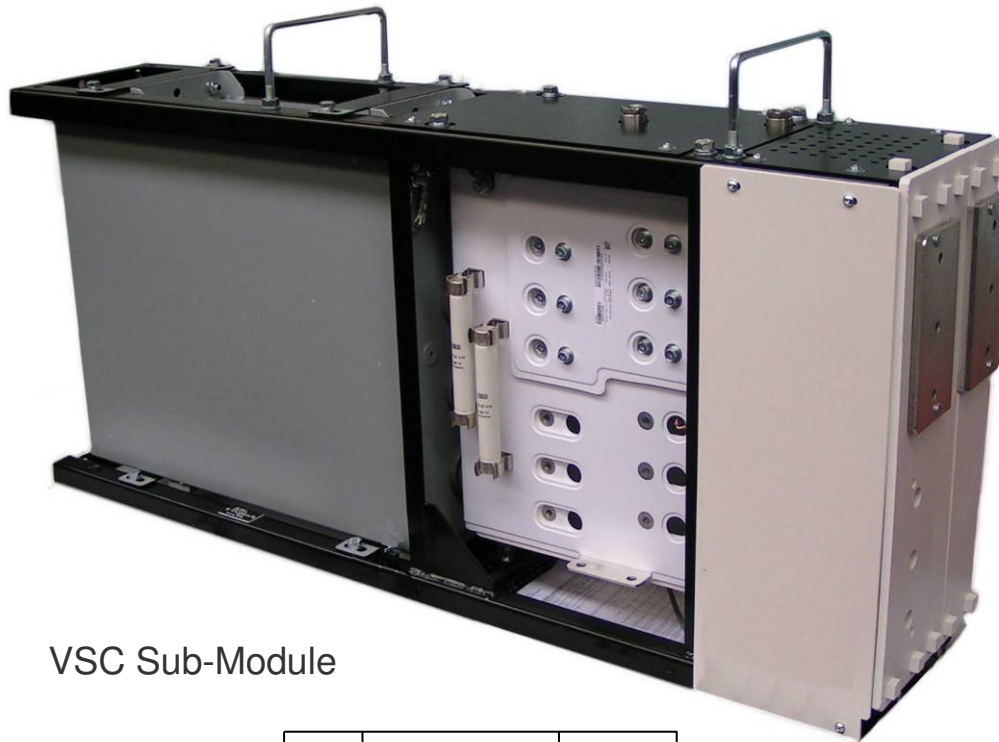

VSC Sub-Module




Inter Sub-module Connector



Bypass Switch




IGBT

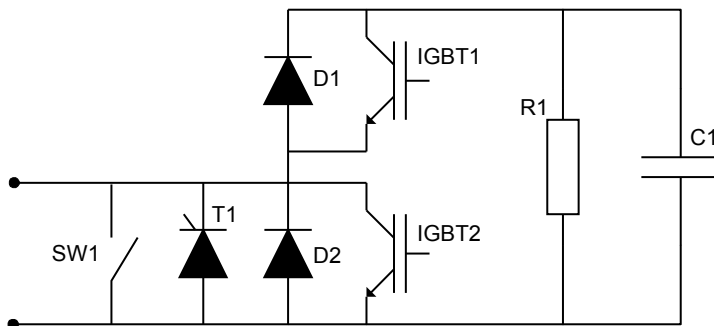


P 27

# Main Components in 'Half Bridge'


IGBT (x2)

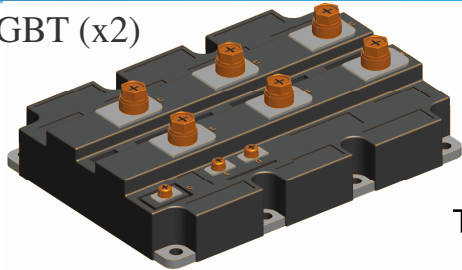


Capacitor +ve  
Test Connection

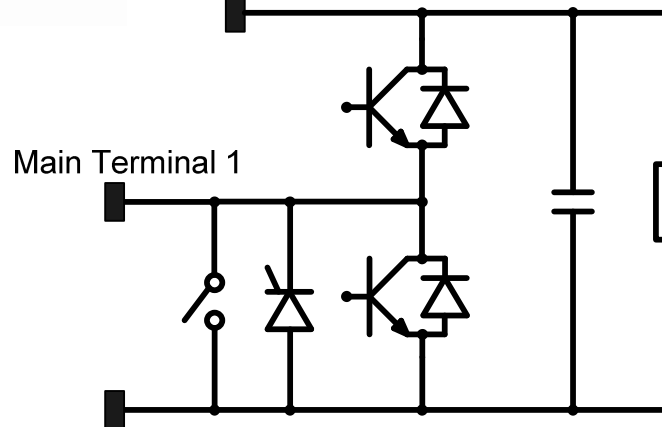


Capacitor

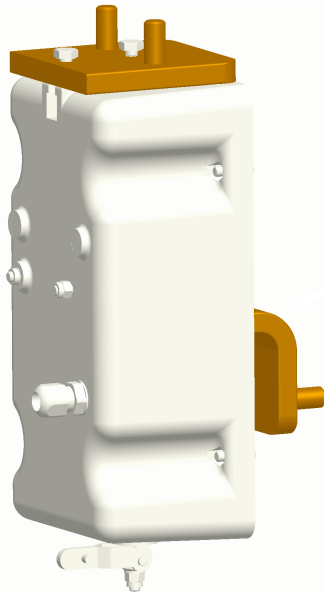


By-pass Switch

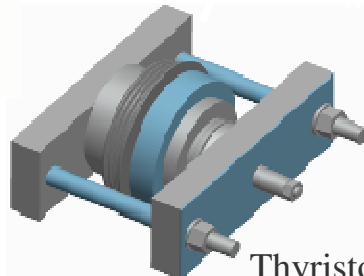

Thyristor and Clamp

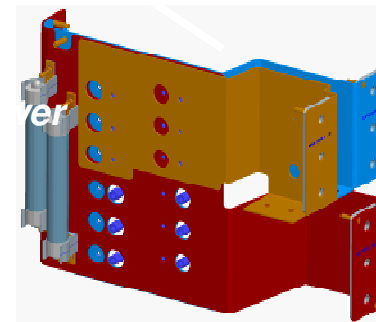



Laminated Bus-Bar

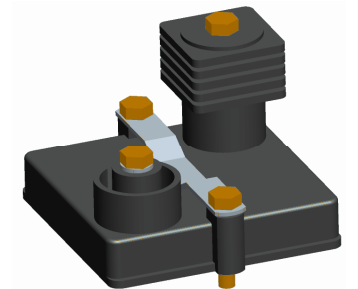


Bleed Resistor (x2)

# Main Components in 'Full Bridge'


IGBT (x4)

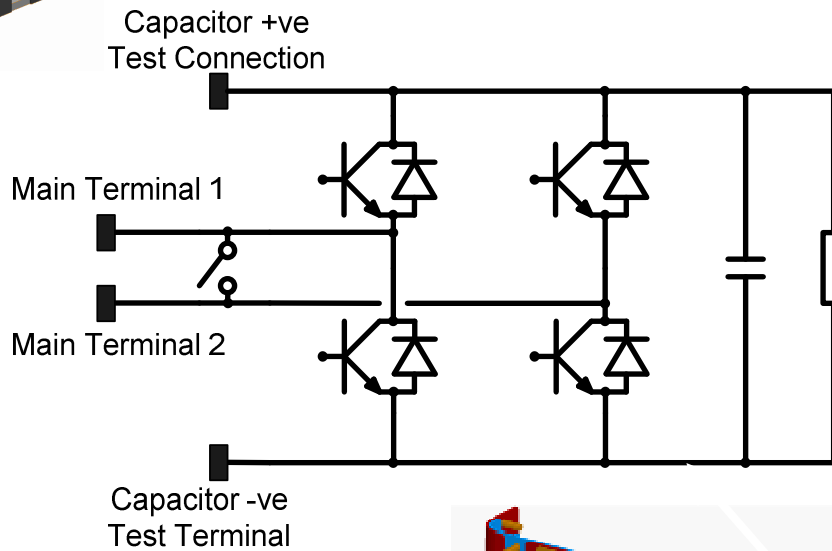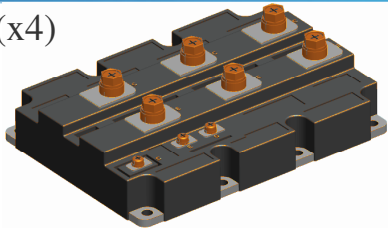


Capacitor

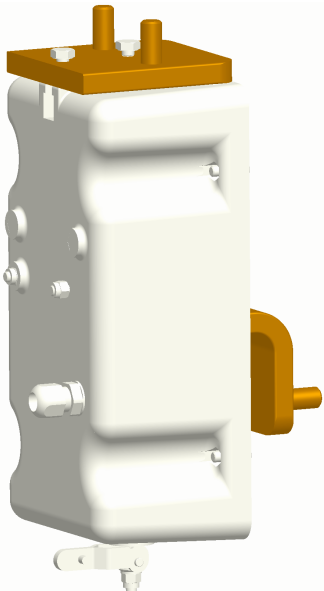

By-pass Switch

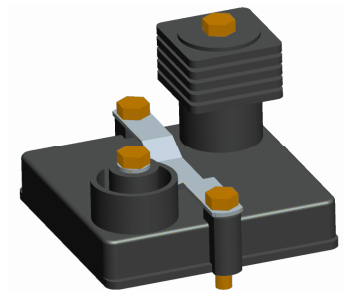

Bleed Resistor (x2)

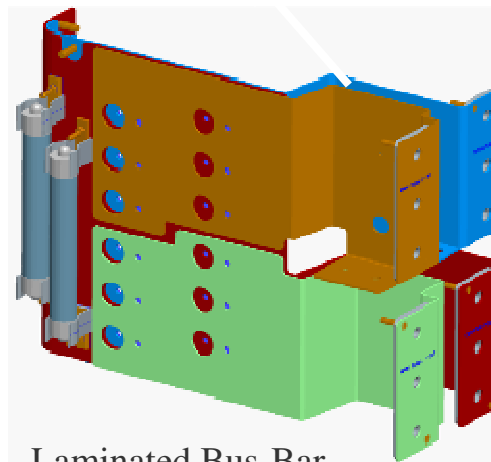

Laminated Bus-Bar

GRID



[www.alstom.com](http://www.alstom.com)

GRID |

**ALSTOM**