 


Digital Fundamentals

Tenth Edition

Floyd




Chapter 5

© 2008 Pearson Education

Summary

Combinational Logic Circuits

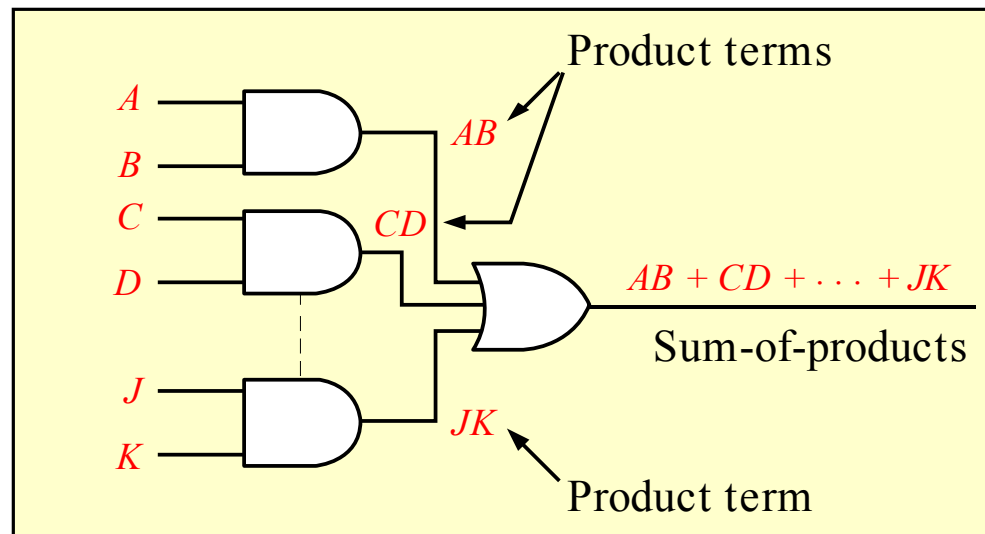
In Sum-of-Products (SOP) form, basic combinational circuits can be directly implemented with AND-OR combinations if the necessary complement terms are available.



Summary

Combinational Logic Circuits

 An example of an SOP implementation is shown. The SOP expression is an AND-OR combination of the input variables and the appropriate complements.




Summary

Combinational Logic Circuits

When the output of a SOP form is inverted, the circuit is called an AND-OR-Invert circuit. The AOI configuration lends itself to product-of-sums (POS) implementation.

 An example of an AOI implementation is shown. The output expression can be changed to a POS expression by applying DeMorgan's theorem twice.



Summary


Exclusive-OR Logic

The truth table for an exclusive-OR gate is
Notice that the output is HIGH whenever
 A and B disagree.

The Boolean expression is $X = \bar{A}B + A\bar{B}$

Inputs		Output
A	B	X
0	0	0
0	1	1
1	0	1
1	1	0


The circuit can be drawn as

 

Symbols:



Distinctive shape

 

Rectangular outline

Summary

Exclusive-NOR Logic


The truth table for an exclusive-NOR gate is

Notice that the output is HIGH whenever *A* and *B* agree.

The Boolean expression is $X = \bar{A}\bar{B} + AB$

Inputs		Output
A	B	X
0	0	1
0	1	0
1	0	0
1	1	1


The circuit can be drawn as

 

Symbols:



Distinctive shape

 


Rectangular outline

Summary

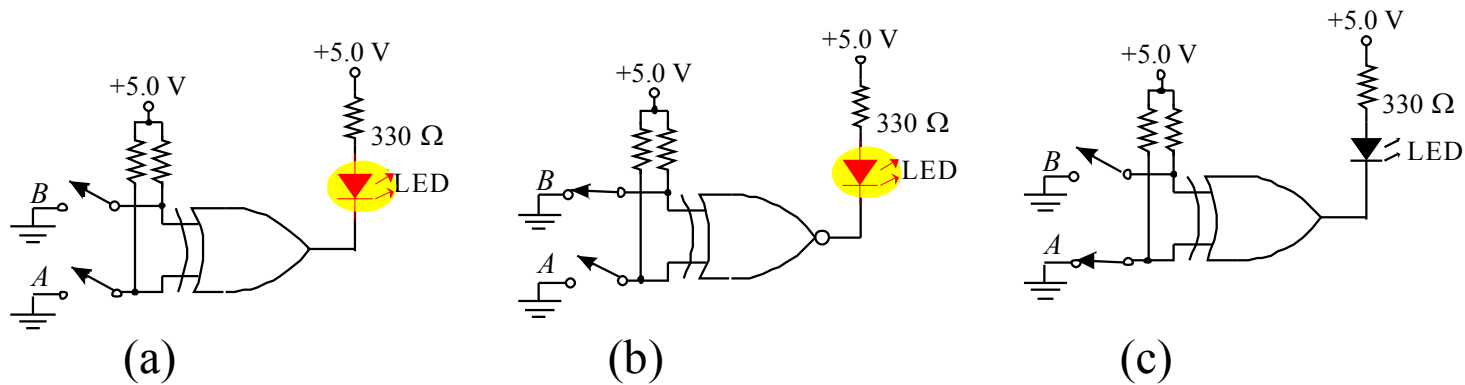Example

For each circuit, determine if the LED should be on or off.



Solution

Circuit (a): XOR, inputs agree, output is LOW, LED is ON.

Circuit (b): XNOR, inputs disagree, output is LOW, LED is ON.

Circuit (c): XOR, inputs disagree, output is HIGH, LED is OFF.


Summary

Implementing Combinational Logic

Implementing a SOP expression is done by first forming the AND terms; then the terms are ORed together.

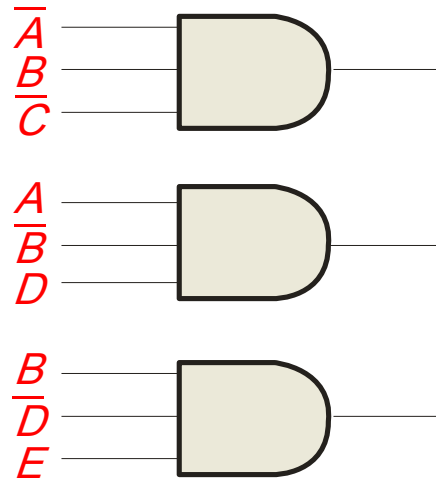Example Show the circuit that will implement the Boolean expression $X = \overline{A}BC + A\overline{B}D + B\overline{D}E$. (Assume that the variables and their complements are available.)

Solution Start by forming the terms using three 3-input AND gates. Then combine the three terms using a 3-input OR gate.




$$X = \overline{A}BC + A\overline{B}D + B\overline{D}E$$

Summary

Karnaugh Map Implementation

For basic combinational logic circuits, the Karnaugh map can be read and the circuit drawn as a minimum SOP.

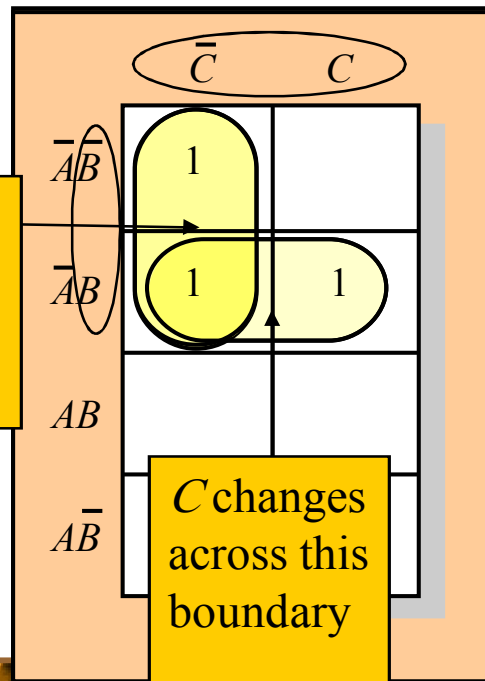Example A Karnaugh map is drawn from a truth table. Read the minimum SOP expression and draw the circuit.



B changes across this boundary

C changes across this boundary


Solution

1. Group the 1's into two overlapping groups as indicated.
2. Read each group by eliminating any variable that changes across a boundary.
3. The vertical group is read $\bar{A}\bar{C}$.
4. The horizontal group is read $\bar{A}B$.

The circuit is on the next slide:

Summary

Solution *continued...*

 

The result is shown as a sum of products.

It is a simple matter to implement this form using only NAND gates as shown in the text and following example.


Summary

NAND Logic

 Example Convert the circuit in the previous example to one that uses only NAND gates.

Solution


Recall from Boolean algebra that double inversion cancels. By adding inverting bubbles to above circuit, it is easily converted to NAND gates:




Summary

Universal Gates

 
NAND gates are sometimes called **universal** gates because they can be used to produce the other basic Boolean functions.




Inverter

 

AND gate

 

OR gate

 


NOR gate


Summary

Universal Gates

 
NOR gates are also **universal** gates and can form all of the basic gates.




Inverter

 

OR gate

 

AND gate

 


NAND gate

Summary

NAND Logic

 Recall from DeMorgan's theorem that $\overline{AB} = \overline{A} + \overline{B}$. By using equivalent symbols, it is simpler to read the logic of SOP forms. The earlier example shows the idea:




The logic is easy to read if you (mentally) cancel the two connected bubbles on a line.

Summary

NOR Logic

 Alternatively, DeMorgan's theorem can be written as $A + B = \overline{A\overline{B}}$. By using equivalent symbols, it is simpler to read the logic of POS forms. For example,




Again, the logic is easy to read if you cancel the two connected bubbles on a line.

Summary

Pulsed Waveforms


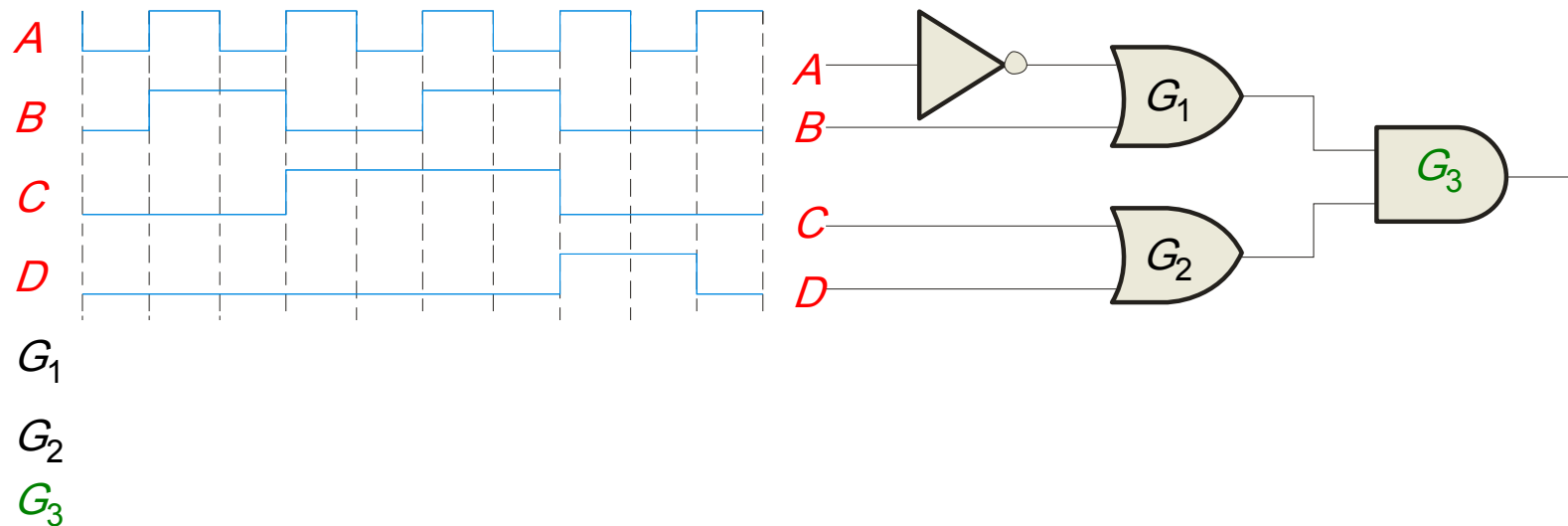
For combinational circuits with pulsed inputs, the output can be predicted by developing intermediate outputs and combining the result. For example, the circuit shown can be analyzed at the outputs of the OR gates:



Summary

Pulsed Waveforms

  Alternatively, you can develop the truth table for the circuit and enter 0's and 1's on the waveforms. Then read the output from the table.



Inputs				Output
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>X</i>
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Selected Key Terms

Universal gate Either a NAND or a NOR gate. The term universal refers to a property of a gate that permits any logic function to be implemented by that gate or by a combination of gates of that kind.

Negative-OR The dual operation of a NAND gate when the inputs are active-LOW.

Negative-AND The dual operation of a NOR gate when the inputs are active-LOW.

Quiz

1. Assume an AOI expression is $\overline{AB + CD}$. The equivalent POS expression is

- a. $(A + B)(C + D)$
- b. $(\overline{A} + \overline{B})(\overline{C} + \overline{D})$
- c. $\overline{(A + B)(C + D)}$
- d. none of the above

Quiz

2. The truth table shown is for


- a. a NAND gate
- b. a NOR gate
- c. an exclusive-OR gate
- d. an exclusive-NOR gate

Inputs		Output
A	B	X
0	0	1
0	1	0
1	0	0
1	1	1

Quiz

3. An LED that should be ON is

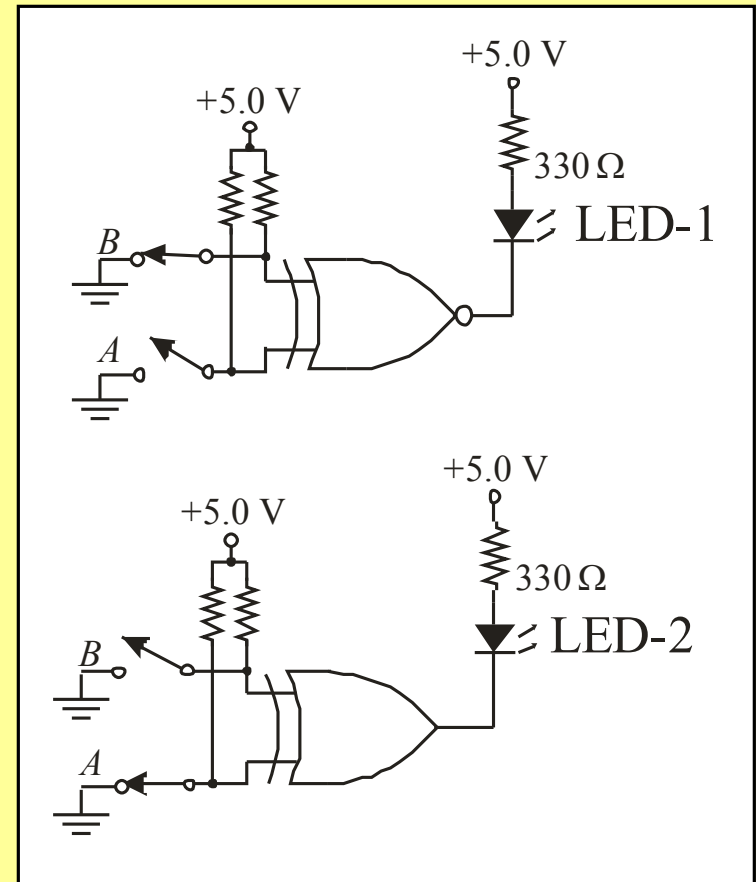
- a. LED-1
- b. LED-2
- c. neither
- d. both



Quiz

4. To implement the SOP expression $X = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}D + B\bar{D}E$ the type of gate that is needed is a

 - a. 3-input AND gate
- b. 3-input NAND gate
- c. 3-input OR gate
- d. 3-input NOR gate



Quiz

5. Reading the Karnaugh map, the logic expression is

a. $\bar{A}\bar{C} + \bar{A}B$

b. $\bar{A}B + A\bar{C}$

c. $A\bar{B} + B\bar{C}$


d. $\bar{A}B + \bar{A}\bar{C}$

	\bar{C}	C
$\bar{A}\bar{B}$	1	
$\bar{A}B$	1	1
AB		
$A\bar{B}$		

Quiz

6. The circuit shown will have identical logic out if all gates are changed to

 - a. AND gates
- b. OR gates
- c. NAND gates
- d. NOR gates



Quiz


7. The two types of gates which are called *universal gates* are

- a. AND/OR
- b. NAND/NOR
- c. AND/NAND
- d. OR/NOR

Quiz

8. The circuit shown is equivalent to an

 
- a. AND gate
- b. XOR gate
- c. OR gate
- d. none of the above



Quiz

9. The circuit shown is equivalent to

 
- a. an AND gate
- b. an XOR gate
- c. an OR gate
- d. none of the above



Quiz

10. During the first *three* intervals for the pulsed circuit shown, the output of

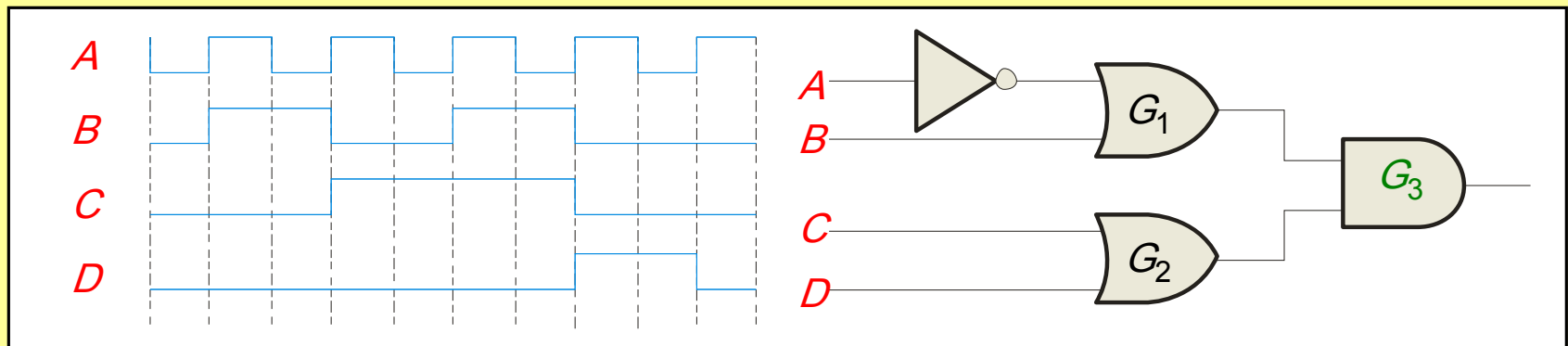- a. G_1 is LOW and G_2 is LOW
- b. G_1 is LOW and G_2 is HIGH
- c. G_1 is HIGH and G_2 is LOW
- d. G_1 is HIGH and G_2 is HIGH



Quiz

Answers:

- | | |
|------|-------|
| 1. b | 6. c |
| 2. d | 7. b |
| 3. a | 8. c |
| 4. c | 9. a |
| 5. d | 10. c |