
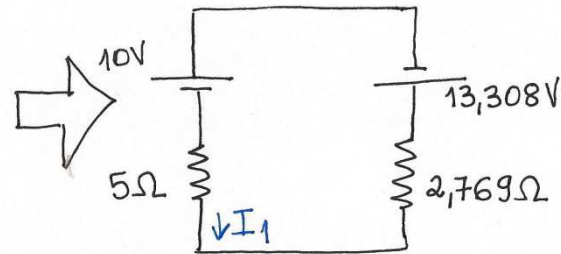
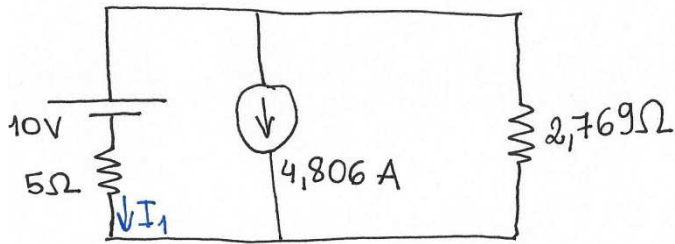
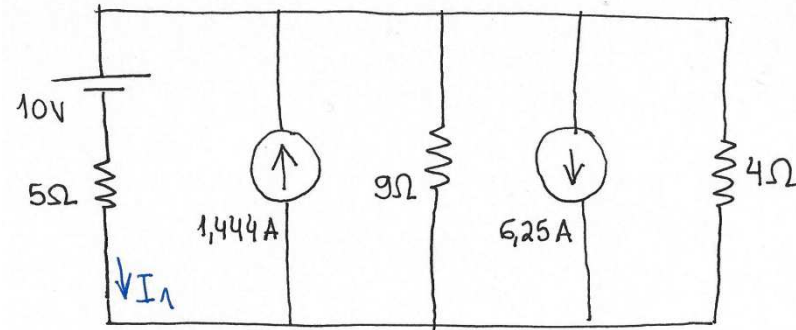


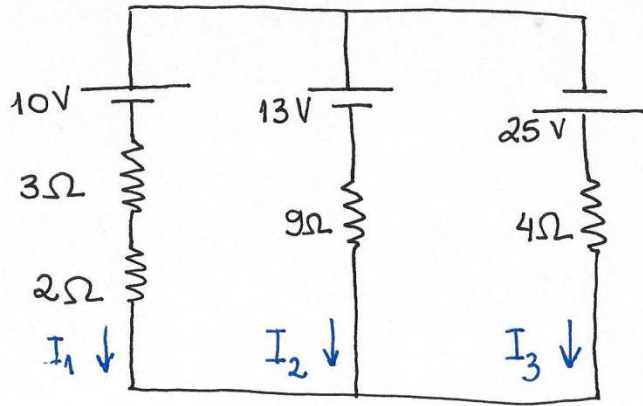Ex. 1.3 (Lista Moodle), resolução por conversão de fontes



$$I_1 = - \frac{(10 + 13,308)}{5 + 2,769 \Omega}$$

$$I_1 = -3A$$


$$V_1 = 10 - 5 \cdot 3 = -5V$$

$$V_2 = V_3 = V_1 = -5V$$

$$V_2 = -5 = 13 - 9(-I_2)$$

$$\rightarrow 9I_2 = -18 \rightarrow I_2 = -2A$$
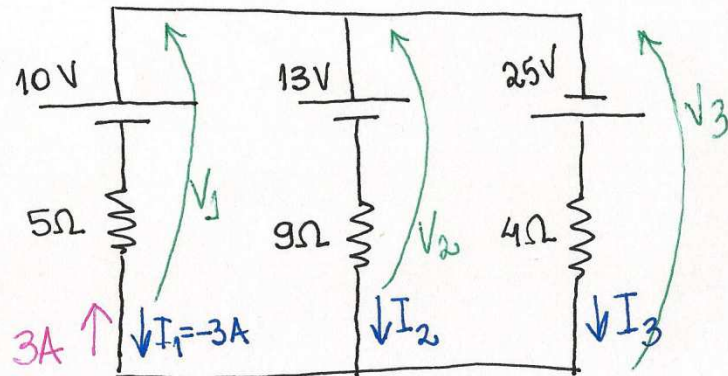
$$V_3 = -5 = -25 + 4I_3 \rightarrow I_3 = 5A$$




PLK/SLK:

$$\text{PLK: } I_1 + I_2 + I_3 = 0$$

$$\text{SLK: } -10 + 13 + 9I_2 - 5I_1 = 0$$

$$-13 - 25 + 4I_3 - 9I_2 = 0$$

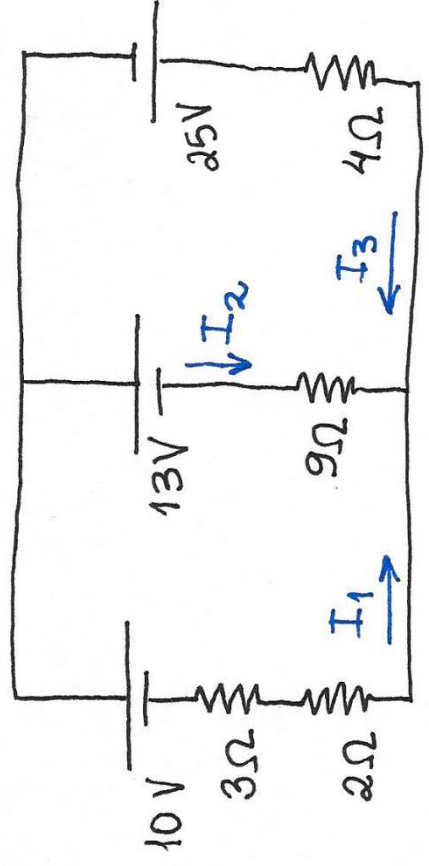

$$\begin{bmatrix} 1 & 1 & 1 \\ -5 & 9 & 0 \\ 0 & -9 & 4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ -3 \\ 38 \end{bmatrix}$$


$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -3 \\ -2 \\ 5 \end{bmatrix}$$

$$I_1 = -3A$$

$$I_2 = -2A$$

$$I_3 = 5A$$

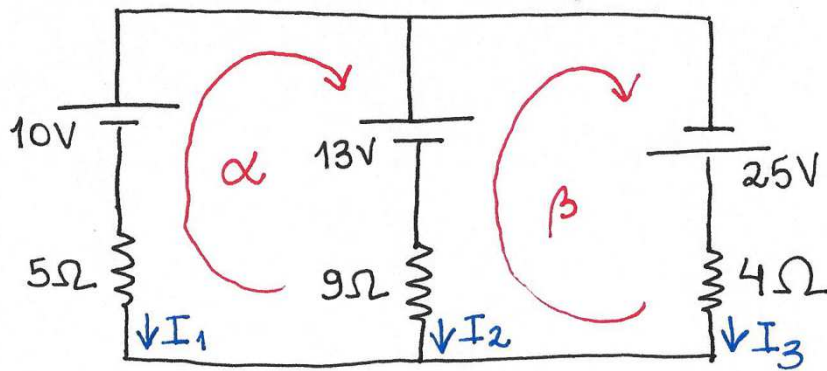Ex. 1.3 (Lista Moodle), resolução pelo método das correntes de Maxwell



$$\begin{aligned} 5\alpha - 10 + 13 + 9(\alpha - \beta) &= 0 \\ 9(\beta - \alpha) - 13 - 25 + 4\beta &= 0 \end{aligned}$$
$$\begin{cases} 14\alpha - 9\beta = -3 \\ -9\alpha + 13\beta = 38 \end{cases}$$

$$\begin{bmatrix} 14 & -9 \\ -9 & 13 \end{bmatrix} \begin{bmatrix} \alpha \\ \beta \end{bmatrix} = \begin{bmatrix} -3 \\ 38 \end{bmatrix}$$


$$\rightarrow \begin{bmatrix} \alpha \\ \beta \end{bmatrix} = \begin{bmatrix} 3 \\ 5 \end{bmatrix}$$

$$I_1 = -\alpha = -3\text{A}$$

$$I_2 = \alpha - \beta = -2\text{A}$$

$$I_3 = \beta = 5\text{A}$$

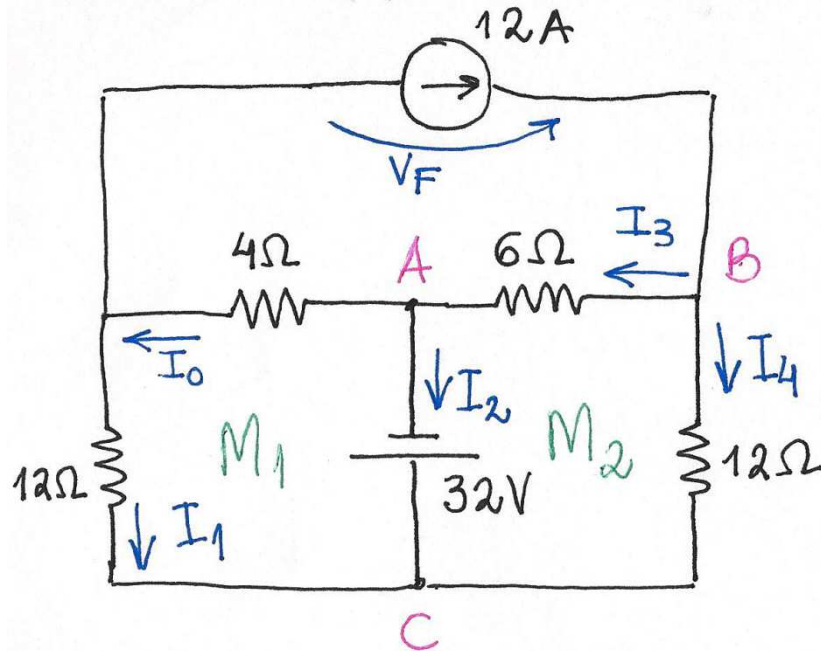Análise de malhas – Circuito com fonte de corrente pertencente a apenas uma malha



PLK/SLK

$$\textcircled{A} \quad -I_0 - I_2 + I_3 = 0$$

$$\textcircled{B} \quad -I_3 - I_4 + 12 = 0$$

$$\textcircled{C} \quad I_1 + I_2 + I_4 = 0$$




$$\textcircled{M_1} \quad -32 - 12I_1 - 4I_0 = 0$$

$$\textcircled{M_2} \quad 32 - 6I_3 + 12I_4 = 0$$

$$\begin{bmatrix} -1 & 0 & -1 & 1 & 0 \\ 0 & 0 & 0 & -1 & -1 \\ 0 & 1 & 1 & 0 & 1 \\ -4 & -12 & 0 & 0 & 0 \\ 0 & 0 & 0 & -6 & 12 \end{bmatrix} \begin{bmatrix} I_0 \\ I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 0 \\ -12 \\ 0 \\ 32 \\ -32 \end{bmatrix} \quad \begin{bmatrix} I_0 \\ I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 7 \text{ A} \\ -5 \text{ A} \\ 2,778 \text{ A} \\ 9,778 \text{ A} \\ 2,222 \text{ A} \end{bmatrix}$$

$$V_F = 6I_3 + 4I_0 = 58,667 + 28 = 86,667 \text{ V}$$
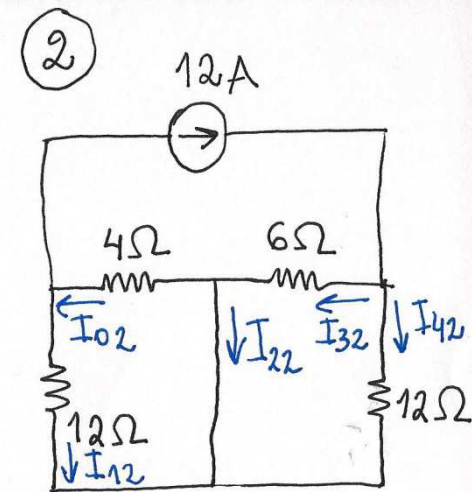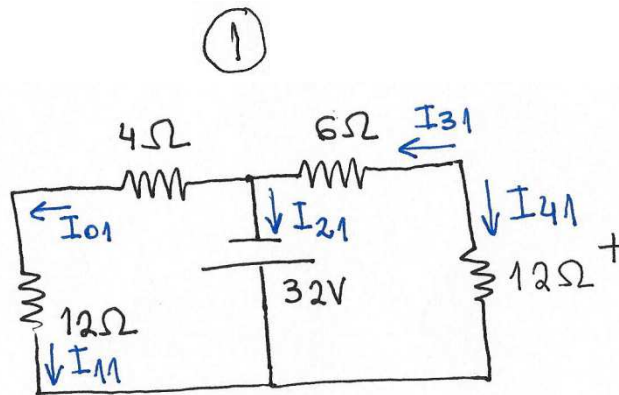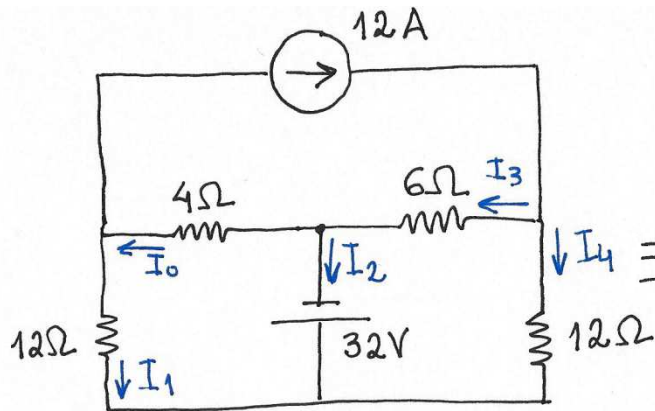
# Circuito com fonte de corrente – Princípio da superposição



Circuito ①:

$$I_{01} = \frac{-32}{16} = -2A; \quad I_{11} = -2A$$

$$I_{31} = \frac{32}{18} = 1,778A; \quad I_{41} = -1,778A$$

$$I_{21} = I_{31} - I_{01} = 1,778 - (-2) = 3,778A$$

$$I_0 = I_{01} + I_{02} = -2 + 9 = 7A$$

$$I_1 = I_{11} + I_{12} = -2 - 3 = -5A$$

$$I_2 = I_{21} + I_{22} = 3,778 - 1 = 2,778A$$

$$I_3 = I_{31} + I_{32} = 1,778 + 8 = 9,778A$$

$$I_4 = I_{41} + I_{42} = -1,778 + 4 = 2,222A$$

Circuito ②:

$$I_{22} = I_{32} - I_{02}$$


$$\begin{cases} -I_{32} - I_{42} + 12 = 0 \\ 6I_{32} = 12I_{42} \end{cases}$$

$$I_{42} = 4A$$


$$I_{32} = 8A$$

$$\begin{cases} -I_{12} + I_{02} - 12 = 0 & I_{12} = -3A \\ 12I_{12} = -4I_{02} & I_{02} = 9A \end{cases}$$

$$I_{22} = 8 - 9 = -1A$$

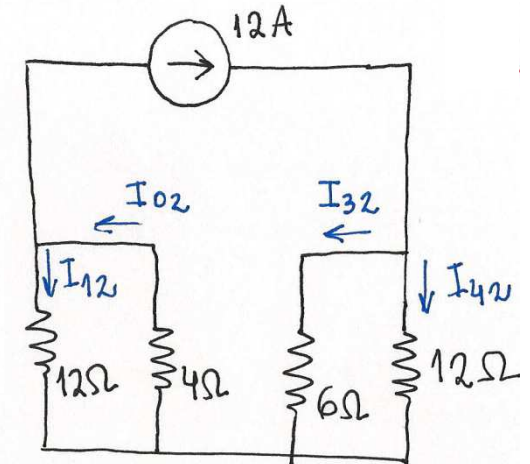

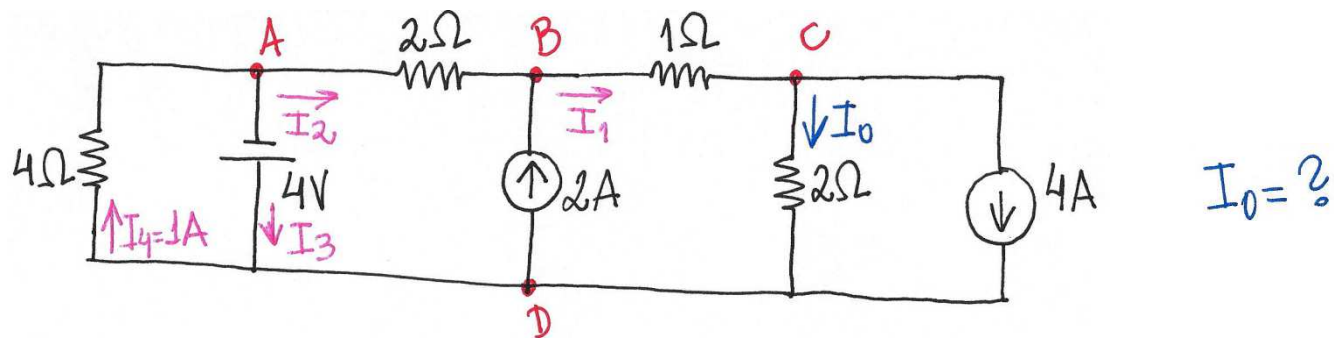Análise de malhas – Circuito com fonte de corrente pertencente a duas malhas



$$\textcircled{A}: -I_2 - I_3 + 1 = 0$$

$$\textcircled{B}: -I_1 + I_2 + 2 = 0$$


$$\textcircled{C}: -I_0 + I_1 - 4 = 0$$

$$\text{ABCD A: } 2I_2 + 1 \cdot I_1 + 2 \cdot I_0 + 4 = 0$$

$$\begin{bmatrix} 0 & 0 & -1 & -1 \\ 0 & -1 & 1 & 0 \\ -1 & 1 & 0 & 0 \\ 2 & 1 & 2 & 0 \end{bmatrix} \begin{bmatrix} I_0 \\ I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -1 \\ -2 \\ 4 \\ -4 \end{bmatrix}$$

$$\begin{bmatrix} I_0 \\ I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -2,4 \text{ A} \\ 1,6 \text{ A} \\ -0,4 \text{ A} \\ 1,4 \text{ A} \end{bmatrix}$$

Outro exemplo com fontes de corrente

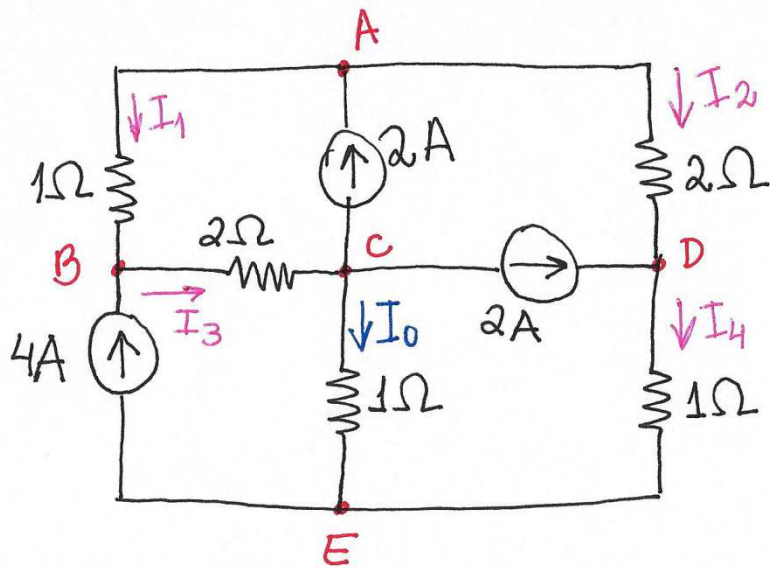

$I_0 = ?$

PLK/SLK:

(A):  $-I_1 + 2 - I_2 = 0$

(B):  $I_1 - I_3 + 4 = 0$


(C):  $-I_0 + I_3 - 2 - 2 = 0$

(D):  $I_2 - I_4 + 2 = 0$

ABCEDA:  $1 \cdot I_1 + 2 \cdot I_3 + 1 \cdot I_0 - 1 \cdot I_4 - 2 \cdot I_2 = 0$

$$\begin{bmatrix} 0 & -1 & -1 & 0 & 0 \\ 0 & 1 & 0 & -1 & 0 \\ -1 & 0 & 0 & 1 & 0 \\ 0 & 0 & 1 & 0 & -1 \\ 1 & 1 & -2 & 2 & -1 \end{bmatrix} \begin{bmatrix} I_0 \\ I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} -2 \\ -4 \\ 4 \\ -2 \\ 0 \end{bmatrix}$$
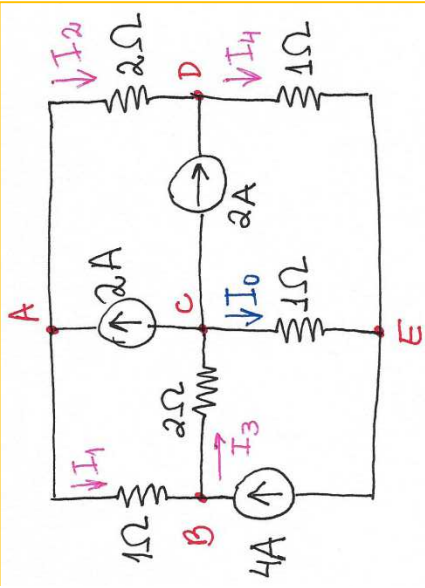
$$\begin{bmatrix} I_0 \\ I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 0 \text{ A} \\ 0 \text{ A} \\ 2 \text{ A} \\ 4 \text{ A} \\ 4 \text{ A} \end{bmatrix}$$



$$-I_{01} + I_{x1} - 2 = 0$$



$$I_{01} \cdot 4 = -I_{x1} \cdot 3$$

$$I_{x1} = -\frac{4}{3} I_{01}$$

$$-I_{01} - \frac{4}{3} I_{01} - 2 = 0$$

$$-\frac{7}{3} I_{01} = 2$$

$$I_{01} = -\frac{6}{7} A$$

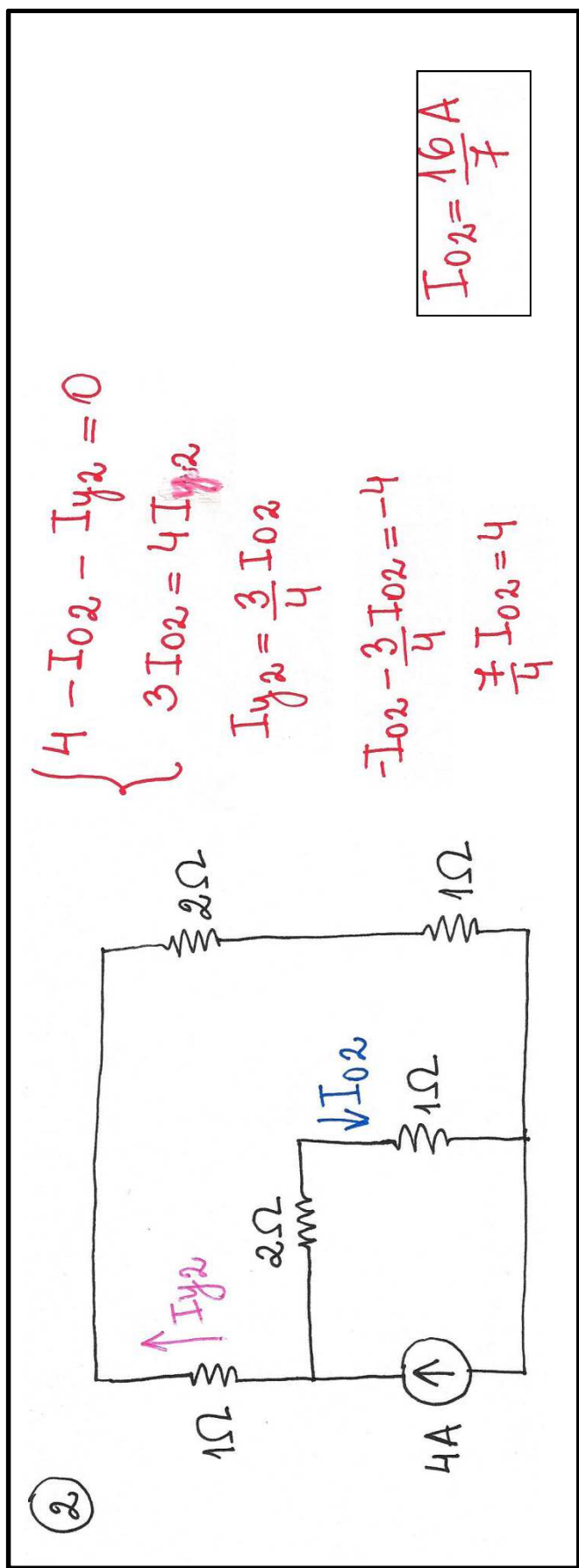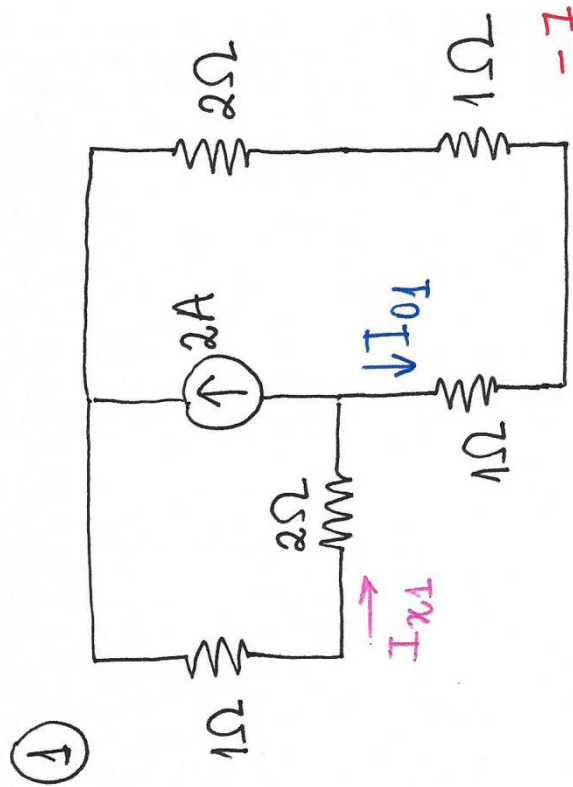

$$4 - I_{02} - I_{y2} = 0$$

$$3 I_{02} = 4 I_{y2}$$



$$I_{y2} = \frac{3}{4} I_{02}$$

$$-I_{02} - \frac{3}{4} I_{02} = -4$$

$$\frac{7}{4} I_{02} = 4$$

$$I_{02} = \frac{16}{7} A$$



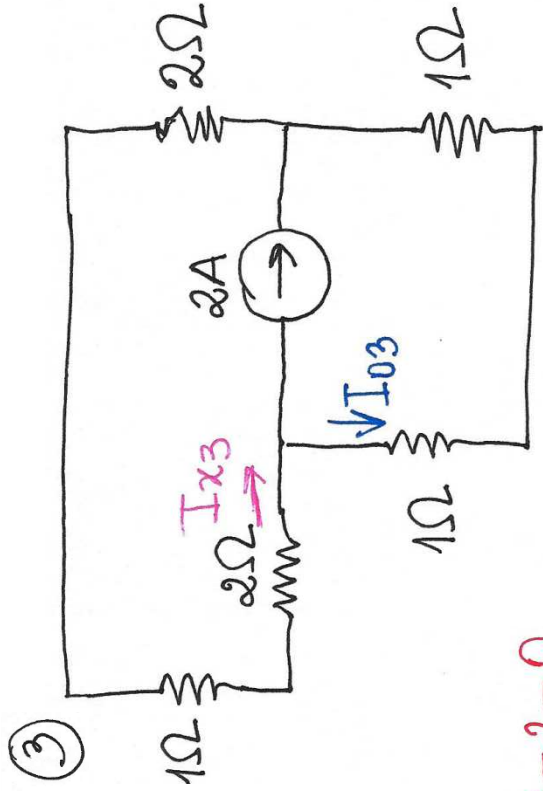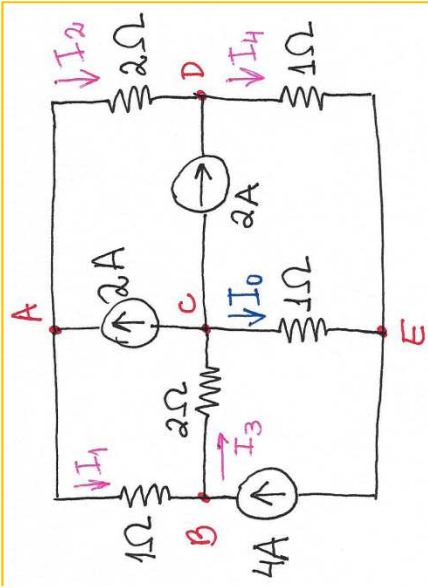

$$\left. \begin{aligned} -I_{03} + I_{x3} - 2 &= 0 \\ 2I_{03} &= -5I_{13} \end{aligned} \right\}$$

$$I_{13} = -\frac{2}{5} I_{03}$$

$$-I_{03} - 2I_{03} - 2 = 0$$

$$\frac{7}{5} I_{03} = -2$$





$$I_{03} = -\frac{10}{7} \text{ A}$$





$$I_0 = I_{01} + I_{02} + I_{03}$$


$$I_0 = -\frac{6}{7} + \frac{16}{7} - \frac{10}{7}$$

$$I_0 = 0 \text{ A}$$
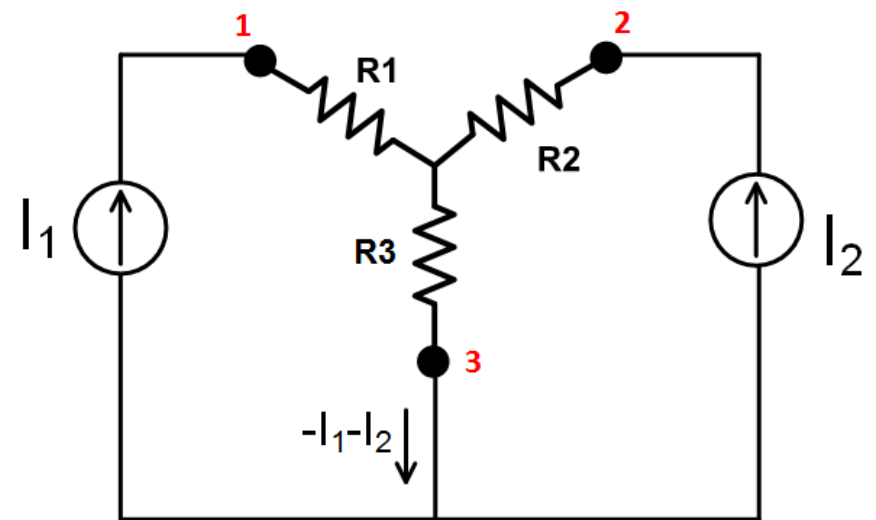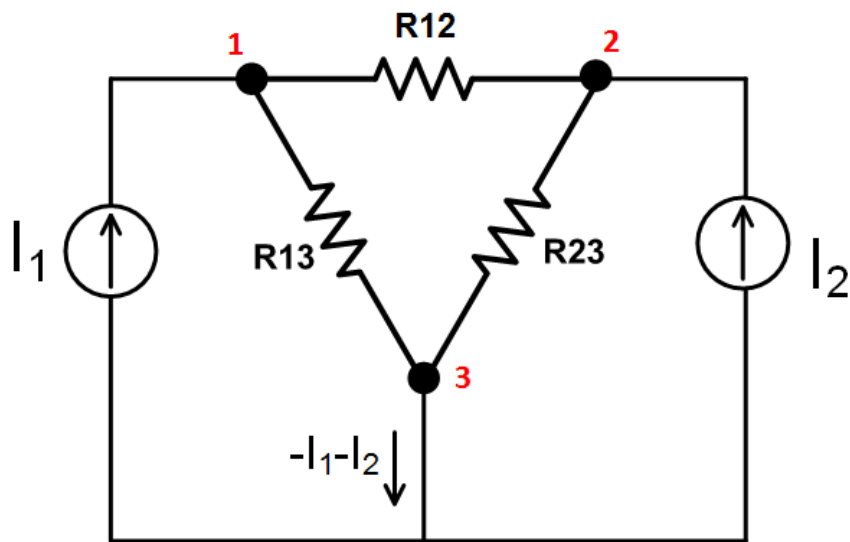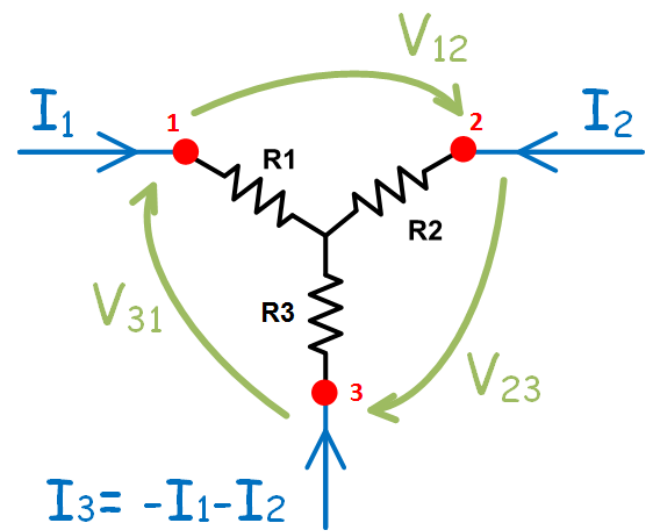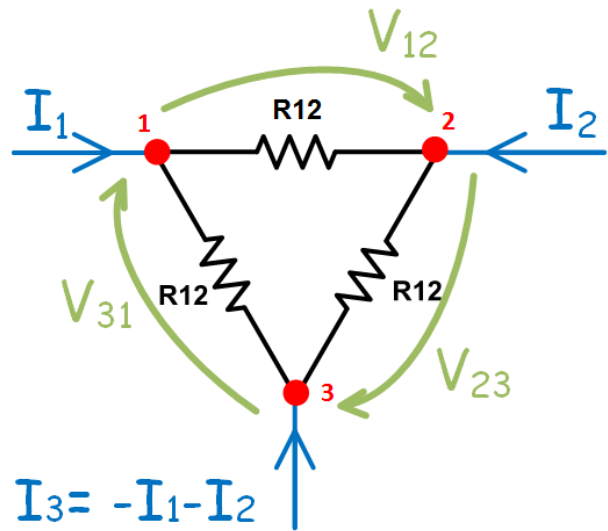
# Transformação $\Delta \leftrightarrow Y$




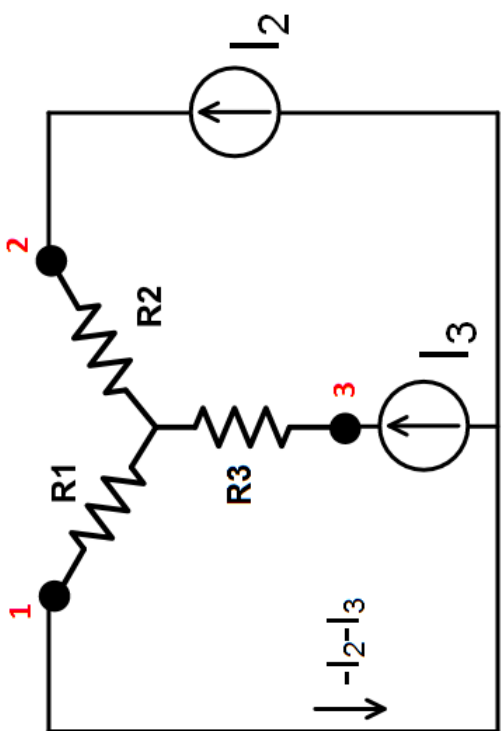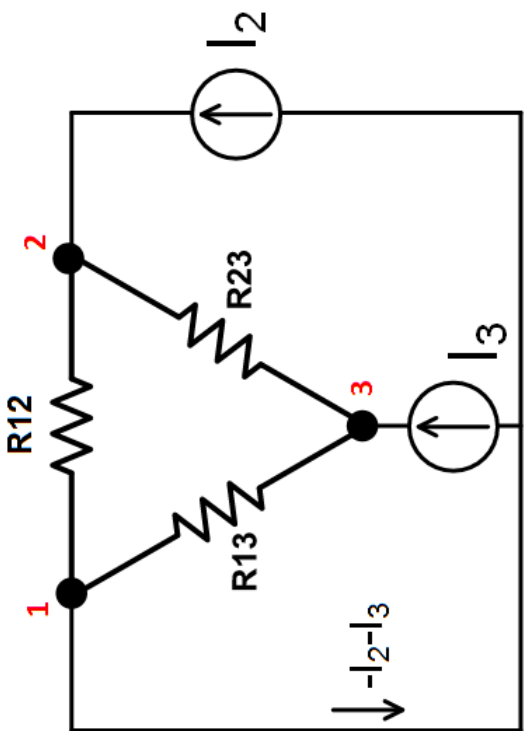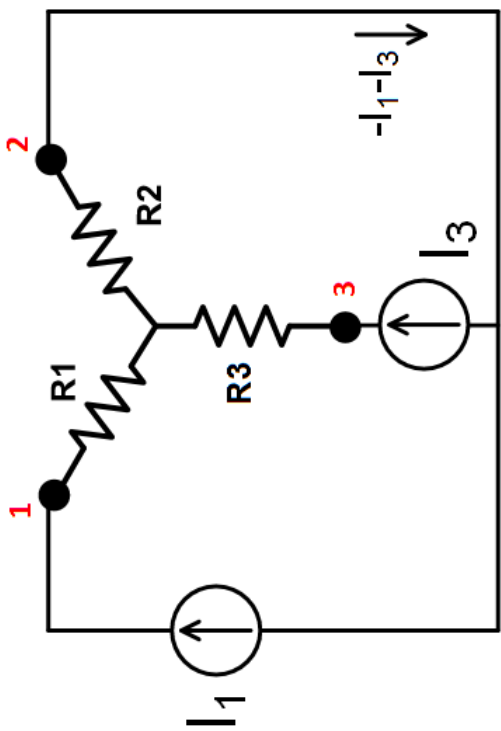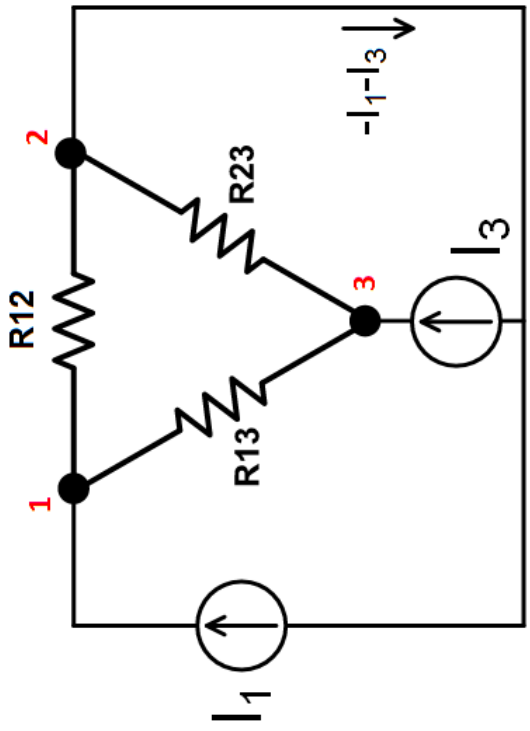

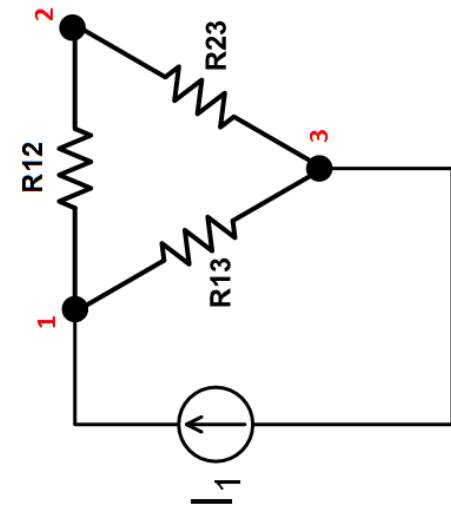


$$R_1 + R_2 = R_{13} \parallel (R_{12} + R_{23})$$
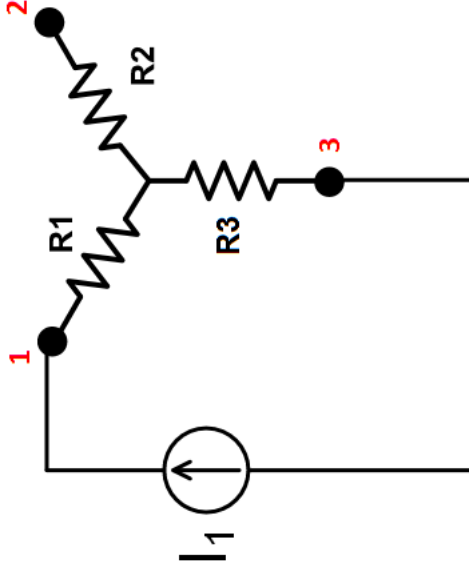
$$= \frac{R_{12} R_{13} + R_{13} R_{23}}{R_{12} + R_{13} + R_{23}}$$





$$R_2 + R_3 = R_{23} \parallel (R_{12} + R_{13})$$
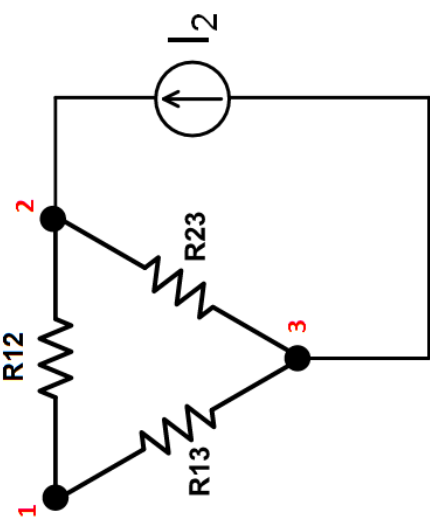
$$= \frac{R_{12} R_{23} + R_{13} R_{23}}{R_{12} + R_{13} + R_{23}}$$



$$R_1 + R_2 = R_{12} \parallel (R_{13} + R_{23})$$
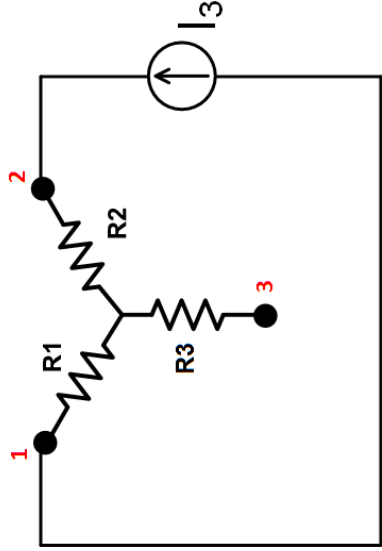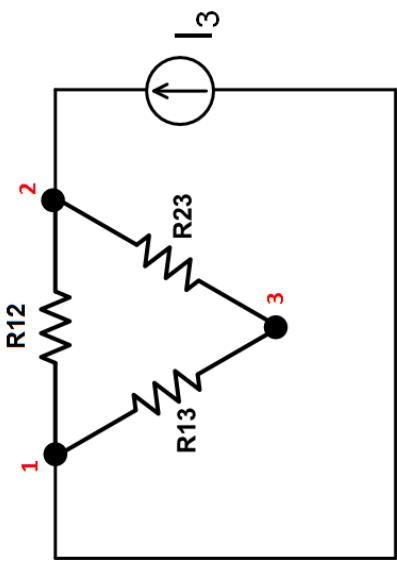
$$= \frac{R_{12} R_{13} + R_{12} R_{23}}{R_{12} + R_{13} + R_{23}}$$



$$R_1 + R_3 = R_{13} // (R_{12} + R_{13} R_{23})$$

$$R_2 + R_3 = R_{23} // (R_{12} + R_{13}) = \frac{R_{12} R_{23} + R_{13} R_{23}}{R_{12} + R_{13} + R_{23}}$$

$$R_1 + R_2 = R_{12} // (R_{13} + R_{23}) = \frac{R_{12} R_{13} + R_{12} R_{23}}{R_{12} + R_{13} + R_{23}}$$

$$\frac{R_1}{R_3} = \frac{R_{12}}{R_{23}} \rightarrow R_{23} = R_{12} \frac{R_3}{R_1} \quad \frac{R_2}{R_3} = \frac{R_{12}}{R_{13}} \rightarrow R_{13} = R_{12} \frac{R_3}{R_2}$$

$$R_1 = \frac{R_{12}}{R_{13}} \left( \frac{R_{12}}{R_2} \frac{R_3}{R_2} \right) \times \frac{R_2 R_1}{R_{12}} + \left( \frac{R_{12}}{R_2} \frac{R_3}{R_1} \right) \times \frac{R_2 R_1}{R_{12}}$$

$$R_1 = \frac{R_{12} R_1 R_3}{R_{13} R_2 + R_1 R_3 + R_2 R_3}$$

$$R_{12} = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3}$$

$$R_{13} = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2}$$




$$R_{23} = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$$

$$R_1 = \frac{R_{12} R_{13}}{R_{12} + R_{13} + R_{23}}$$

$$R_2 = \frac{R_{12} R_{23}}{R_{12} + R_{13} + R_{23}}$$

$$R_3 = \frac{R_{13} R_{23}}{R_{12} + R_{13} + R_{23}}$$

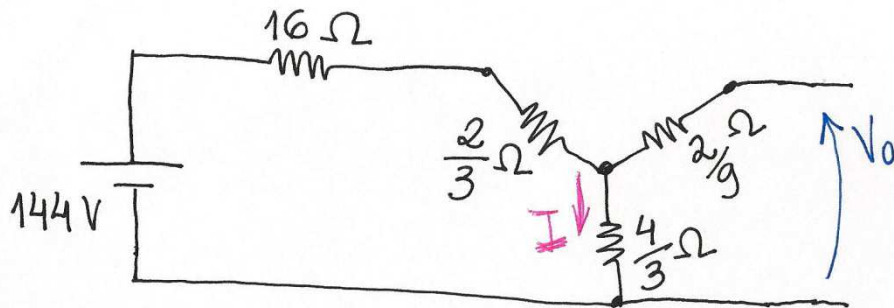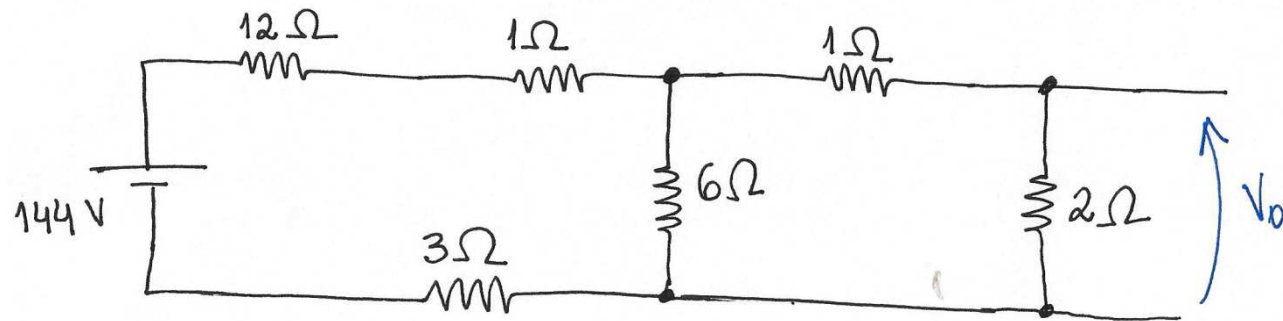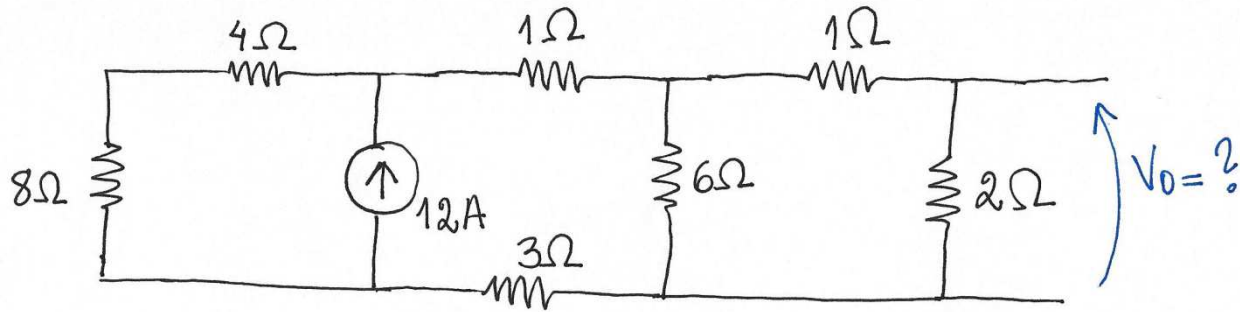Exemplo de resolução por transformação  $\Delta \leftrightarrow Y$



$$V_0 = 0.2 + \frac{4}{3} I$$

$$I = \frac{144}{16 + \frac{2}{3} + \frac{4}{3}} = 8A$$

$$V_0 = \frac{4}{3} \cdot 8 = \frac{32}{3} A$$