




MAC0329

23/06/2020

BOM DIA!

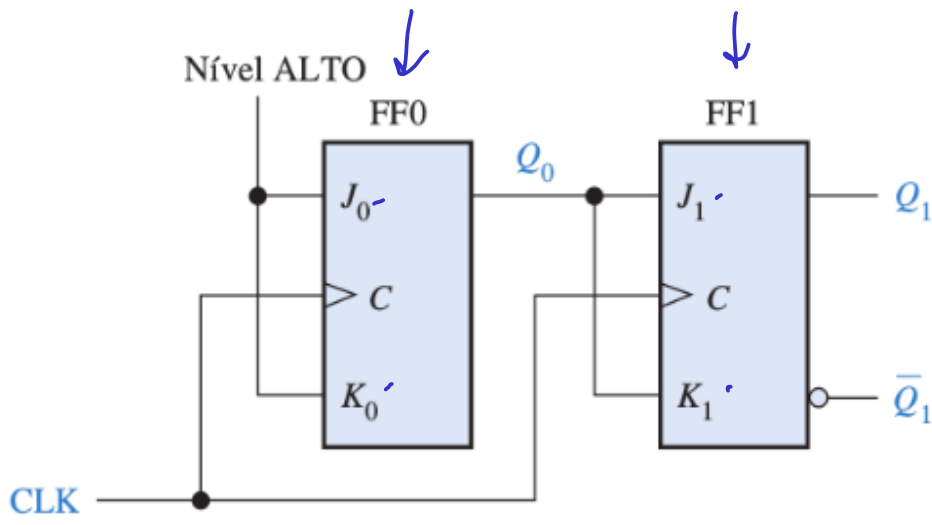- Análise de Circuitos Seq.
- Logisim + EP3



J	K	Q	Q*
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$$Q^* = ? \quad J\bar{Q} + \bar{K}Q$$

JK	0	1
00	0	1
01	0	0
11	1	0
10	1	1

Annotations: A green circle around the '1' in the 00 row is labeled $\bar{K}Q$. A green circle around the '1' in the 10 row is labeled $J\bar{Q}$.

1) Sinais dos J e K

2) Equação do próximo estado

$$J_0 = K_0 = 1$$

$$J_1 = K_1 = Q_0$$


$$Q_0^* = J_0 \bar{Q}_0 + \bar{K}_0 Q_0$$

$$= 1 \cdot \bar{Q}_0 + 0 \cdot Q_0 = \bar{Q}_0$$

3) Tabela de transição de estados

$Q_1 Q_0$	$Q_1^* Q_0^*$
00	01
01	10
10	11
11	00

4) Diagrama de Trans. Estados

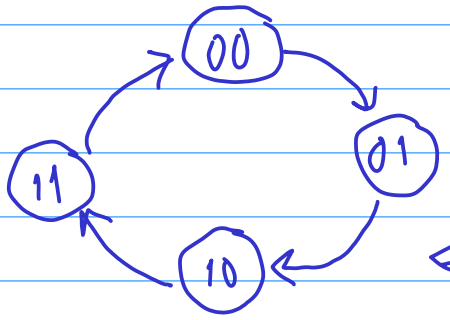


$$Q_1^* = J_1 \bar{Q}_1 + \bar{K}_1 Q_1$$

$$= Q_0 \bar{Q}_1 + \bar{Q}_0 Q_1 = Q_0 \oplus Q_1$$

← contador de 2 bits módulo 2^2

$S=R=1 \Rightarrow$ don't care

$$Q^* = S + Q\bar{R}$$

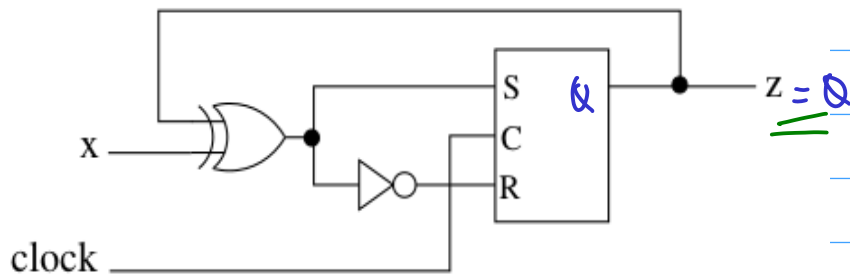

3) Tabela de Trans. Est.

1) Sinal de S e R

$$S = x \oplus Q$$

$$R = \overline{x \oplus Q} = \bar{S}$$

Q	Q^*/z	
	$x=0$	$x=1$
<u>0</u>	0/0	1/1 $\rightarrow Q^*/z$
<u>1</u>	1/1	0/0

2) Próximo estado Q^*

$$Q^* = \underbrace{x \oplus Q}_S + Q(\overline{x \oplus Q}) = \underbrace{x \oplus Q}_S = S$$

4) Diagrama

