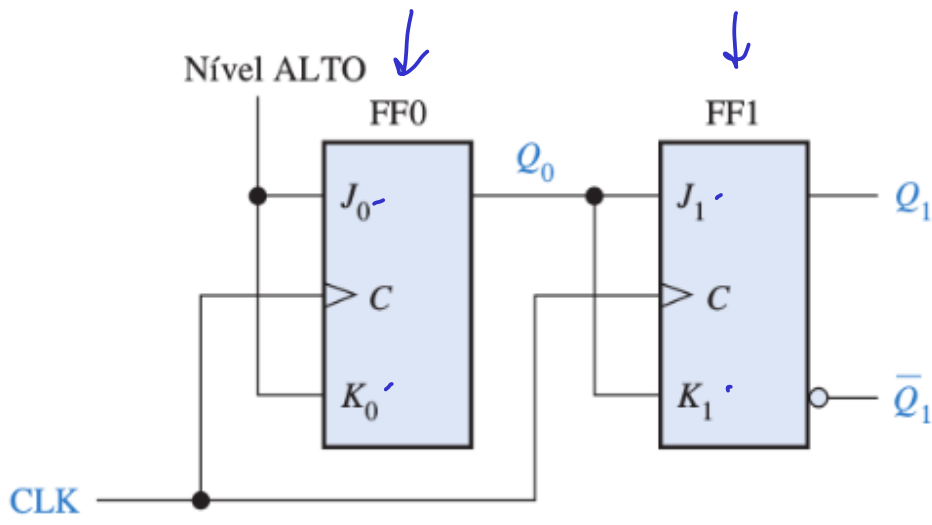


MAC0329

25/06/2020

BOM DIA!



| J | K | Q | Q* |
|---|---|---|----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

$Q^* = ? \quad J\bar{Q} + \bar{K}Q$

| JK | Q | Q* |
|----|---|----|
| 00 | 0 | 1 |
| 01 | 0 | 0 |
| 11 | 1 | 0 |
| 10 | 1 | 1 |

Annotations: $\bar{K}Q$ points to the 00 row, $J\bar{Q}$ points to the 10 row.

1) Sinais dos J e K

$J_0 = K_0 = 1$
 $J_1 = K_1 = Q_0$

2) Equação do próximo estado


$Q_0^* = J_0\bar{Q}_0 + \bar{K}_0Q_0$
 $= 1\bar{Q}_0 + 0Q_0 = \bar{Q}_0$

3) Tabela de transição de estados

| Q_1Q_0 | $Q_1^*Q_0^*$ |
|----------|--------------|
| 00 | 01 |
| 01 | 10 |
| 10 | 11 |
| 11 | 00 |

Annotations: Two upward-pointing arrows are under the 10 and 11 rows.

4) Diagrama de Trans. Estados

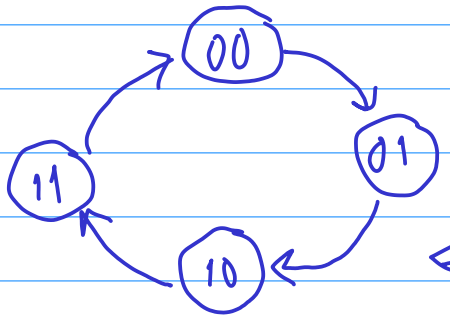


← contador de 2 bits módulo 2²

$Q_1^* = J_1\bar{Q}_1 + \bar{K}_1Q_1$
 $= Q_0\bar{Q}_1 + \bar{Q}_0Q_1 = Q_0 \oplus Q_1$

$S=R=1 \Rightarrow$ don't care

$$Q^* = S + Q\bar{R}$$

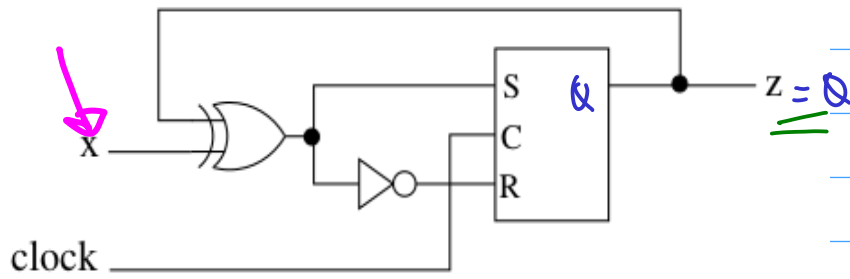

3) Tabela de Trans. Est.

1) Sinal de S e R

$$S = x \oplus Q$$


$$R = \overline{x \oplus Q} = \bar{S}$$

| Q | Q^*/z | |
|----------|---------|-------------------------|
| | $x=0$ | $x=1$ |
| <u>0</u> | 0/0 | 1/1 $\rightarrow Q^*/z$ |
| <u>1</u> | 1/1 | 0/0 |

2) Próximo estado Q^*


$$Q^* = \underbrace{x \oplus Q}_S + Q(\overline{x \oplus Q}) = \underbrace{x \oplus Q}_S = S$$

4) Diagrama

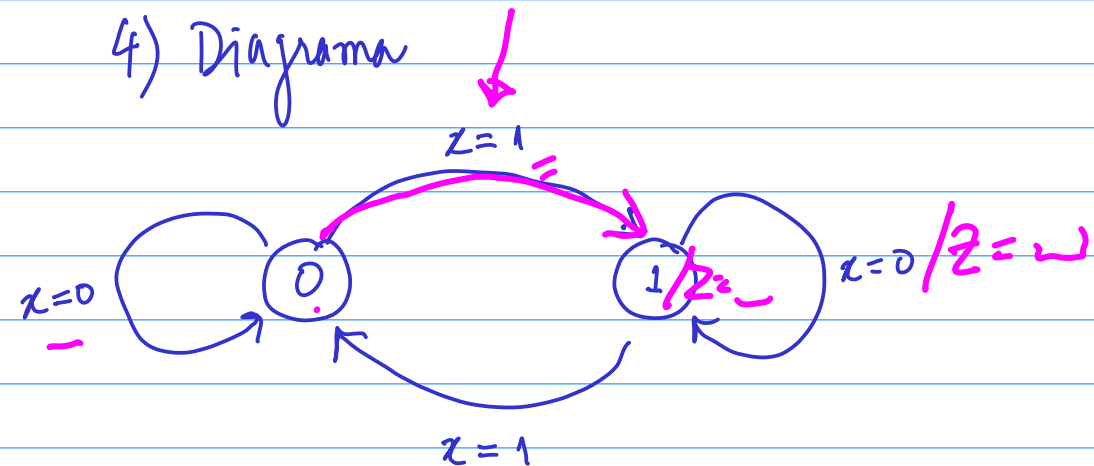

Projeto de circuitos sequenciais

①


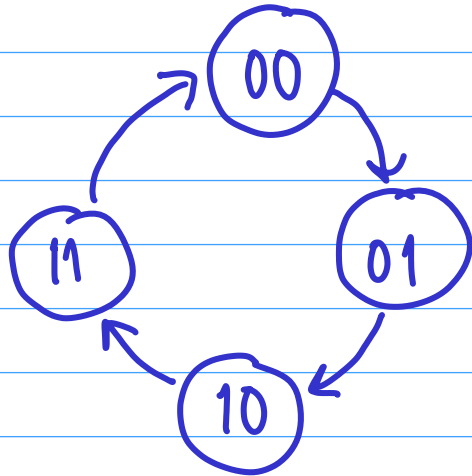


| Q_1, Q_0 | Q_1^*, Q_0^* |
|------------|----------------|
| 00 | 01 |
| 01 | 10 |
| 10 | 11 |
| 11 | 00 |

| $Q \rightarrow Q^*$ | J | K |
|---------------------|---|---|
| 0 \rightarrow 0 | 0 | x |
| 0 \rightarrow 1 | 1 | x |
| 1 \rightarrow 0 | x | 1 |
| 1 \rightarrow 1 | x | 0 |

$$Q_0^* = f_0(Q_0, Q_1) \quad Q_1^* = f_1(Q_0, Q_1)$$

② Quanto FFs? 2 flip-flops

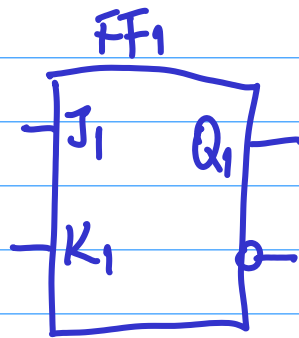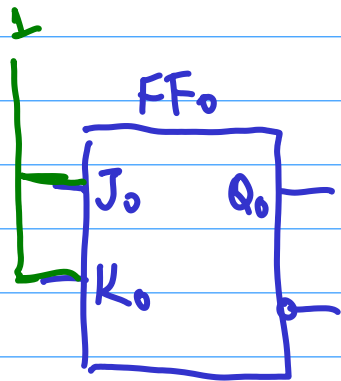

| Q_1 / Q_0 | 0 | 1 |
|-------------|---|---|
| 0 | 1 | x |
| 1 | 1 | x |


$J_0 = 1$

| Q_1 / Q_0 | 0 | 1 |
|-------------|---|---|
| 0 | x | 1 |
| 1 | x | 1 |

$K_0 = 1$

Projeto de circuitos sequenciais

1

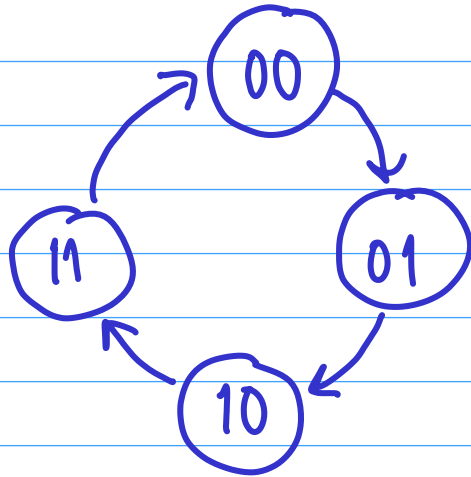


| Q_1, Q_0 | Q_1^* | Q_0^* |
|------------|---------|---------|
| 00 | 0 | 1 |
| 01 | 1 | 0 |
| 10 | 1 | 1 |
| 11 | 0 | 0 |

| $Q \rightarrow Q^*$ | J | K |
|---------------------|---|---|
| 0 → 0 | 0 | x |
| 0 → 1 | 1 | x |
| 1 → 0 | x | 1 |
| 1 → 1 | x | 0 |

~~$Q_0^* = f_0(Q_0, Q_1)$~~ $Q_1^* = f_1(Q_0, Q_1)$

2) Quanto FFs? 2 flip-flops


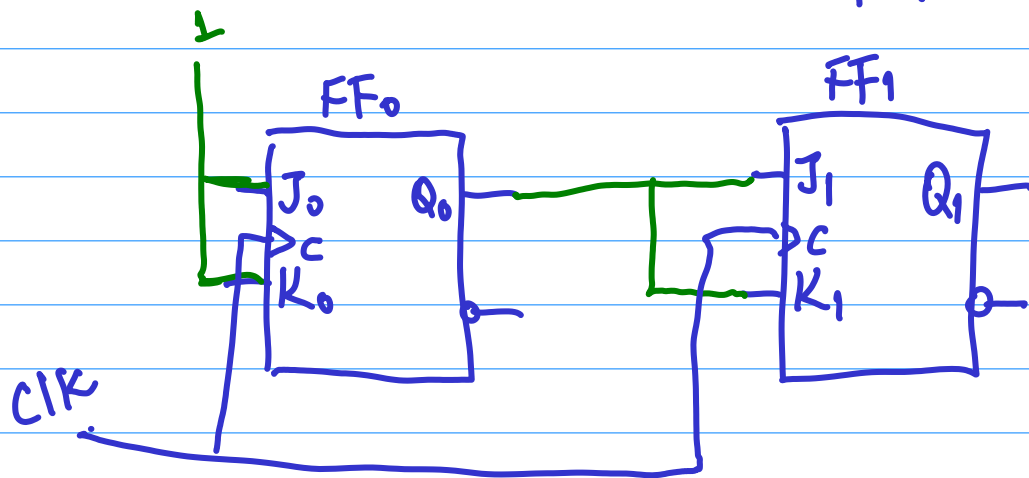


| Q_1/Q_0 | 0 | 1 |
|-----------|---|---|
| 0 | 0 | 1 |
| 1 | x | x |

$J_1 = Q_0$

| Q_1/Q_0 | 0 | 1 |
|-----------|---|---|
| 0 | x | x |
| 1 | 0 | 1 |

$K_1 = Q_0$

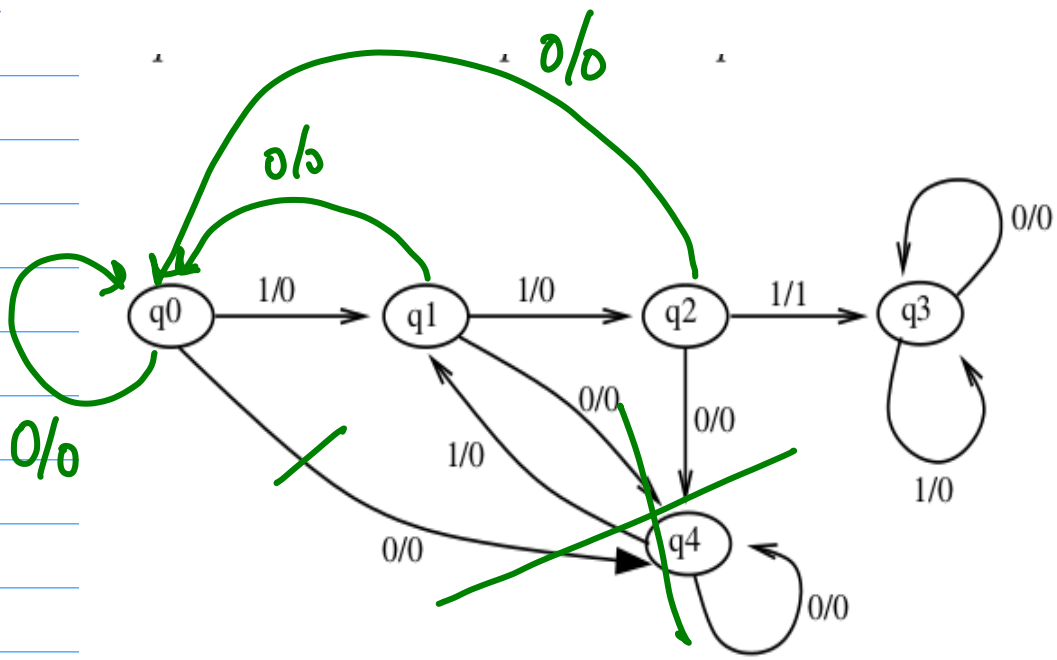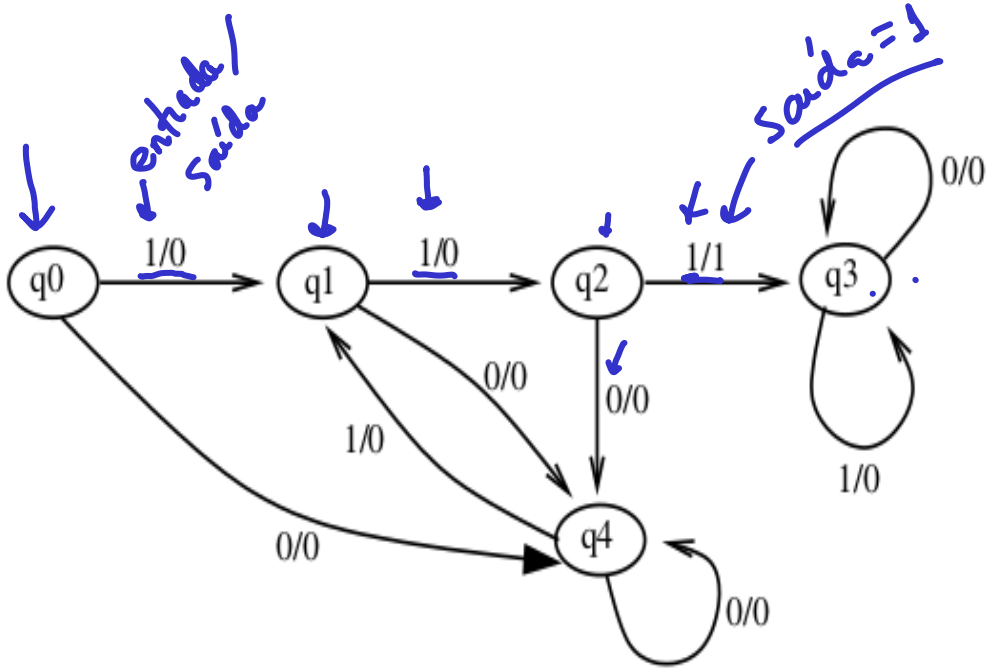

| Estado atual | Próx. estado/saída | |
|--------------|--------------------|---------|
| | $x = 0$ | $x = 1$ |
| q_0 | $q_0/0$ | $q_1/0$ |
| q_1 | $q_0/0$ | $q_2/0$ |
| q_2 | $q_0/0$ | $q_3/1$ |
| q_3 | $q_3/0$ | $q_3/0$ |
| q_4 | $q_4/0$ | $q_1/0$ |

Handwritten green annotations: The first and last rows of the table are highlighted with a green box. Green arrows point to the $q_1/0$ and $q_1/0$ cells. A green bracket is drawn under the last two rows.

| Estados atual | Próximo estado | |
|------------------|----------------|-------|
| | x=0 | x=1 |
| a | a/0 | c/0 |
| b | a/0 | d/1 ← |
| c | a/0 | b/0 |
| d | d/0 | d/0 |

| Estados | Associação | | |
|---------|------------|----|----|
| | 1 | 2 | 3 |
| a | 00 | 00 | 00 |
| b | 01 | 11 | 10 |
| c | 11 | 01 | 01 |
| d | 10 | 10 | 11 |

x 1
x 1

Associação 3

| | $Q_1^* Q_0^*$ | |
|---|---------------|-----|
| | x=0 | x=1 |
| a | 00 | 01 |
| b | 00 | 11 |
| c | 00 | 10 |
| d | 11 | 11 |

| $Q_1^* Q_0^*$ | 0 | 1 |
|---------------|---|---|
| 00 | — | |
| 01 | | |
| 11 | | |
| 10 | | |

| $Q_1^* Q_0^*$ | 0 | 1 |
|---------------|---|---|
| 00 | — | |
| 01 | | |
| 11 | | |
| 10 | | |

$J_1 =$

$K_1 =$

| Estados atual | Próximo estado | |
|---------------|----------------|-----|
| | x=0 | x=1 |
| a | a/0 | c/0 |
| b | a/0 | d/1 |
| c | a/0 | b/0 |
| d | d/0 | d/0 |

| Q → Q* | J | K |
|--------|---|---|
| 0 → 0 | 0 | X |
| 0 → 1 | 1 | X |
| 1 → 0 | X | 1 |
| 1 → 1 | X | 0 |

$$Z = x Q_1 \bar{Q}_0$$

Associação 3 $Q_1^* Q_0^*$

| | $Q_1^* Q_0^*$ | |
|---|---------------|-----|
| | x=0 | x=1 |
| a | 00 | 01 |
| b | 00 | 11 |
| c | 00 | 10 |
| d | 11 | 11 |

| $Q_1 Q_0$ \ x | 0 | 1 |
|---------------|---|---|
| 00 | 0 | 0 |
| 01 | 0 | 1 |
| 11 | X | X |
| 10 | X | X |

$$J_1 = Q_0 x$$

| $Q_1 Q_0$ \ x | 0 | 1 |
|---------------|---|---|
| 00 | X | X |
| 01 | X | X |
| 11 | 0 | 0 |
| 10 | 1 | 0 |

$$K_1 = \bar{Q}_0 \bar{x}$$


$$J_0 = x$$

$$J_1 = x Q_0$$

$$z = x Q_1 \bar{Q}_0$$

$$K_0 = \bar{Q}_1$$

$$K_1 = \bar{x} \bar{Q}_0$$

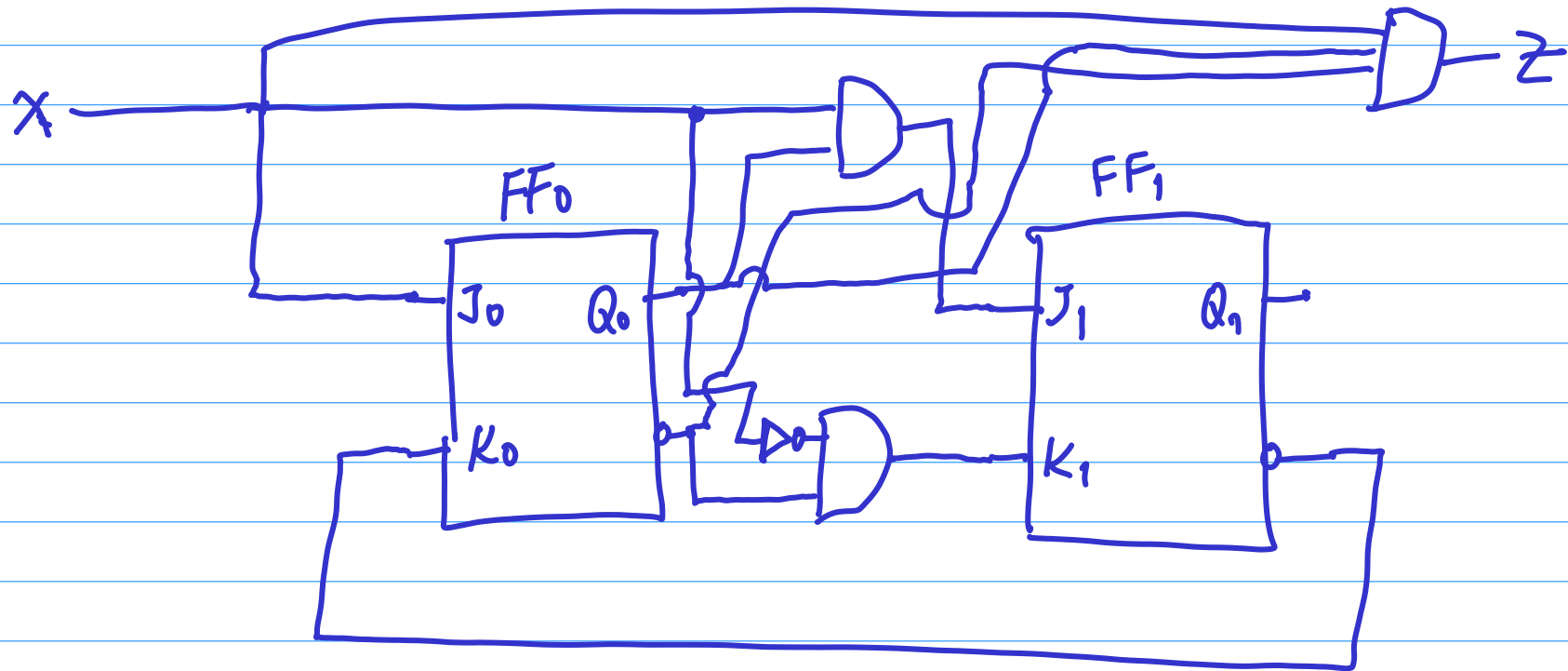

Mealy \rightarrow saída depende de Q e de x ~~\neq~~

Moore \rightarrow saída depende de Q ~~\neq~~

Máquina de estados

$(Q, q_0, \Sigma, O, \delta, \gamma)$

alf. entrada

alf. saída

transição de est.
 $\delta: Q \times \Sigma \rightarrow Q$

$\begin{cases} \lambda: Q \times \Sigma \rightarrow O \\ \lambda: Q \rightarrow O \end{cases}$