
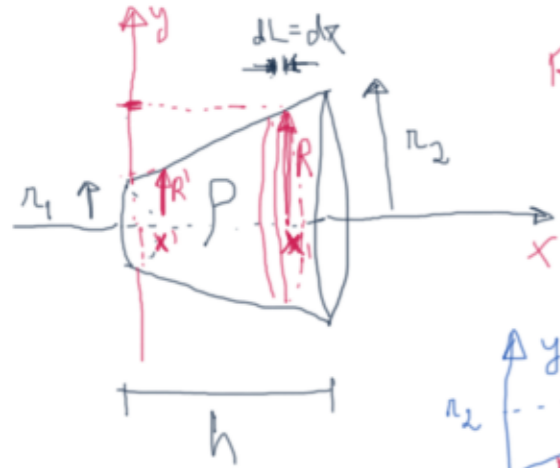


25.63, p. 164

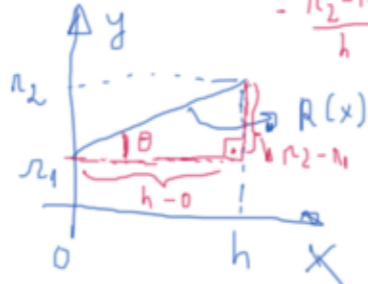

$$R = R(x)$$

$$m = \tan \theta = \frac{r_2 - r_1}{h}$$



$$R(x) = mx + r_1$$

a) $R = ?$

$$R = \rho \cdot \frac{L}{A} \quad R(x) = \left(\frac{r_2 - r_1}{h} \right) x + r_1$$

$$dR = \rho \frac{dL}{A}$$

$$R(x) = Ax + r_1$$

$$\int_0^R dR' = \int_{\text{compr.}} \rho \frac{dL}{A} = \int_0^h \rho \frac{dx}{\pi [R(x)]^2}$$

$$R = \frac{\rho}{\pi} \int_{x=0}^{x=h} \frac{1}{(Ax + r_1)^2} dx$$

$$u = Ax + r_1$$

$$\frac{du}{dx} = A \rightarrow du = A dx \rightarrow \frac{1}{A} du = dx$$

$$x=0 \rightarrow u = r_1$$

$$x=h \rightarrow u = A \cdot h + r_1 = \frac{r_2 - r_1}{h} h + r_1 = r_2$$

$$R = \frac{\rho}{A\pi} \int_{r_1}^{r_2} \frac{1}{u^2} du =$$

$$= \frac{\rho}{A\pi} \int_{r_1}^{r_2} u^{-2} du$$


$$\int x^n dx = \frac{x^{n+1}}{n+1} + k$$

$$= \frac{\rho}{\pi A} \left[-\frac{1}{u} \right]_{r_1}^{r_2} = \frac{\rho h}{\pi(r_2 - r_1)} \left(\frac{1}{r_1} - \frac{1}{r_2} \right) =$$


$$= \frac{\rho h}{\pi(r_2 - r_1)} \cdot \frac{r_2 - r_1}{r_1 r_2} \rightarrow R = \frac{\rho h}{\pi r_1 r_2}$$

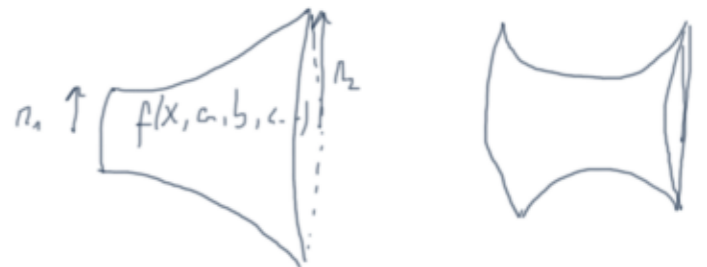b) $r_1 = r_2 = r$ \rightarrow

$$R = \frac{\rho h}{\pi r^2} = \rho \cdot \frac{h}{A} \rightarrow \text{cilindro}$$



Circuitos Elétricos

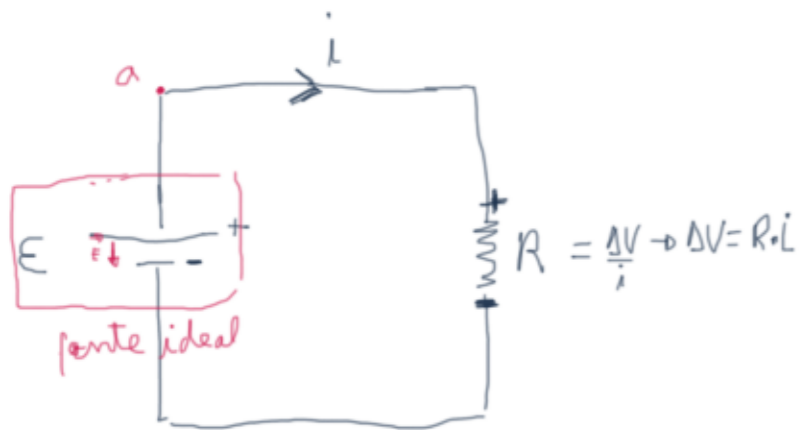

ENERGIA

$$P = \Delta V \cdot i = \frac{\text{Energia}}{\Delta t}$$

↓
potência

Na bateria ideal: $P = \epsilon \cdot i$

No resistor: $P = Ri^2 = \frac{\Delta V^2}{R}$


Corrente elétrica

A) Balanço energético:

$$P_{\text{bateria}} = P_{\text{resistor}}$$

$$\epsilon \cdot i = Ri^2 \rightarrow i = \frac{\epsilon}{R}$$

(bateria ideal)

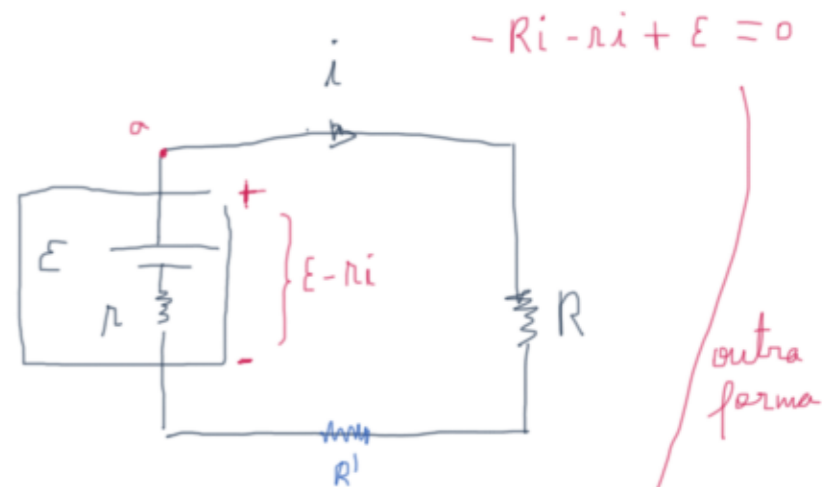

$$P_{\text{bateria}} = P_{\text{resistor}}$$

$$(\epsilon - r \cdot i) i = Ri^2$$

$$\epsilon - r i = R i$$

$$i = \frac{\epsilon}{R + r + R'}$$

(bateria real)

outra forma

B) Balanço de Tensões


$$V_A - V_B = \oint_A^B \vec{E} \cdot d\vec{l} = \int_A^C \dots + \int_C^D \dots + \int_D^B \dots = 0$$

Para o circuito ideal:

$$\rightarrow Ri + \epsilon = 0 \rightarrow i = \frac{\epsilon}{R}$$

Associação de Resistores

Série

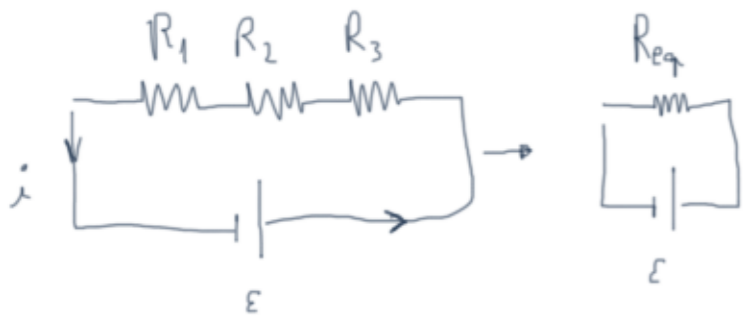

$$E = \underbrace{\Delta V_1}_{R_1 \cdot i} + \underbrace{\Delta V_2}_{R_2 \cdot i} + \underbrace{\Delta V_3}_{R_3 \cdot i}$$

$$E = (R_1 + R_2 + R_3) \cdot i$$


$$E = R_{eq} \cdot i$$

$$R_{eq} = R_1 + R_2 + R_3$$

$$R_{eq} = \sum_{j=1}^{j=N} R_j$$

Paralelo

$$R = \frac{\Delta V}{i}$$

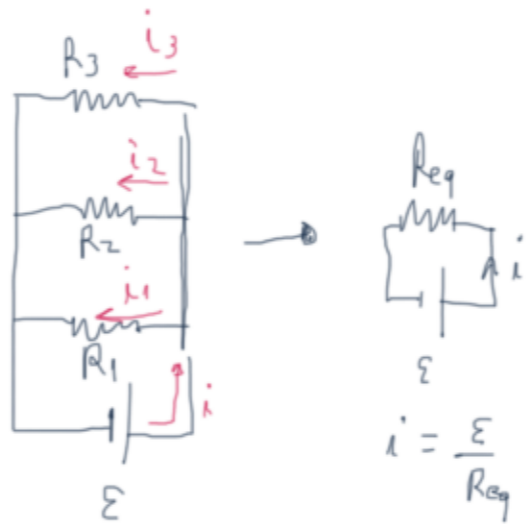

$$i = \frac{E}{R_{eq}}$$

$$i = i_1 + i_2 + i_3$$


$$= \frac{E}{R_1} + \frac{E}{R_2} + \frac{E}{R_3}$$

$$= E \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_{eq}} = \sum_{j=1}^N \frac{1}{R_j}$$

$$25.31, p. 161$$

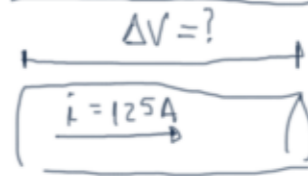

$$d = 10,0 \text{ cm}$$

$$L = 100 \text{ km}$$

$$A = \frac{\pi d^2}{4}$$

a) $\Delta V = ?$

$$\Delta V = E L$$

$$E = \rho J = \rho \frac{i}{A}$$

$$\rho_{cu} = 1,72 \cdot 10^{-8} \Omega \cdot m$$

$$\Delta V = \rho \frac{i}{A} \cdot L$$

$$= \frac{1,72 \cdot 10^{-8} \cdot 125 \cdot 100 \cdot 10^3}{\pi \frac{(10,0 \cdot 10^{-2})^2}{4}} = 27,4 \text{ V}$$

$$b) P = \Delta V \cdot i$$

$$P = 27,4 \cdot 125$$

$$P = 3,42 \cdot 10^3 \text{ W}$$

$$\text{ou}$$
$$P = 3,42 \text{ kW}$$

$$E_{1h} = P \cdot \Delta t$$
$$= 3,42 \cdot 10^3 \cdot 3600$$
$$= 1,23 \cdot 10^7 \text{ J}$$

$$E_{1h} = 3,42 \text{ kW} \cdot 1h$$

$$E_{1h} = 3,42 \text{ kWh}$$