

Exercício 7

00000

sem sinal $\rightarrow 0$

compl. 1 $\rightarrow 0$

compl. 2 $\rightarrow 0$

} valor de acordo com as três interpretações

complemento de 1 = 11111 \rightarrow -0

complemento de 2 = 00000 \rightarrow 0


$$\boxed{1|2} + \boxed{8|8} = \underline{\underline{100}} \leftarrow$$

$$\boxed{0|0} \text{ a } \boxed{9|9}$$

$$\boxed{1|2} + \boxed{8|7} = \boxed{9|9} \leftarrow$$

$$00001 \xrightarrow{\text{compl. 1}} 11110 \xrightarrow{+} \underline{11111} \leftarrow$$
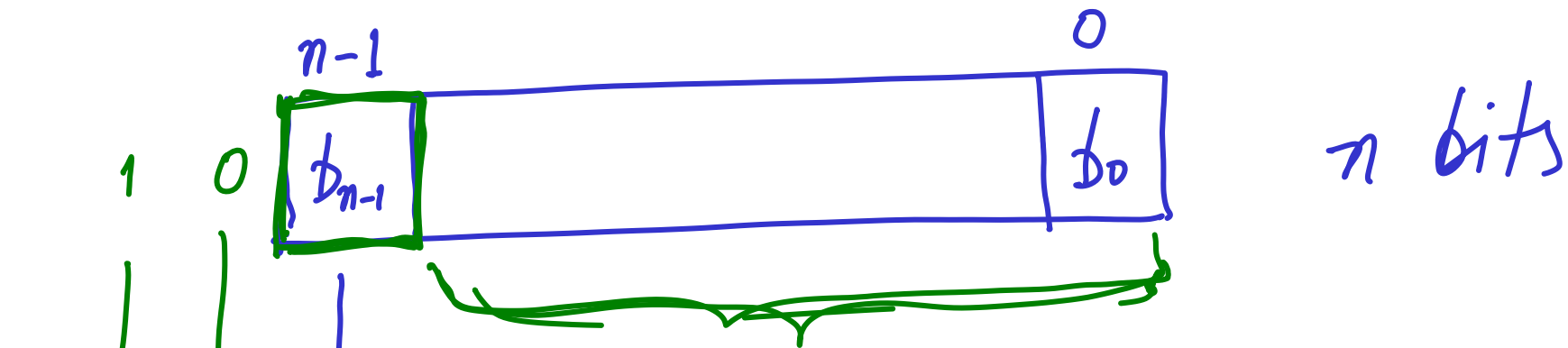
$$\underline{00001} \xrightarrow{\text{compl. 2}} \begin{array}{r} \overset{1}{7} \overset{1}{1} \overset{1}{1} \overset{1}{1} \overset{1}{1} \\ 71111 \\ + \\ \hline \end{array} \xrightarrow{+} \underline{00000} \leftarrow$$
$$\boxed{100000}$$





$$-b_{n-1} 2^{n-1} + b_{n-2} 2^{n-2} + \dots + b_0 2^0$$

$$-b_{n-1} 2^{n-1} + \sum_{i=0}^{n-2} b_i 2^i$$

↑
complemento
de 2

Operações lógicas

	x	y	E xy	OU $x+y$	$N\tilde{A}\tilde{O}$ \bar{x}
→	0	0	0	0	1
→	0	1	0	1	1
→	1	0	0	1	0
→	1	1	1	1	0

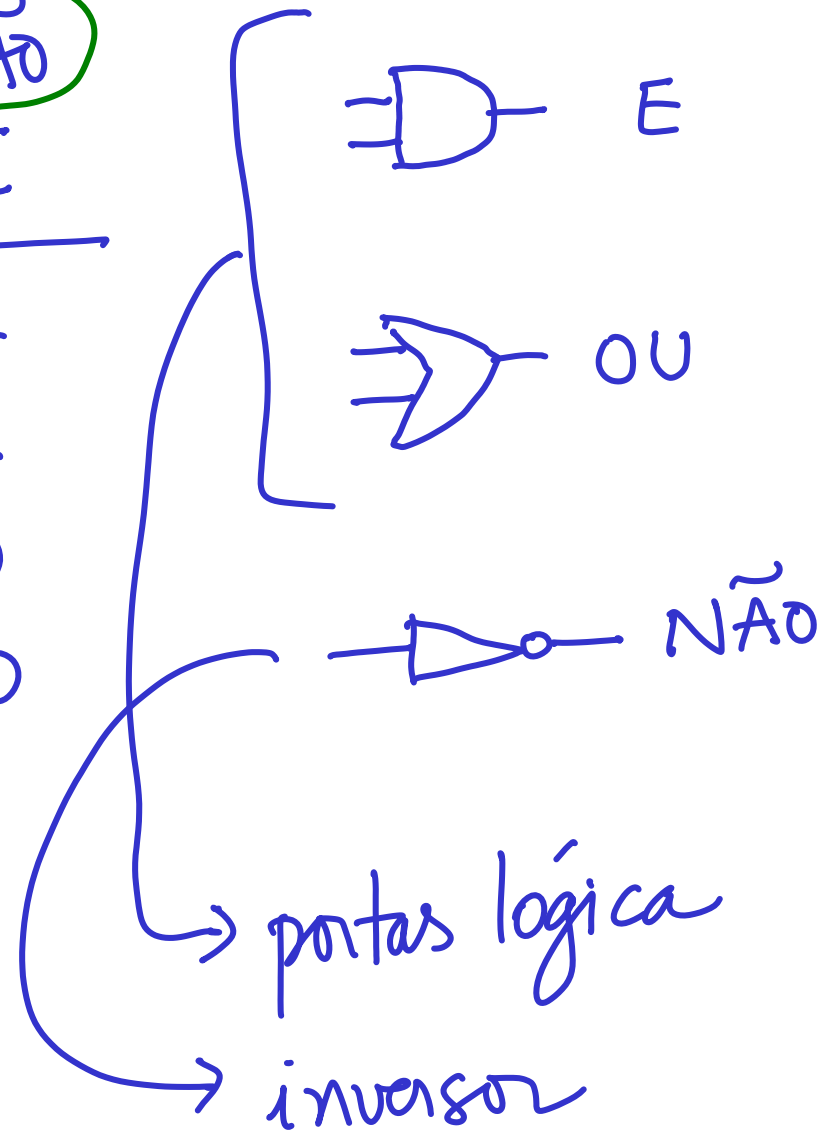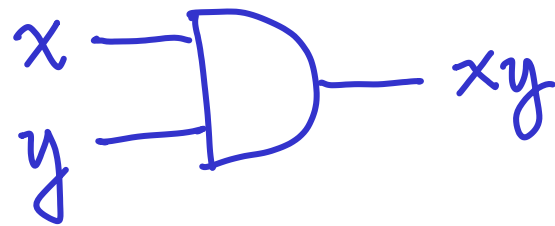

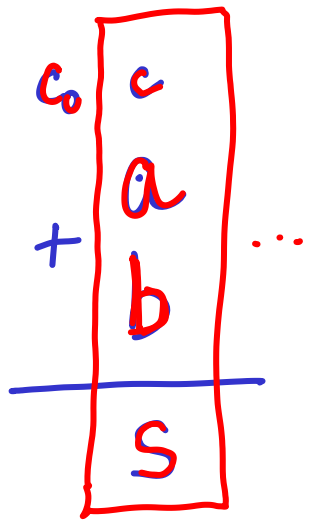


Tabela-
verdade

Funções
binária

a	b	c	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

entadas

2 saídas

a	b	c	s	Cost
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


$$s(a,b,c) = \bar{a}\bar{b}c + \bar{a}b\bar{c} + a\bar{b}\bar{c} + abc$$

0+0+0
0+0=0

$$\text{Cost}(a,b,c) = \bar{a}bc + a\bar{b}c + ab\bar{c} + abc$$

$$S(a, b, c) = \bar{a}\bar{b}c + \bar{a}b\bar{c} + a\bar{b}\bar{c} + abc$$


001
010
100
111

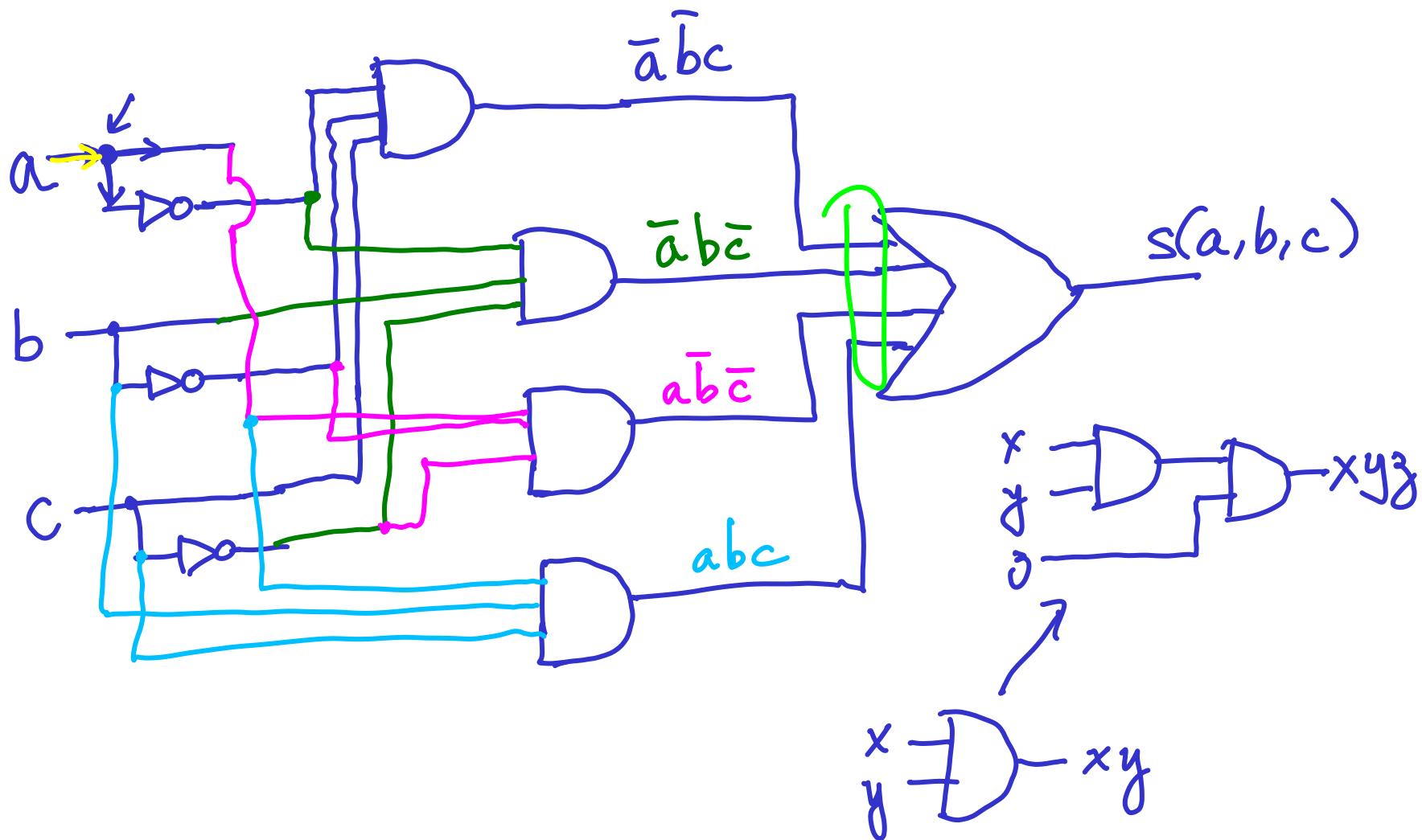

$$S(a, b, c) = \bar{a}\bar{b}c + \bar{a}b\bar{c} + a\bar{b}\bar{c} + abc$$


001
010
100
111

Expresión algebraica

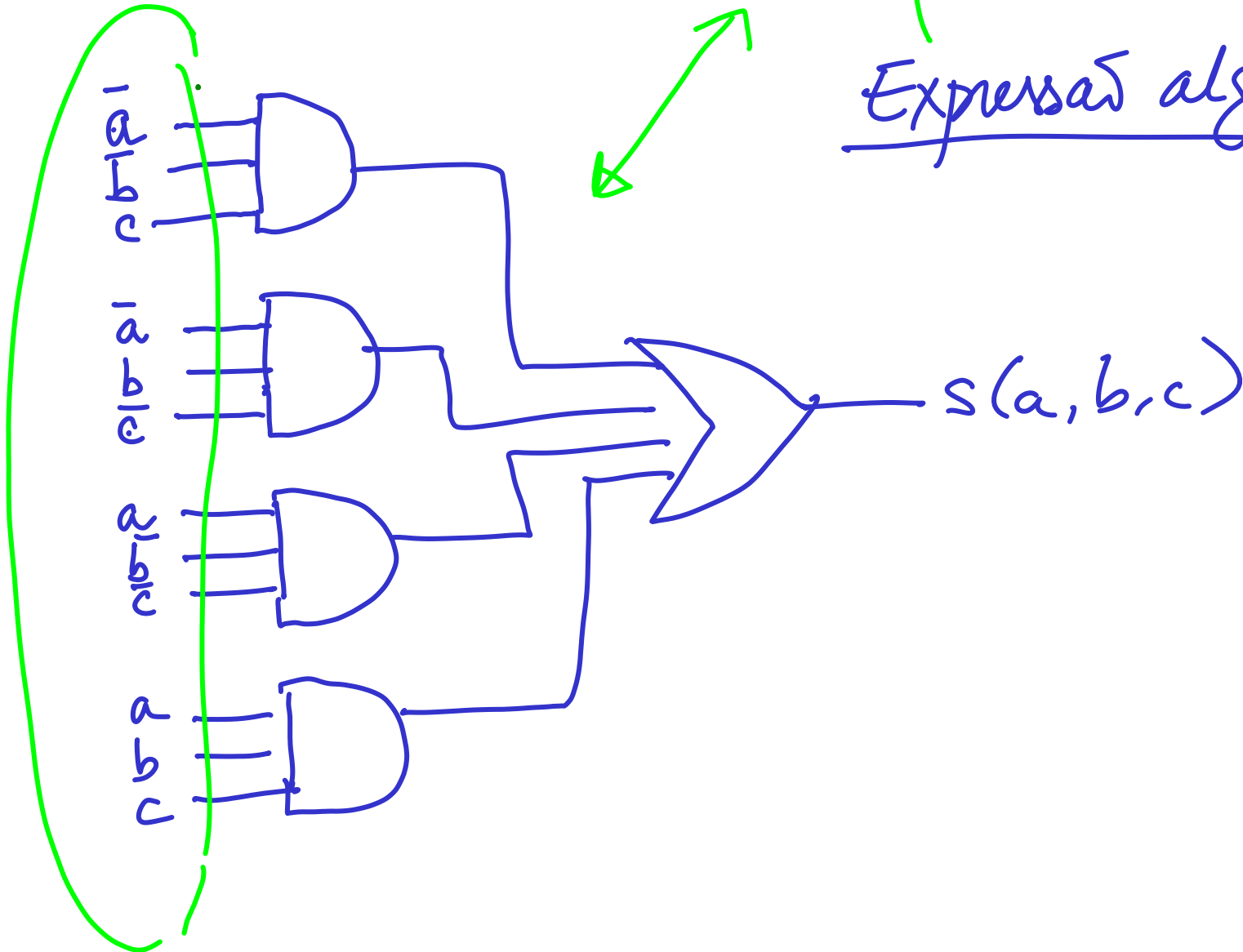

$$s(a, b, c) = \underline{\hspace{10em}}$$
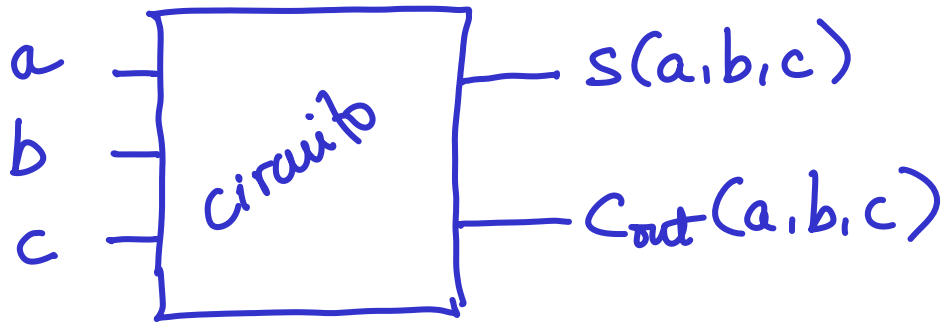
$$C_{out}(a, b, c) = \underline{\hspace{10em}}$$




módulo somador de bits.


$$n = 3 \quad A = a_2 a_1 a_0$$

$$B = b_2 b_1 b_0$$

$$S = A + B \Rightarrow \begin{array}{r} c_3 \quad c_2 \quad c_1 \quad c_0 \\ a_2 \quad a_1 \quad a_0 \\ + \quad b_2 \quad b_1 \quad b_0 \\ \hline s_2 \quad s_1 \quad s_0 \end{array}$$

$$S = s_2 s_1 s_0$$

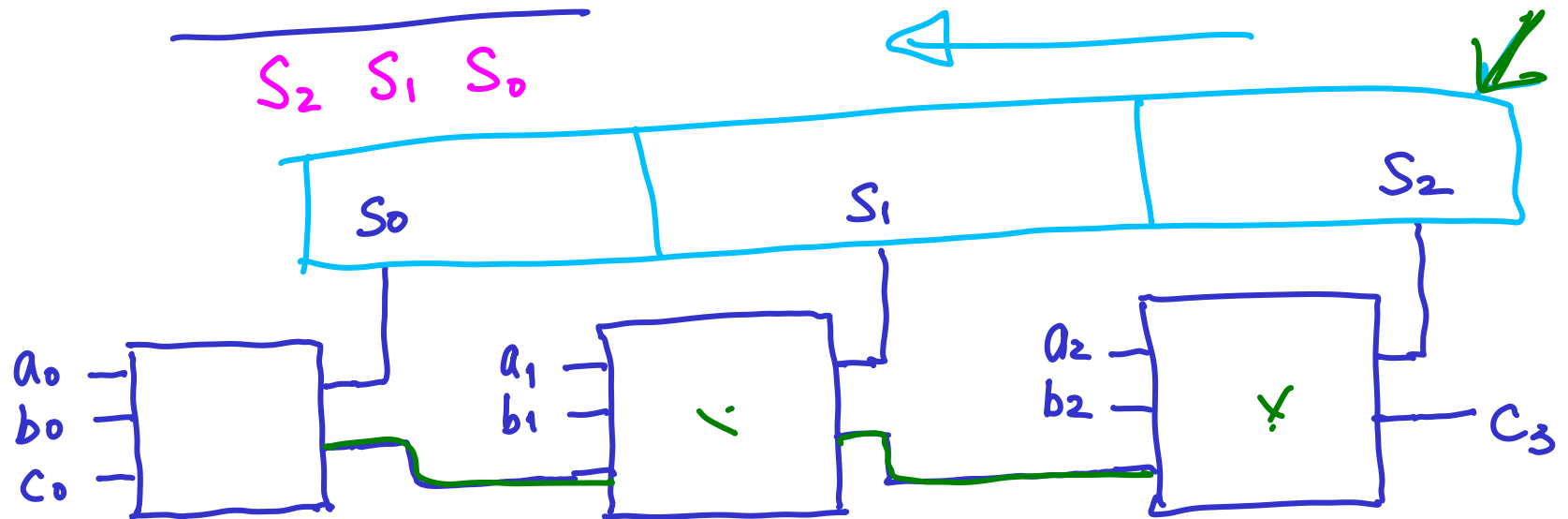

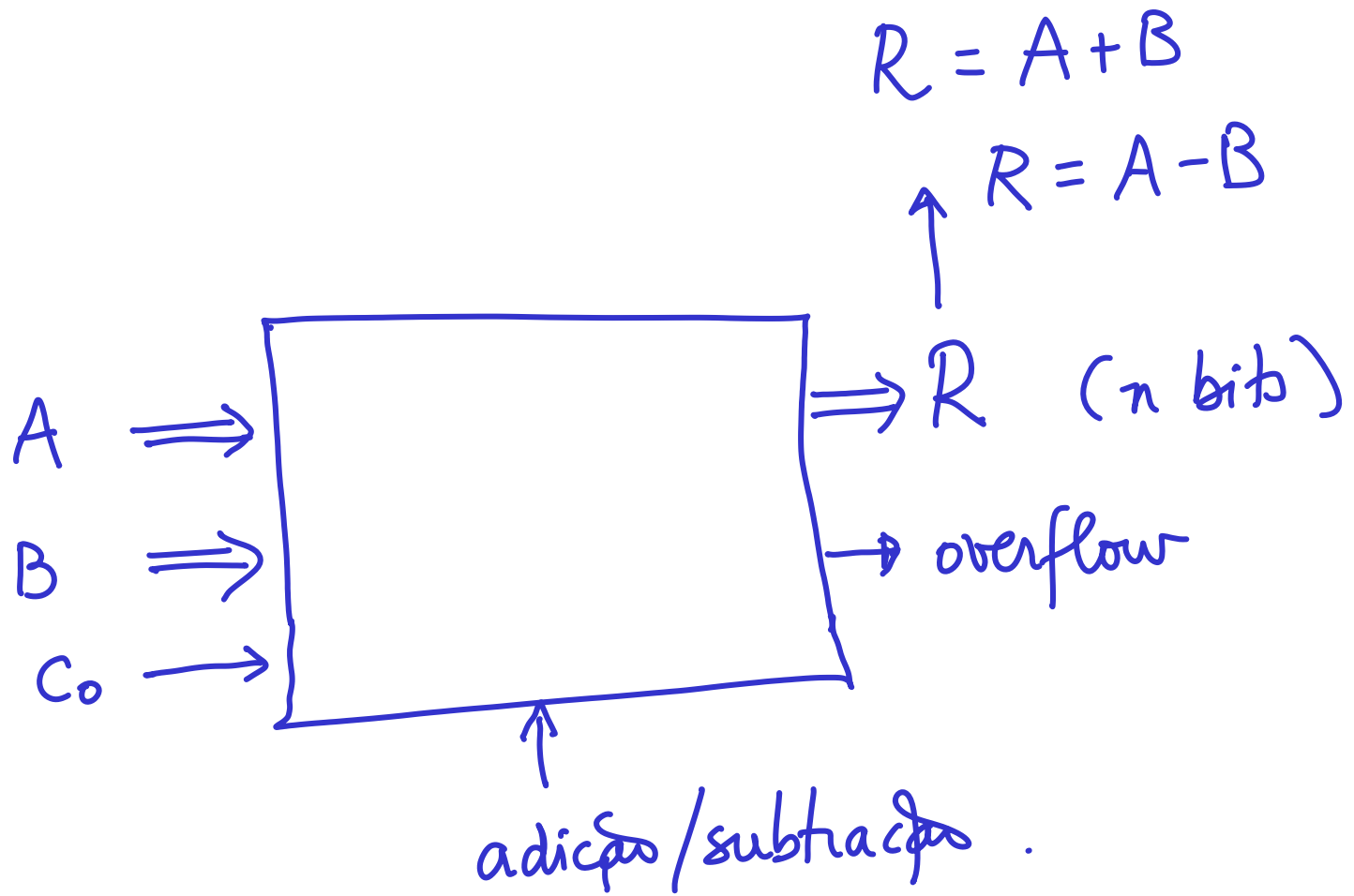

$A, B \rightarrow n$ bits

$S(a, b, c)$
 $C_{out}(a, b, c)$

Flip-flop

