

## CHECKPOINT #2

1. Consider the following filter circuit

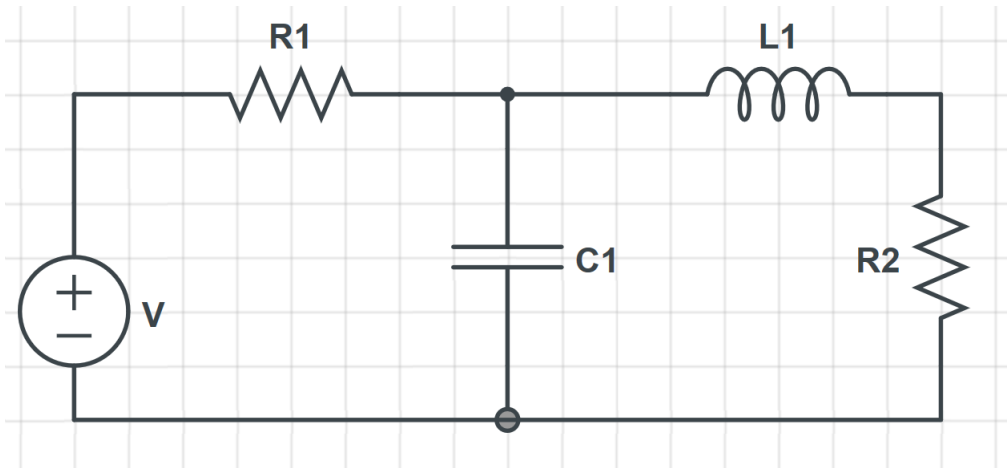


Figure 1: Filter circuit

- Apply the mesh analysis method considering the capacitor and the inductor in frequency domain (capacitor  $= 1/sC_1$  and inductor  $sL_1$ ).
- Using symbolic variables find the current solutions.
- Find the transfer function  $G = R_2 I_2(s)/V(s)$ .
- Now, assuming that:
  - $R_1 = R_2 = 1\Omega$
  - $L_1 = 1mH$
  - $C_1 = 100\mu F$ ,find:
  - The poles of transfer function;
  - The zeroes of transfer function;
  - The pole/zero map;
  - The impulse response;
  - The step response.
- Find the state space realization with evaluated transfer function.