
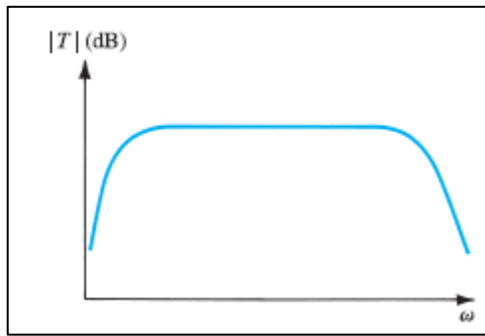


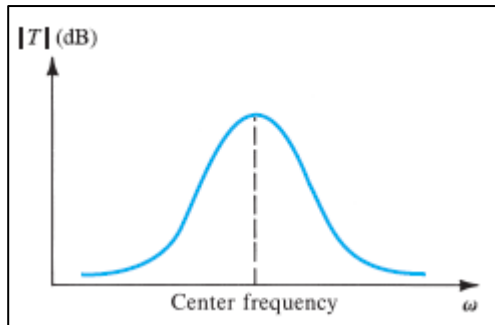**Op Amp
Imperfections
(Offset Voltage)**




Example: audio signal amplifiers.

capacitively coupled amplifiers | (ac amplifiers)




Example: amplifiers for the design of radio and TV receivers.

bandpass amplifiers

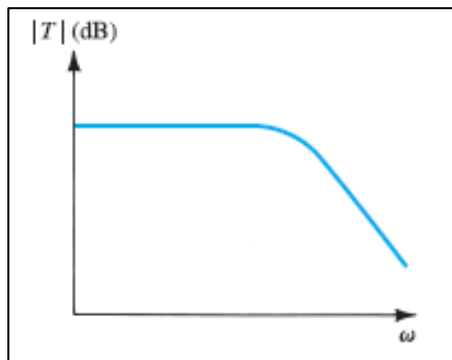

Example: IC amplifiers.

direct-coupled amplifiers | (dc amplifiers)

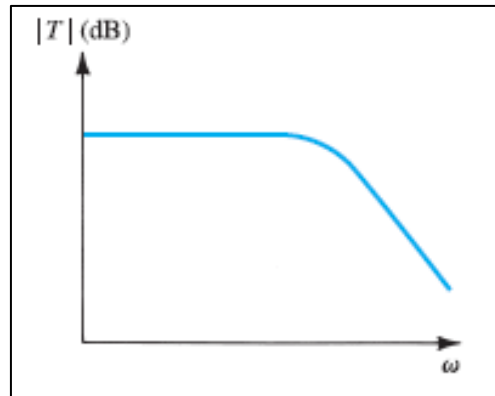

Op amp amplifiers.

direct-coupled amplifiers | (dc amplifiers)

1

Op amps are **direct-coupled devices** with large gains at dc. They are prone to dc problems. **The first such problem is the dc input offset voltage (V_{os})**.

The input offset voltage arises as a result of the unavoidable mismatches present in the input differential stage inside the op amp.

2

If the two input terminals of the op amp are tied together and connected to ground, it will be found that despite the fact that $v_{id} = 0$, a finite dc voltage exists at the output.

3

The op-amp output can be brought back to its ideal value of 0 V by connecting a dc voltage source of appropriate polarity and magnitude between the two input terminals of the op amp. This external source balances out the input offset voltage of the op amp. **It follows that the input offset voltage must be of equal magnitude and of opposite polarity to the voltage we applied externally.**


4

The value of V_{OS} depends on temperature. The op amp data sheets usually specify typical and maximum values for V_{OS} at room temperature as well as the temperature coefficient of V_{OS} (usually in $\mu\text{V}/^\circ\text{C}$). General-purpose op amps exhibit V_{OS} in the range of **1 mV to 5 mV**.

They do not, however, specify the polarity of V_{OS} because the component mismatches that give rise to V_{OS} are obviously not known a priori. **Different units of the same op-amp type may exhibit either a positive or a negative V_{OS} .**


5

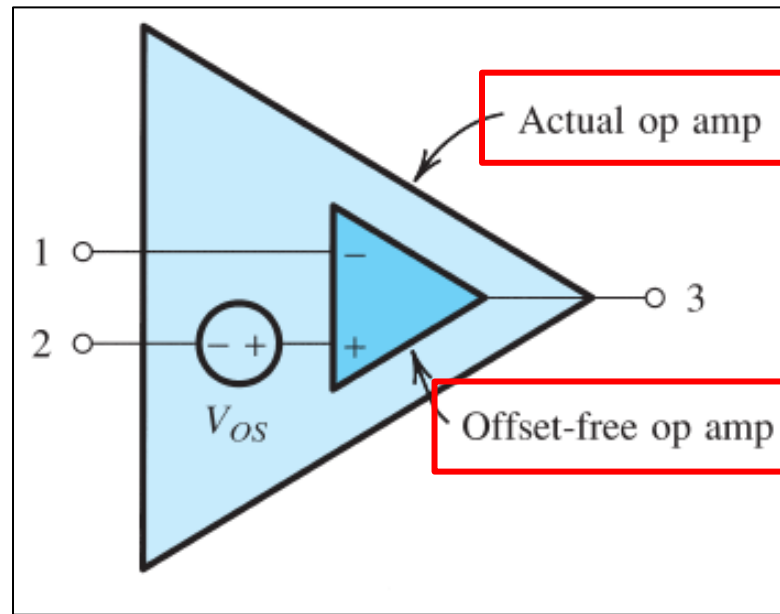To analyze the effect of V_{OS} on the operation of op-amp circuits, we need a circuit model for the op amp with input offset voltage, as shown below.




Circuit model for an op amp with an input offset voltage V_{OS}

6

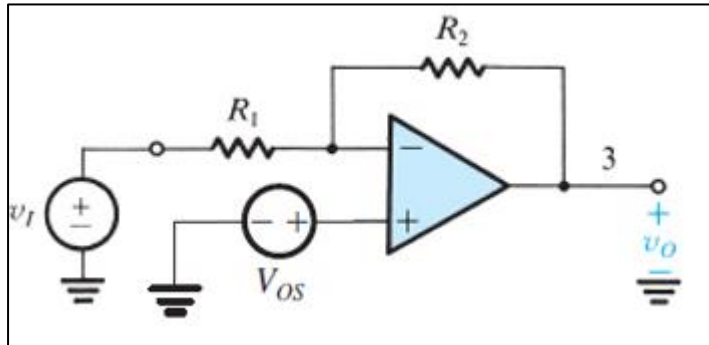


V_{OS} model for the
Inverter Amplifier

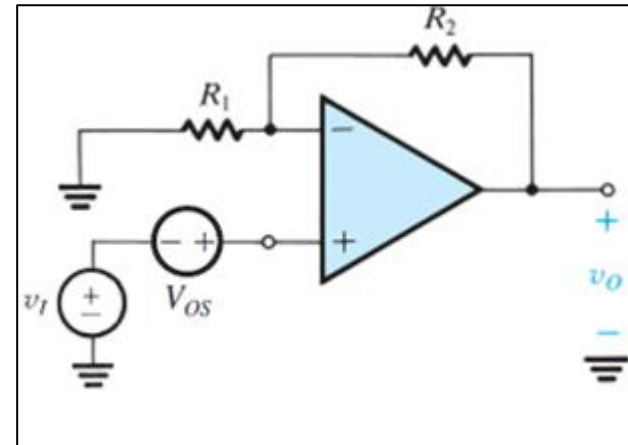


V_{OS} model for the
Noninverter Amplifier

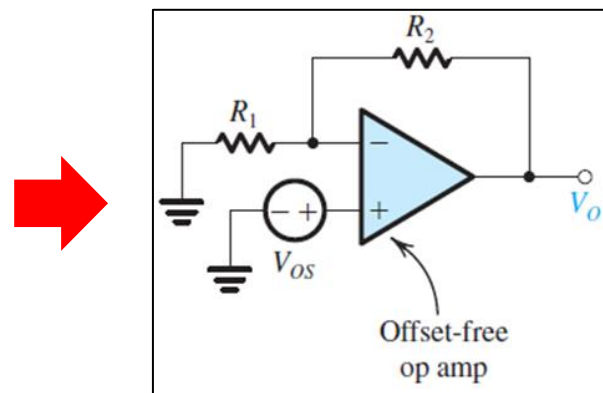In both amplifiers grounding the inputs results in a noninverter amplifier with a V_{OS} input .



$$V_O = V_{OS} \left(1 + \frac{R_2}{R_1} \right)$$

7

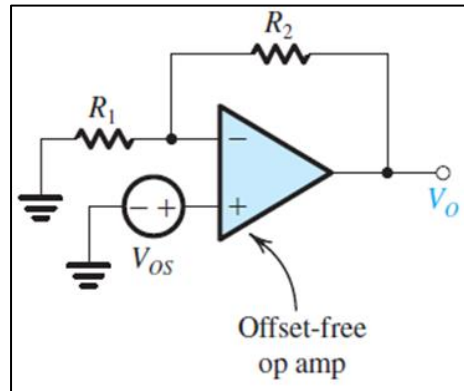

$$V_o = V_{OS} \left(1 + \frac{R_2}{R_1} \right)$$

This output dc voltage can have a large magnitude.


For instance, a noninverting amplifier with a closed-loop gain of 1000, when constructed from an op amp with a 5-mV input offset voltage, will have a dc output voltage of +5 V or -5 V (depending on the polarity of V_{OS}) rather than the ideal value of 0 V.

Now, when an input signal is applied to the amplifier, the corresponding signal output will be superimposed on the 5V dc.

Even worse, if the signal to be amplified is dc, we would not know whether the output is due to V_{OS} or to the signal !

8

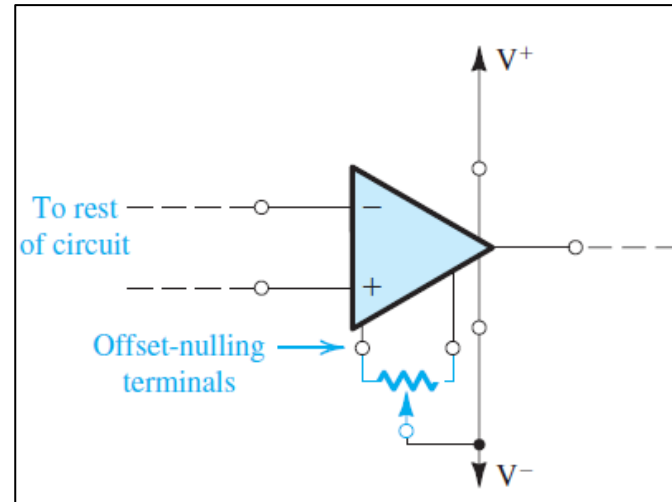Some op amps are provided with two additional terminals to which a specified circuit can be connected to trim to zero the output dc voltage due to V_{OS} . The circuit below shows such an arrangement that is typically used with general-purpose op amps.





A potentiometer is connected between the offset-nulling terminals with the wiper of the potentiometer connected to the op-amp negative supply. Moving the potentiometer wiper introduces an imbalance that counteracts the asymmetry present in the internal op-amp circuitry and that gives rise to V_{OS} .

It should be noted, however, that even though the dc output offset can be trimmed to zero, the problem remains of the variation (or drift) of V_{OS} with temperature !


Op Amp 741

Offset Nulling Terminals

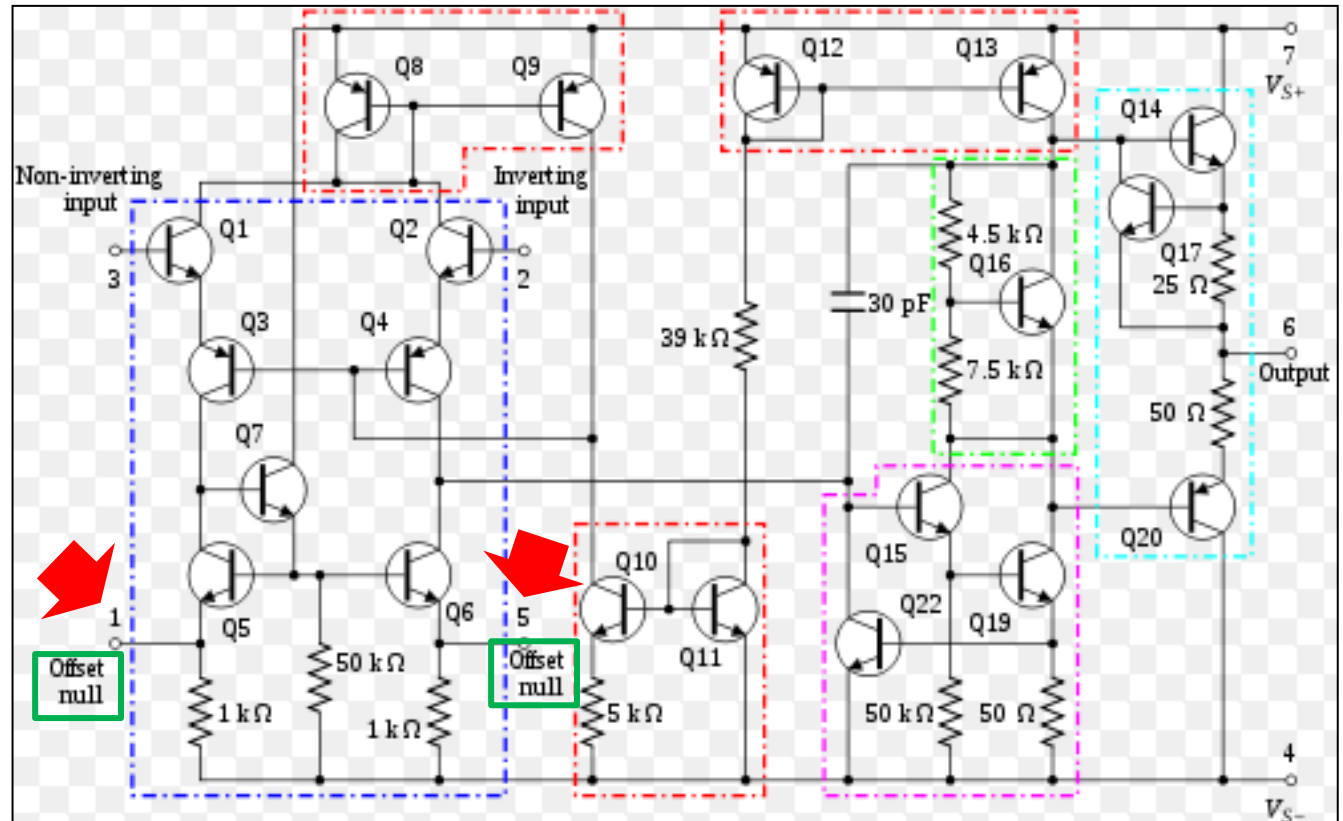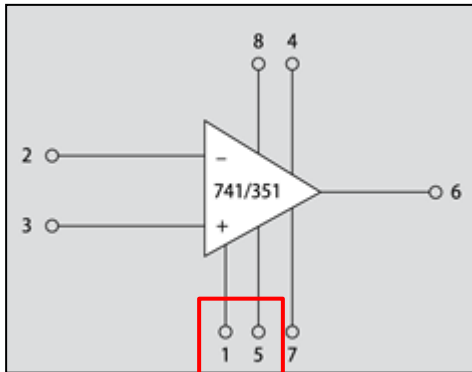

9

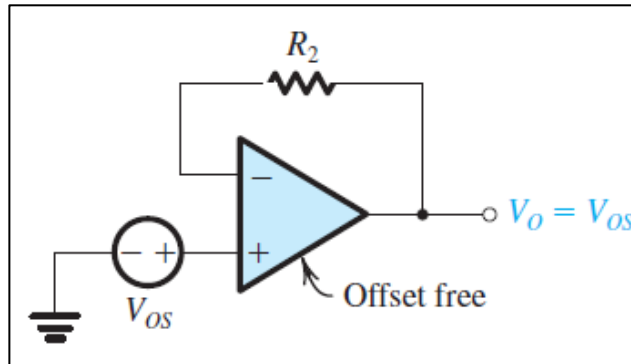
As a result, the equivalent circuit for determining the dc output voltage resulting from the op-amp input offset voltage V_{OS} will be:



$$V_o = V_{OS} \left(1 + \frac{R_2}{R_1} \right)$$

$$R_1 = \infty$$


$$V_o = V_{OS}$$

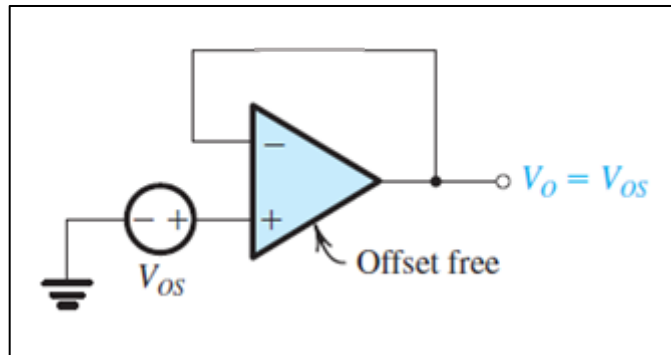

$$V_o = V_{OS}$$

Thus, V_{OS} sees in effect a unity-gain voltage follower, and the dc output voltage V_O will be equal to V_{OS} rather than $V_{OS} (1 + R_2/R_1)$. The R_2 resistance can be replaced by a short circuit.

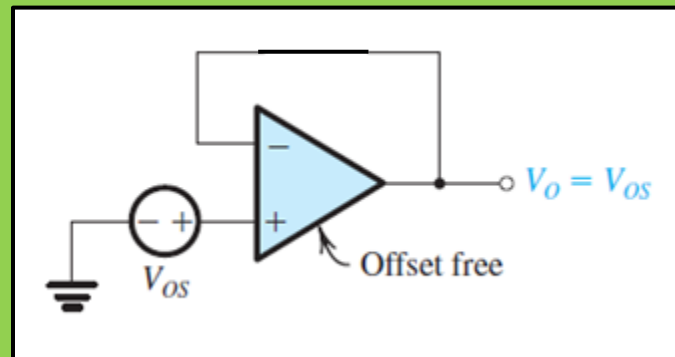Measurement of the Offset Voltage in the LTSPice





$$V_o = V_{os}$$

Input Offset Voltage – Op Amp LF351

The data sheet of the op amp LF351 shows de following information:

"Input Offset Voltage" (V_{OS} ou V_{IO})	5 mV
Corrente de polarização da entrada ($I_B = \frac{I_p + I_n}{2}$)	50 pA
Offset de corrente da entrada (I_{OS} ou $I_{IO} = I_p - I_n$)	25 pA
Ganho de tensão em malha aberta (A_{VOL})	100 V/mV (100 dB)
"Slew rate" (SR)	13 V/ μ s
Frequência de Transição (f_T)	4 MHz

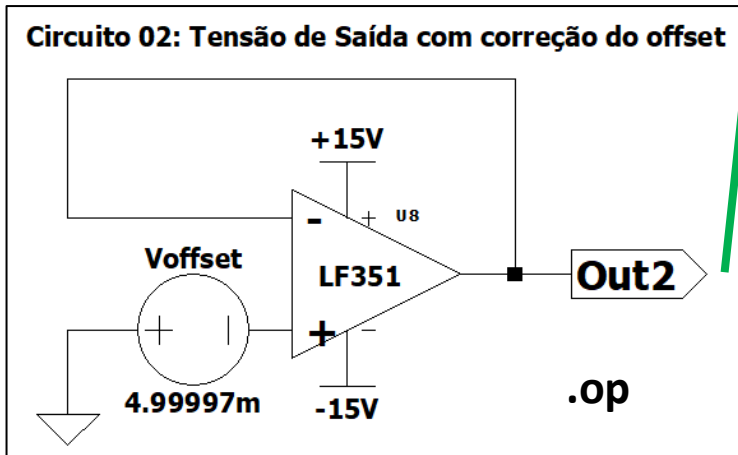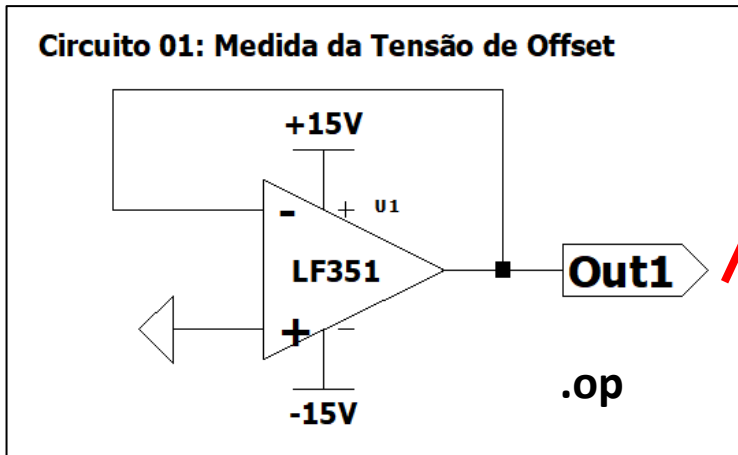
The “Input Offset Voltage” can be measured in simulation using a voltage follower circuit with the input grounded, as shown in the figure below. As expected, the output is very close to zero when a DC source with a voltage equal the measured voltage is used in the inverter input.




--- Operating Point ---

V(out1):	0.00499997	voltage
V(n001):	15	voltage
V(n002):	-15	voltage
V(out2):	5.00007e-009	voltage
V(n004):	-0.00499997	voltage
V(n003):	15	voltage
V(n005):	-15	voltage
I(Voffset):	3.89975e-011	device_current
Ix(u1:1):	3.90025e-011	subckt_current
Ix(u1:2):	8.90074e-011	subckt_current
Ix(u1:99):	0.0021	subckt_current
Ix(u1:50):	-0.0021	subckt_current
Ix(u1:28):	-8.90074e-011	subckt_current
Ix(u3:1):	-0.0021	subckt_current
Ix(u5:1):	0.0021	subckt_current
Ix(u8:1):	3.89975e-011	subckt_current
Ix(u8:2):	8.90025e-011	subckt_current
Ix(u8:99):	0.0021	subckt_current
Ix(u8:50):	-0.0021	subckt_current
Ix(u8:28):	-8.90025e-011	subckt_current
Ix(u10:1):	-0.0021	subckt_current
Ix(u12:1):	0.0021	subckt_current

Circuit 1: Measurement of the Offset Voltage

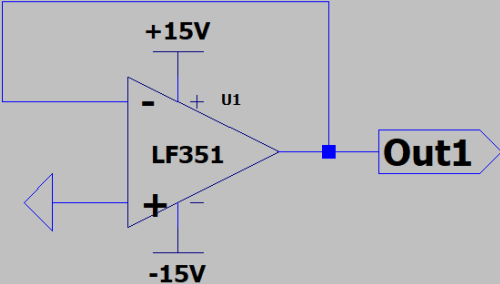

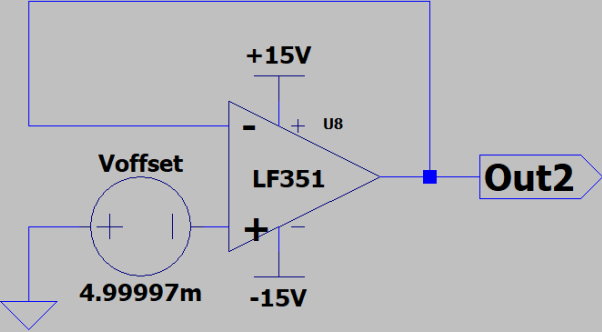Circuit 2: Output with the Offset Voltage Correction




.op

It's important to mention that **many op amps don't have their performance affected by the offset voltage** if it has a very low value (LM741, LM318, TL081, ...) !

Influence of the Input Offset Voltage in the **Open Loop Gain**


Open Loop Gain

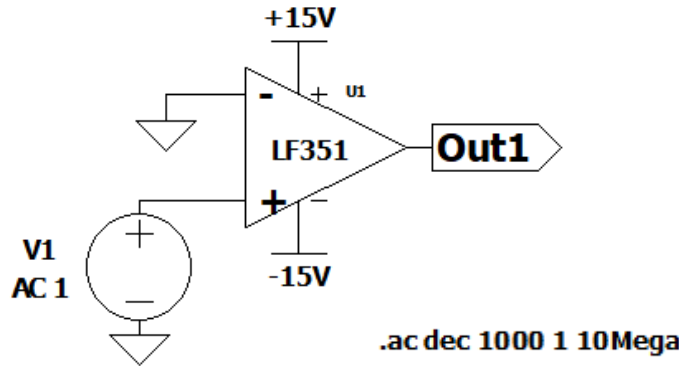Circuito 1: Ganho de Tensão em Malha Aberta sem correção do offset




Wrong Result !

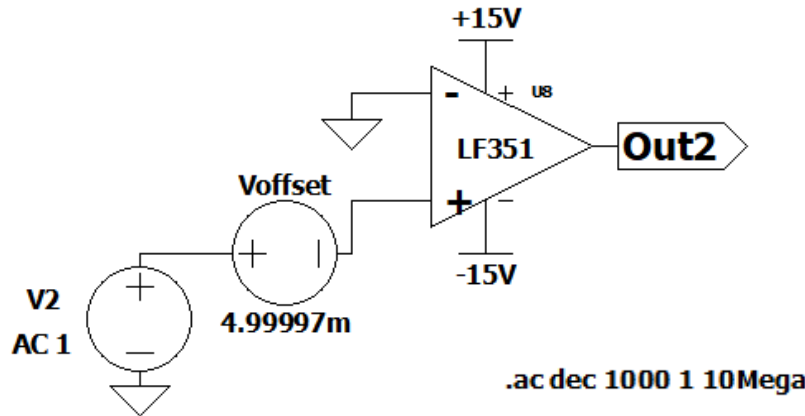Circuito 2: Ganho de Tensão em Malha Aberta com correção do offset




Right Result !


Circuit 1: Open-Loop Gain without the offset voltage correction

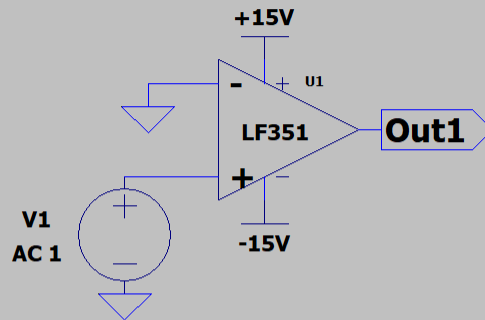

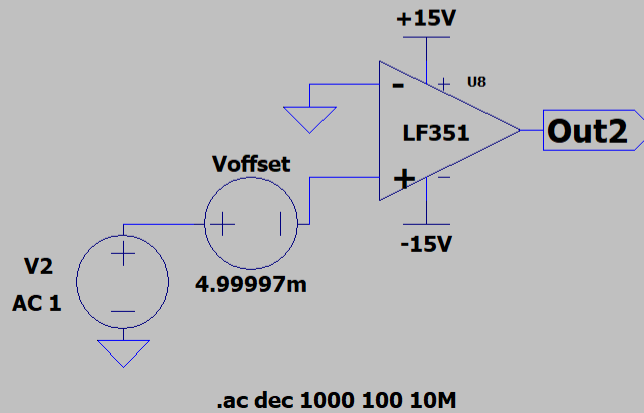
Circuit 2: Open-Loop Gain with the offset voltage correction



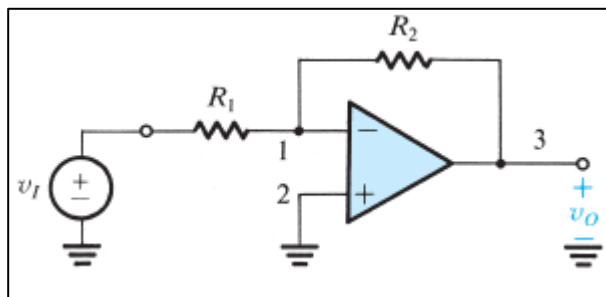**Influence of the Input Offset
Voltage in the Closed Loop Gain**




$$G = -\frac{R_2}{R_1}$$

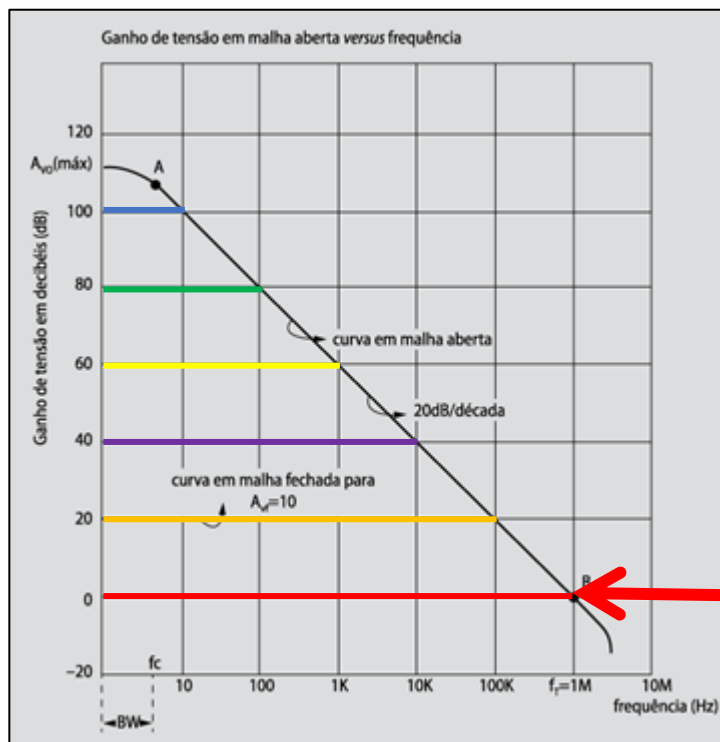

Frequency Transition (f_T)


Closed Loop Gain

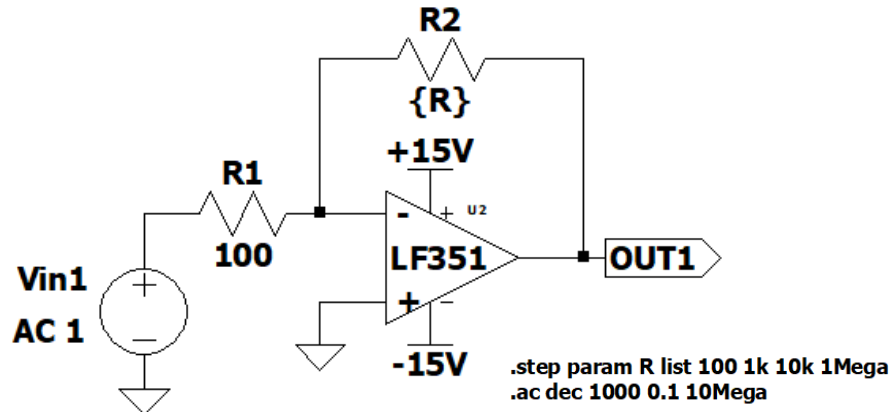Circuit 1: Closed gain without the offset voltage correction




Wrong Result !

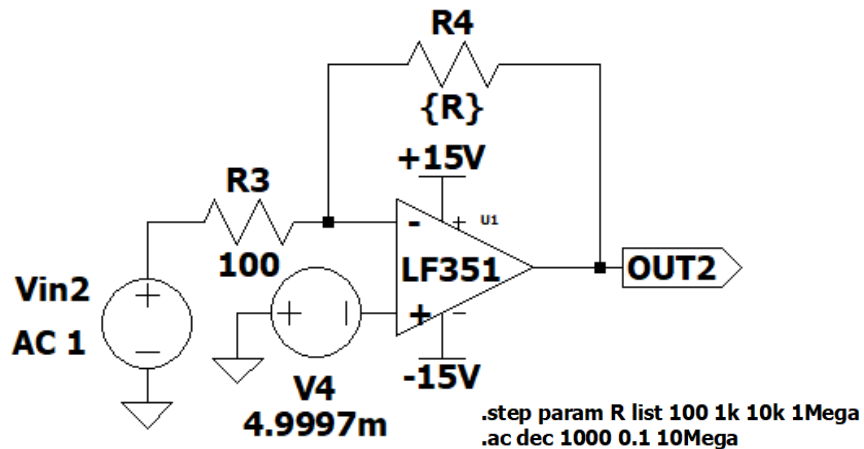
Circuit 2: Closed gain with the offset voltage correction




Right Result !

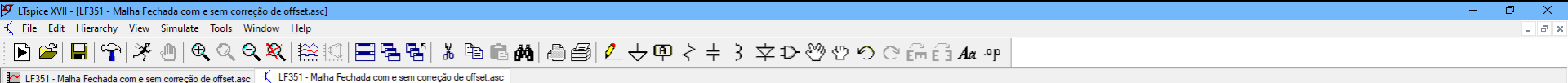

Circuit 1: Closed gain without the offset voltage correction

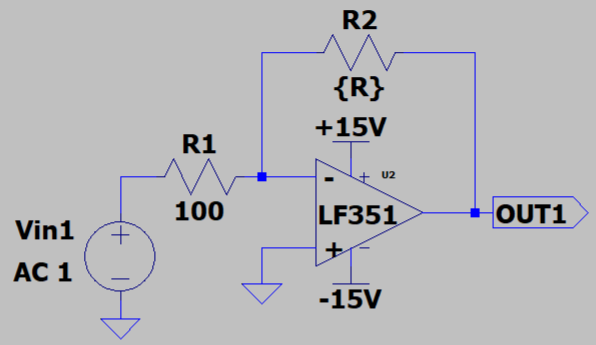

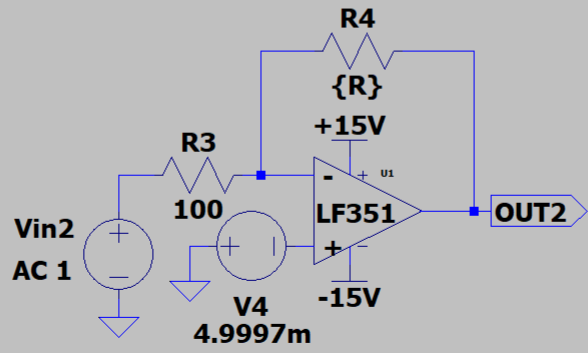Circuit 2: Closed gain with the offset voltage correction



```
.step param R list 100 1k 10k 1Mega  
.ac dec 1000 0.1 10Mega
```

It's important to mention that **many op amps don't have their performance affected by the offset voltage** if it has a very low value (LM741, LM318, TL081, ...) !