

# **Laboratório 3**

## **Filtros Ativos Passa-Banda**

# Roteiro Experimental

SEL393 – Laboratório de Instrumentação Eletrônica I  
 Escola de Engenharia de São Carlos - USP  
 Departamento de Engenharia Elétrica e de Computação  
 Laboratório 3 - Filtro Ativo Passa Banda

**1. Implementação em Protoboard**

- Implemente um filtro passa-banda de ordem 4 de Butterworth com topologia de realimentação múltipla (figura 1.1), frequência central de 10KHz,  $Q=10$  e  $A_m=1$ . Utilize  $C=10nF$ .

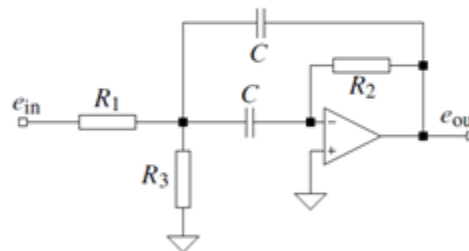


Fig. 1.1 – Topologia de realimentação múltipla de cada filtro de ordem 2 de um filtro passa-banda de ordem 4

- Determine a frequência intermediária  $f_m$ , o fator de qualidade  $Q$  e o ganho na frequência intermediária  $A_m$  de cada filtro de ordem 2.
- Determine a frequência intermediária  $f_m$ , o fator de qualidade  $Q$  e o ganho na frequência intermediária  $A_m$  do filtro de ordem 4.

## 2. Simulação no LTSpice

Simule o circuito da Fig. 1.1.

- a) Determine a frequência intermediária  $f_m$ , o fator de qualidade  $Q$  e o ganho na frequência intermediária  $A_m$  de cada filtro de ordem 2 e compare com os valores teóricos, conforme equações abaixo.

### Parâmetros do Filtro Passa Banda:

$$\text{mid-frequency: } f_m = \frac{1}{2\pi C} \sqrt{\frac{R_1 + R_3}{R_1 R_2 R_3}} \quad \text{filter quality: } Q = \pi f_m R_2 C$$

$$\text{gain at } f_m: \quad -A_m = \frac{R_2}{2R_1} \quad \text{bandwidth: } B = \frac{1}{\pi R_2 C}$$


- b) Determine a frequência intermediária  $f_m$ , o fator de qualidade  $Q$  e o ganho na frequência intermediária  $A_m$  do filtro de ordem 4.
- c) Verifique a influência de diferentes amplificadores operacionais na resposta do filtro utilizando na simulação o 741, o TL1022 e o LT081.]

## 3. Referências Bibliográficas


Carter B, Mancini R. Op Amps for Everyone, In: Active Filter Design Techniques, Chapter 16, ~~Newnes~~, 2009.

## Referência Bibliográfica


[OP AMPS for Everyone](#)  
Newnes, 2009

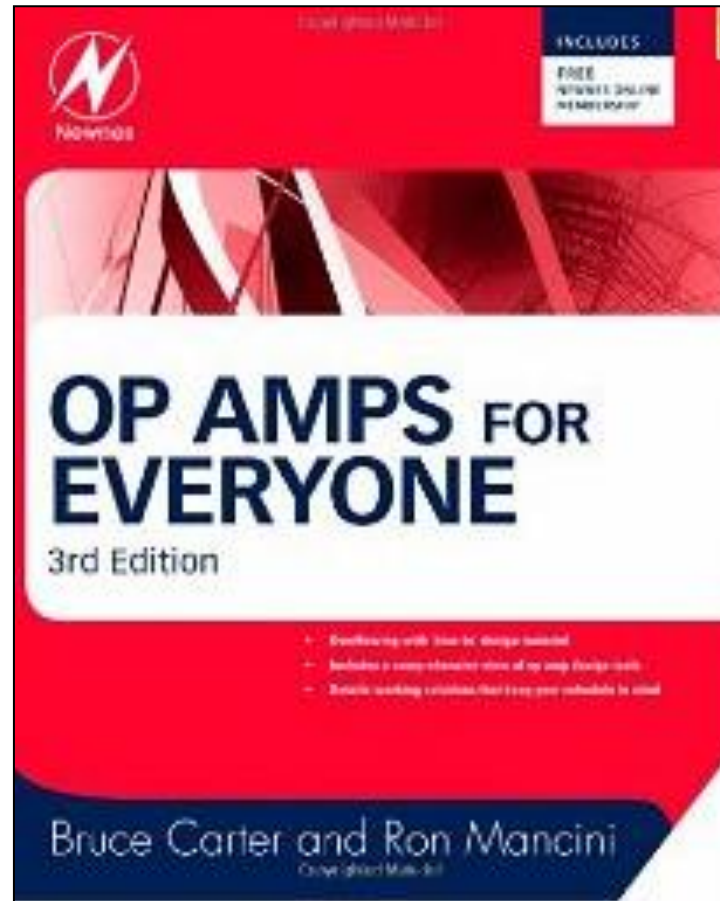

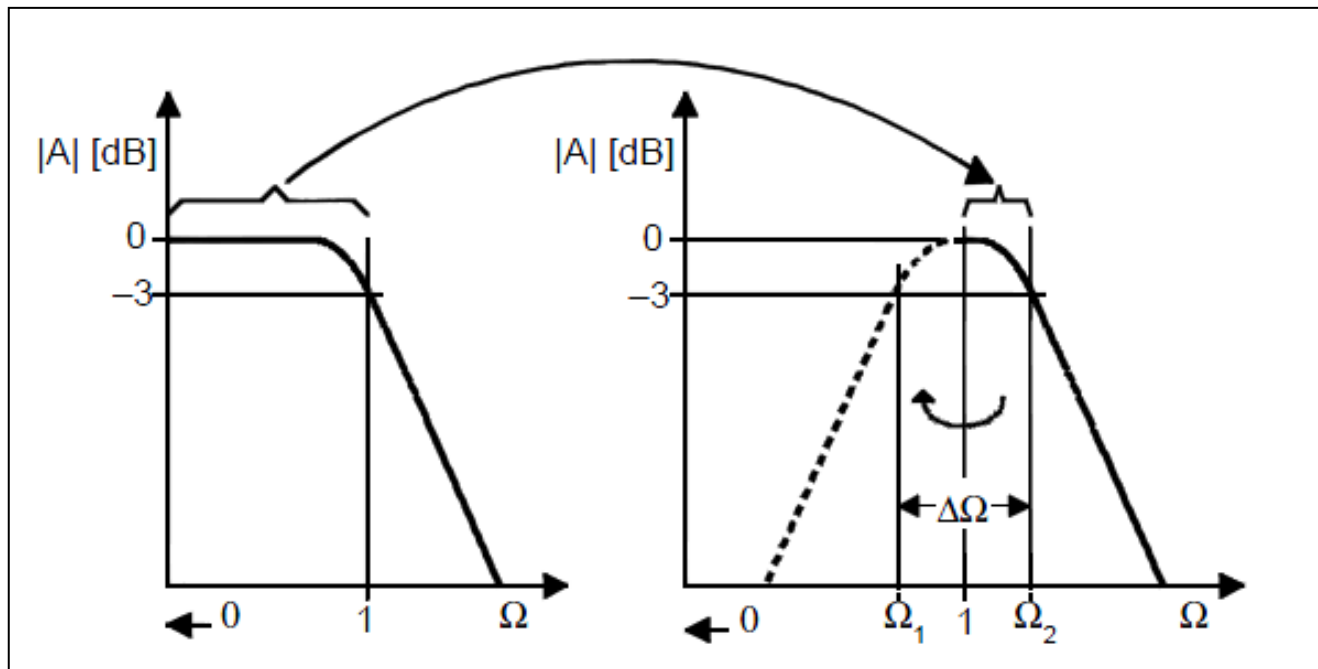- 1 The passband characteristic of a low-pass filter is transformed into the upper passband half of a band-pass filter. The upper passband is then mirrored at the mid frequency,  $f_m$  ( $\Omega=1$ ), into the lower passband half



2

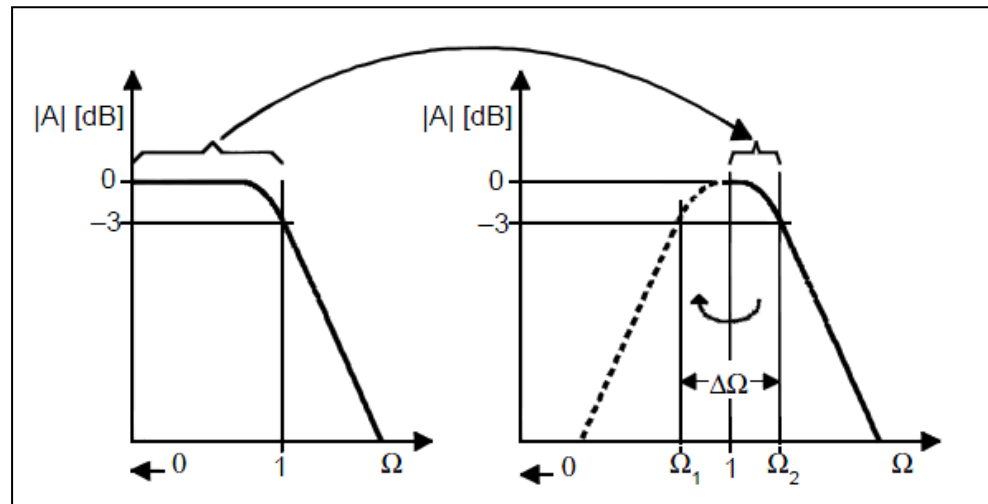

Normalized bandwidth



$$\Delta\Omega = \Omega_2 - \Omega_1$$

Normalized mid bandwidth



$$\Omega_m = 1 = \Omega_2 \cdot \Omega_1$$

Q factor



$$Q = \frac{f_m}{B} = \frac{f_m}{f_2 - f_1} = \frac{1}{\Omega_2 - \Omega_1} = \frac{1}{\Delta\Omega}$$

- 3 **The simplest design of a band-pass filter is the connection of a high-pass filter and a lowpass filter in series**, which is commonly done in wide-band filter applications.
- 4 A first order high-pass and a first-order low-pass provide a second-order band-pass.
- 5 A second-order high-pass and a second-order low-pass result in a fourth-order band-pass response.
- 6 Narrow-band filters of higher order consist of cascaded second-order band-pass filters that use the Sallen-Key or the Multiple Feedback (MFB) topology.



7

To develop the frequency response of a **second-order band-pass filter**, apply the

Transformation  $s \rightarrow \frac{1}{\Delta\Omega} \left( s + \frac{1}{s} \right)$  to a **first-order low-pass transfer function**:

$$s \rightarrow \frac{1}{\Delta\Omega} \left( s + \frac{1}{s} \right)$$



$$A(s) = \frac{A_0}{1 + s}$$



$$A(s) = \frac{A_0 \cdot \Delta\Omega \cdot s}{1 + \Delta\Omega \cdot s + s^2}$$

8

When designing band-pass filters, **the parameters of interest are the gain at the mid frequency ( $A_m$ ) and the quality factor ( $Q$ )**, which represents the selectivity of a band-pass filter.


$$Q = \frac{f_m}{B} = \frac{f_m}{f_2 - f_1} = \frac{1}{\Omega_2 - \Omega_1} = \frac{1}{\Delta\Omega}$$

Therefore, replace  $A_0\Delta\Omega$  with  $A_m/Q$  and  $\Delta\Omega$  with  $1/Q$  (Equation 16–7) to obtain:

$$A(s) = \frac{A_0 \cdot \Delta\Omega \cdot s}{1 + \Delta\Omega \cdot s + s^2}$$


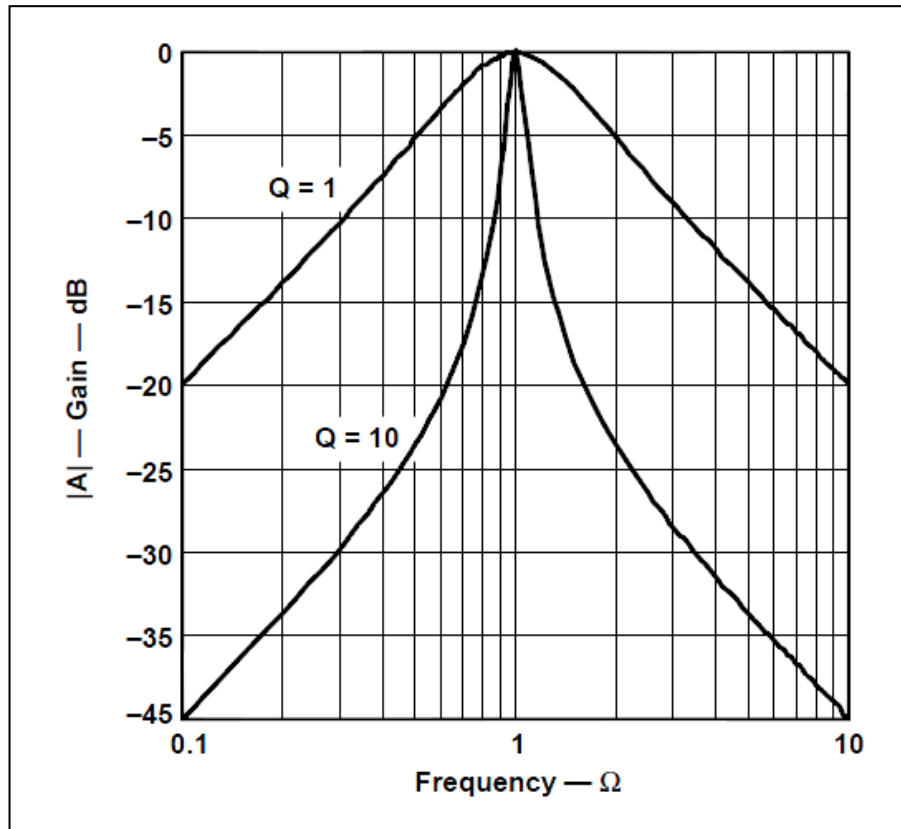
$$A(s) = \frac{\frac{A_m}{Q} \cdot s}{1 + \frac{1}{Q} \cdot s + s^2}$$




$$Q = \frac{f_m}{B} = \frac{f_m}{f_2 - f_1} = \frac{1}{\Omega_2 - \Omega_1} = \frac{1}{\Delta\Omega}$$

**Normalized gain response of a second order bandpass filter**


# **Band Pass Filters**

## **Second Order Topology**


## Sallen-Key Topology

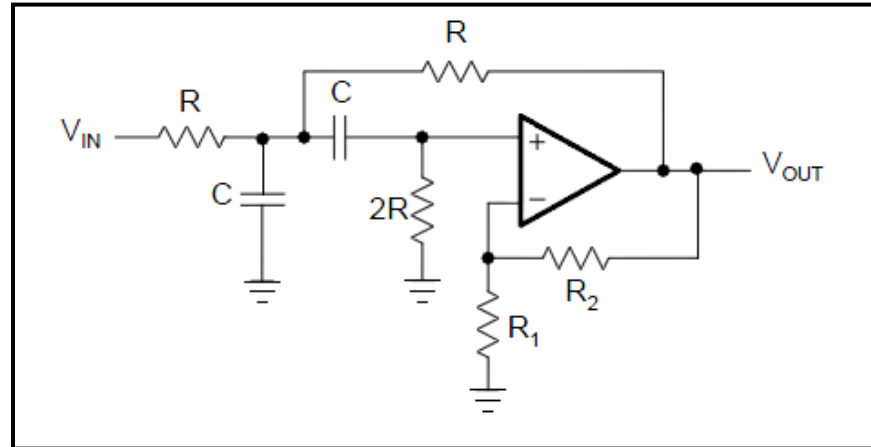

## Multiple Feedback Topology

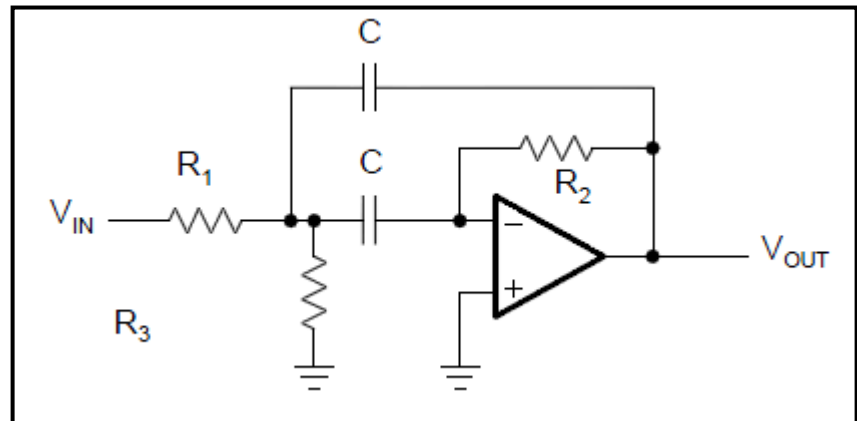

# Sallen-Key Topology

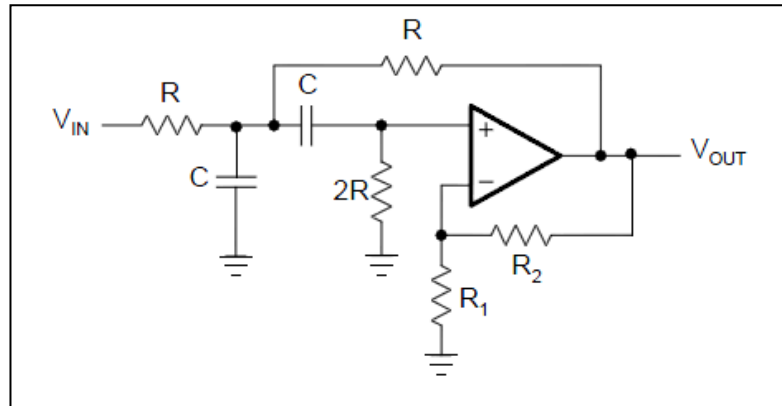

$$A(s) = \frac{\frac{A_m}{Q} \cdot s}{1 + \frac{1}{Q} \cdot s + s^2}$$




$$A(s) = \frac{G \cdot RC\omega_m \cdot s}{1 + RC\omega_m(3 - G) \cdot s + R^2C^2\omega_m^2 \cdot s^2}$$

$$G = 1 + R_2 / R_1$$

filter quality:  $Q = \frac{1}{3 - G}$

mid-frequency:  $f_m = \frac{1}{2\pi RC}$

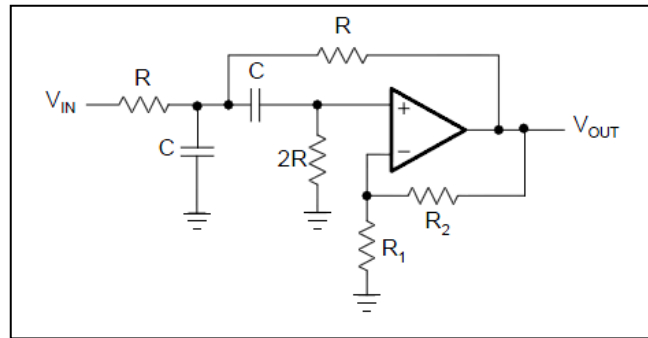gain at  $f_m$ :  $A_m = \frac{G}{3 - G}$



- 1 The Sallen-Key circuit has the advantage that the quality factor ( $Q$ ) can be varied via the inner gain ( $G$ ) without modifying the mid frequency ( $f_m$ ).


$$\text{filter quality: } Q = \frac{1}{3 - G} \quad \text{mid-frequency: } f_m = \frac{1}{2\pi RC}$$

- 2 A drawback is that  $Q$  and  $A_m$  cannot be adjusted independently.

$$\text{filter quality: } Q = \frac{1}{3 - G} \quad \text{gain at } f_m: \quad A_m = \frac{G}{3 - G}$$

- 3 Care must be taken when  $G$  approaches the value of 3 because  $A_m$  becomes infinite.

# Multiple Feedback Topology

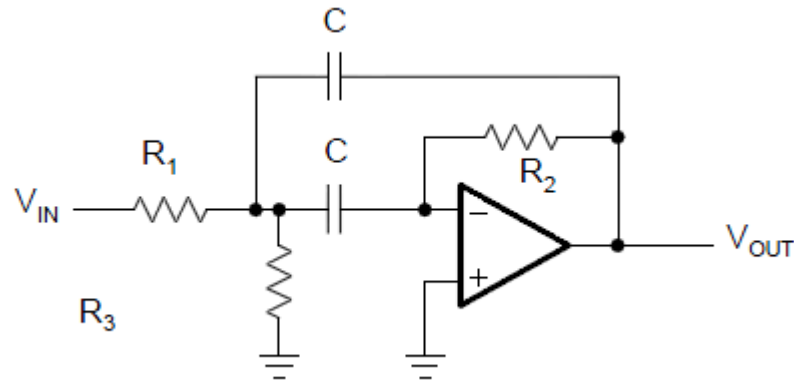

$$A(s) = \frac{\frac{A_m}{Q} \cdot s}{1 + \frac{1}{Q} \cdot s + s^2}$$



$$A(s) = \frac{-\frac{R_2 R_3}{R_1 + R_3} C \omega_m \cdot s}{1 + \frac{2R_1 R_3}{R_1 + R_3} C \omega_m \cdot s + \frac{R_1 R_2 R_3}{R_1 + R_3} C^2 \cdot \omega_m^2 \cdot s^2}$$

mid-frequency:  $f_m = \frac{1}{2\pi C} \sqrt{\frac{R_1 + R_3}{R_1 R_2 R_3}}$

filter quality:  $Q = \pi f_m R_2 C$


gain at  $f_m$ :  $-A_m = \frac{R_2}{2R_1}$

bandwidth:  $B = \frac{1}{\pi R_2 C}$



# Designing a Band Pass Filters Second Order Topology

# Sallen-Key Topology

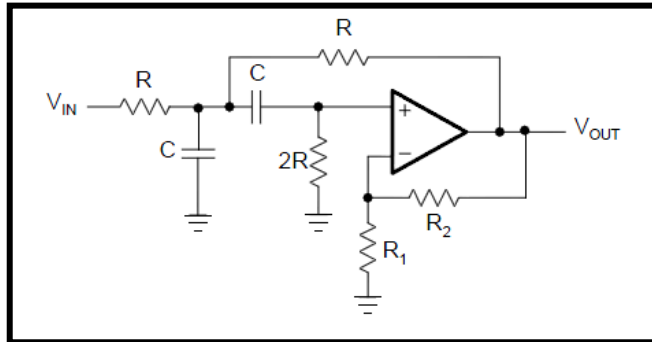

**1** Specify  $f_m$  and  $C$

**2** 
$$R = \frac{1}{2\pi f_m C}$$

**3a** Specify  $A_m$ , calculate  $G$  and  $R_2 / R_1$

$$R_2 = \frac{2A_m - 1}{1 + A_m}$$

$$A_m = \frac{G}{3 - G}$$

$$G = 1 + R_2 / R_1$$


**3b** Specify  $Q$ , calculate  $G$  and  $R_2 / R_1$

$$R_2 = \frac{2Q - 1}{Q}$$

$$Q = \frac{1}{3 - G}$$

$$G = 1 + R_2 / R_1$$

# Multiple Feedback Topology

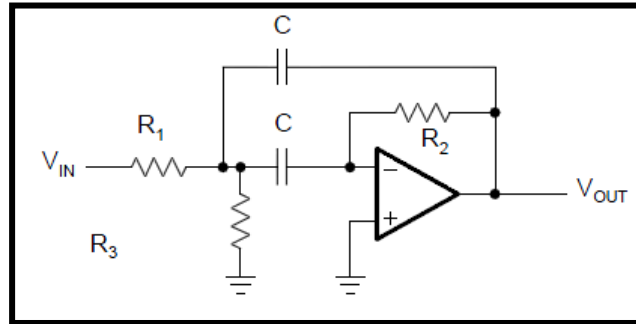

1 Specify  $f_m$ ,  $Q$ ,  $A_m$  and  $C$

2

$$R_2 = \frac{Q}{\pi f_m C}$$

3


$$R_1 = \left| \frac{R_2}{-2A_m} \right|$$

4

$$R_3 = \left| \frac{-A_m R_1}{Q^2 + A_m} \right|$$
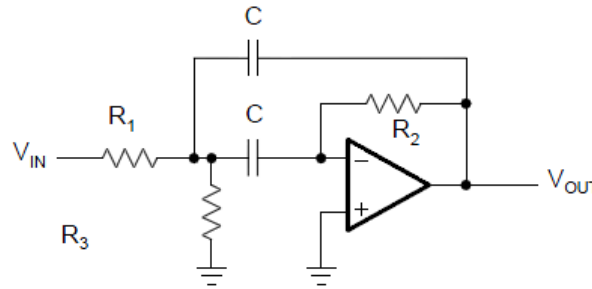
### Example 1:

Design a second-order MFB band-pass filter with a mid frequency of  $f_m = 1$  kHz, a quality factor of  $Q = 10$ , and a gain of  $A_m = -2$ . Assume a capacitor value of  $C = 100$  nF.



$$R_2 = \frac{Q}{\pi f_m C} = \frac{10}{\pi \cdot 1 \text{ kHz} \cdot 100 \text{ nF}} = 31.8 \text{ k}\Omega$$

$$R_1 = \left| \frac{R_2}{-2A_m} \right| = \frac{31.8 \text{ k}\Omega}{4} = 7.96 \text{ k}\Omega$$

$$R_3 = \left| \frac{-A_m R_1}{2Q^2 + A_m} \right| = \frac{2 \cdot 7.96 \text{ k}\Omega}{200 - 2} = 80.4 \text{ }\Omega$$

# **Band Pass Filters**

## **Higher Order Topology**

Replacing the  $s$  term with the transformation  $\frac{1}{\Delta\Omega} \left( s + \frac{1}{s} \right)$

in a **second order low pass transfer function** gives the general transfer function of a **fourth-order band-pass**:

$$\frac{1}{\Delta\Omega} \left( s + \frac{1}{s} \right) \rightarrow A(s) = \frac{A_0}{\prod_i (1 + a_i s + b_i s^2)}$$

$$A(s) = \frac{\frac{s^2 \cdot A_0 (\Delta\Omega)^2}{b_1}}{1 + \frac{a_1}{b_1} \Delta\Omega \cdot s + \left[ 2 + \frac{(\Delta\Omega)^2}{b_1} \right] \cdot s^2 + \frac{a_1}{b_1} \Delta\Omega \cdot s^3 + s^4}$$

$$A(s) = \frac{\frac{A_{mi}}{Q_i} \cdot \alpha s}{\left[ 1 + \frac{\alpha s}{Q_i} + (\alpha s)^2 \right]} \cdot \frac{\frac{A_{mi}}{Q_i} \cdot \frac{s}{\alpha}}{\left[ 1 + \frac{1}{Q_i} \left( \frac{s}{\alpha} \right) + \left( \frac{s}{\alpha} \right)^2 \right]}$$

$$A(s) = \frac{\frac{A_{mi}}{Q_i} \cdot \alpha s}{\left[1 + \frac{\alpha s}{Q_1} + (\alpha s)^2\right]} \cdot \frac{\frac{A_{mi}}{Q_i} \cdot \frac{s}{\alpha}}{\left[1 + \frac{1}{Q_i} \left(\frac{s}{\alpha}\right) + \left(\frac{s}{\alpha}\right)^2\right]}$$

This equation represents the connection in series of two second-order band-pass filters where:

- 1  $A_{mi}$  is the gain at the mid frequency,  $f_{mi}$ , of each partial filter

$$A_{mi} = \frac{Q_i}{Q} \cdot \sqrt{\frac{A_m}{b_1}}$$

- 2  $Q_i$  is the pole quality of each filter

$$Q_i = Q \cdot \frac{(1 + \alpha^2)b_1}{\alpha \cdot a_1}$$

$$A(s) = \frac{\frac{A_{mi}}{Q_i} \cdot \alpha s}{\left[1 + \frac{\alpha s}{Q_1} + (\alpha s)^2\right]} \cdot \frac{\frac{A_{mi}}{Q_i} \cdot \frac{s}{\alpha}}{\left[1 + \frac{1}{Q_i} \left(\frac{s}{\alpha}\right) + \left(\frac{s}{\alpha}\right)^2\right]}$$

- 3  $\alpha$  and  $1/\alpha$  are the factors by which the mid frequencies of the individual filters,  $f_{m1}$  and  $f_{m2}$ , derive from the mid frequency,  $f_m$ , of the overall bandpass.

$$f_{m1} = \frac{f_m}{\alpha} \quad f_{m2} = f_m \cdot \alpha$$

- 4 Factor  $\alpha$  needs to be determined through successive approximation, using equation:

$$\alpha^2 + \left[ \frac{\alpha \cdot \Delta\Omega \cdot a_1}{b_1(1 + \alpha^2)} \right]^2 + \frac{1}{\alpha^2} - 2 - \frac{(\Delta\Omega)^2}{b^1} = 0$$

Values of  $\alpha$  For Different Filter Types and Different values of  $Q$ :


Bessel				Butterworth				Tschebyscheff			
<b>a<sub>1</sub></b>	1.3617			<b>a<sub>1</sub></b>	1.4142			<b>a<sub>1</sub></b>	1.0650		
<b>b<sub>1</sub></b>	0.6180			<b>b<sub>1</sub></b>	1.0000			<b>b<sub>1</sub></b>	1.9305		
<b>Q</b>	100	10	1	<b>Q</b>	100	10	1	<b>Q</b>	100	10	1
<b>ΔΩ</b>	<b>0.01</b>	<b>0.1</b>	<b>1</b>	<b>ΔΩ</b>	<b>0.01</b>	<b>0.1</b>	<b>1</b>	<b>ΔΩ</b>	<b>0.01</b>	<b>0.1</b>	<b>1</b>
<b>α</b>	1.0032	1.0324	1.438	<b>α</b>	1.0035	1.036	1.4426	<b>α</b>	1.0033	1.0338	1.39



$$A(s) = \frac{\frac{A_{mi}}{Q_i} \cdot \alpha s}{\left[1 + \frac{\alpha s}{Q_1} + (\alpha s)^2\right]} \cdot \frac{\frac{A_{mi}}{Q_i} \cdot \frac{s}{\alpha}}{\left[1 + \frac{1}{Q_i} \left(\frac{s}{\alpha}\right) + \left(\frac{s}{\alpha}\right)^2\right]}$$

- 5 In a fourth-order band-pass filter with high Q, the mid frequencies of the two partial filters differ only slightly from the overall mid frequency. This method is called **staggered tuning**. A flat gain response shows up as well as a sharp pass-band to stop-band transition.

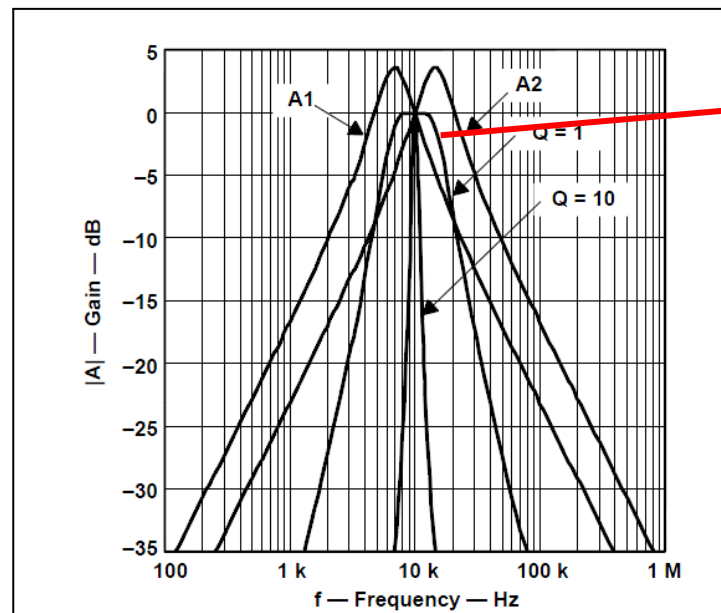
**Example:** Gain response of a fourth-order Butterworth band-pass filter with staggered tuning where with  $Q = 1$ . Its partial filters are shown as well as the gain of a non staggered tuning filter with  $Q = 10$ .



# Designing a Band Pass Filters Higher Order Topology
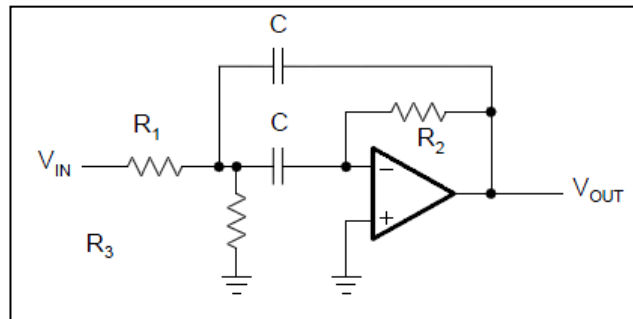
## Example:


Design a fourth-order Butterworth band-pass with  $f_m = 10\text{KHz}$ ,  $Q = 10$  and  $A_m = 1$  using a second order multiple feedback topology.



**1** From table:  $a_1 = 1.4142$ ,  $b_1 = 1$ ,  $\alpha = 1,036$



Bessel				Butterworth				Tschebyscheff			
$a_1$	1.3617			$a_1$	1.4142			$a_1$	1.0650		
$b_1$	0.6180			$b_1$	1.0000			$b_1$	1.9305		
$Q$	100	10	1	$Q$	100	10	1	$Q$	100	10	1
$\Delta\Omega$	<b>0.01</b>	<b>0.1</b>	<b>1</b>	$\Delta\Omega$	<b>0.01</b>	<b>0.1</b>	<b>1</b>	$\Delta\Omega$	<b>0.01</b>	<b>0.1</b>	<b>1</b>
$\alpha$	1.0032	1.0324	1.438	$\alpha$	1.0035	1.036	1.4426	$\alpha$	1.0033	1.0338	1.39

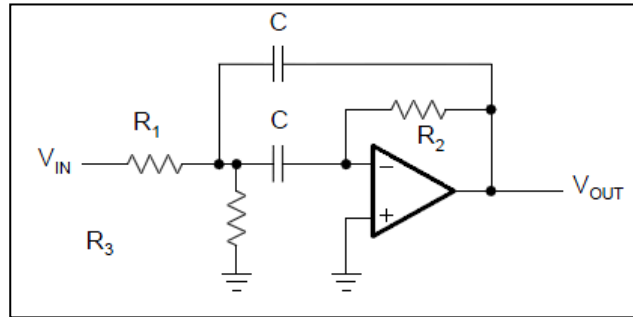


**2** Calculate  $f_{m1}$  and  $f_{m2}$

$$f_{m1} = \frac{f_m}{\alpha} \quad \rightarrow \quad f_{mi} = \frac{10 \text{ kHz}}{1.036} = 9.653 \text{ kHz}$$

$$f_{m2} = f_m \cdot \alpha \quad \rightarrow \quad f_{m2} = 10 \text{ kHz} \cdot 1.036 = 10.36 \text{ kHz}$$

**3** Calculate  $Q_i$
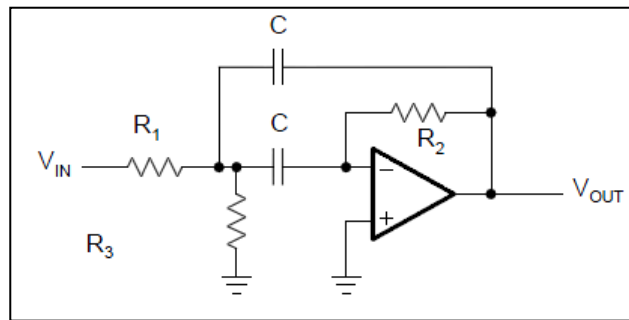
$$Q_i = Q \cdot \frac{(1 + \alpha^2)b_1}{\alpha \cdot a_1} \quad \rightarrow \quad Q_i = 10 \cdot \frac{(1 + 1.036^2) \cdot 1}{1.036 \cdot 1.4142} = 14.15$$



4 Calculate  $A_{mi}$

$$A_{mi} = \frac{Q_i}{Q} \cdot \sqrt{\frac{A_m}{b_1}} \quad \rightarrow \quad A_{mi} = \frac{14.15}{10} \cdot \sqrt{\frac{1}{1}} = 1.415$$

5 Calculate the MF resistance components for filter 1 and filter 2 using  $C = 10\text{nF}$

$$R_{2i} = \frac{Q_i}{\pi f_{mi} C} \quad R_{1i} = \left| \frac{R_2}{-2A_{mi}} \right| \quad R_{3i} = \left| \frac{-A_{mi}R_1}{2Q_i^2 + A_{mi}} \right|$$

**Filter 1:**

$$R_{21} = \frac{Q_i}{\pi f_{m1} C} = \frac{14.15}{\pi \cdot 9.653 \text{ kHz} \cdot 10 \text{ nF}} = 46.7 \text{ k}\Omega$$

$$R_{11} = \left| \frac{R_{21}}{-2A_m} \right| = \left| \frac{46.7 \text{ k}\Omega}{-2 \cdot 1.415} \right| = 16.5 \text{ k}\Omega$$

$$R_{31} = \left| \frac{-A_{mi}R_{11}}{2Q_i^2 + A_{mi}} \right| = \left| \frac{1.415 \cdot 16.5 \text{ k}\Omega}{2 \cdot 14.15^2 + 1.415} \right| = 58.1 \text{ }\Omega$$

**Filter 2:**


$$R_{22} = \frac{Q_i}{\pi f_{m2} C} = \frac{14.15}{\pi \cdot 10.36 \text{ kHz} \cdot 10 \text{ nF}} = 43.5 \text{ k}\Omega$$

$$R_{12} = \left| \frac{R_{22}}{-2A_{mi}} \right| = \left| \frac{43.5 \text{ k}\Omega}{-2 \cdot 1.415} \right| = 15.4 \text{ k}\Omega$$

$$R_{32} = \left| \frac{-A_{mi}R_{12}}{2Q_i^2 + A_{mi}} \right| = \left| \frac{1.415 \cdot 15.4 \text{ k}\Omega}{2 \cdot 14.15^2 + 1.415} \right| = 54.2 \text{ }\Omega$$

# Resultados (Simulação LTPice)


# Filtro Passa Banda (LM741)

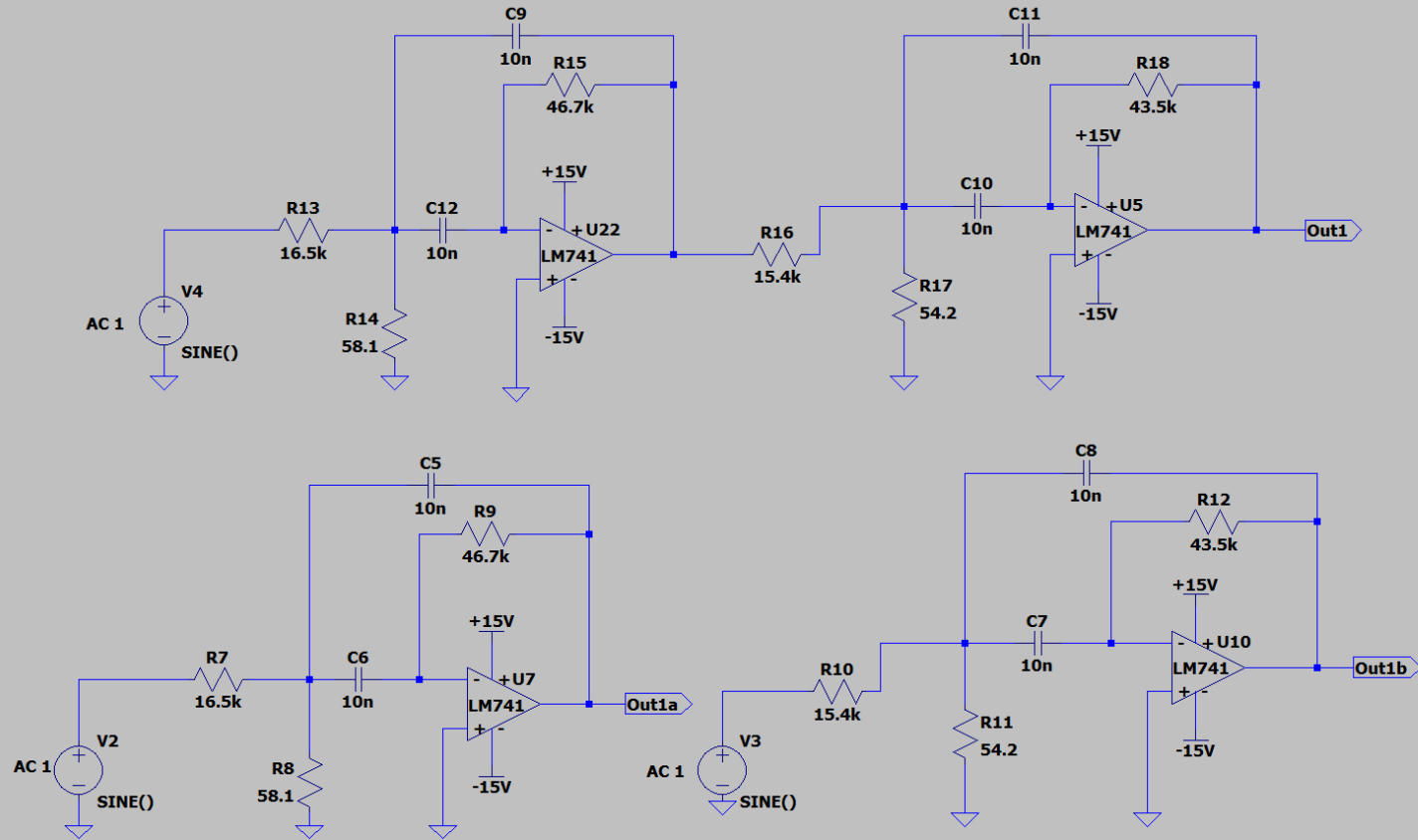

.ac dec 1000 1K 100K


Os valores dos componentes foram medidos !

# Filtro Passa Banda (LM741)

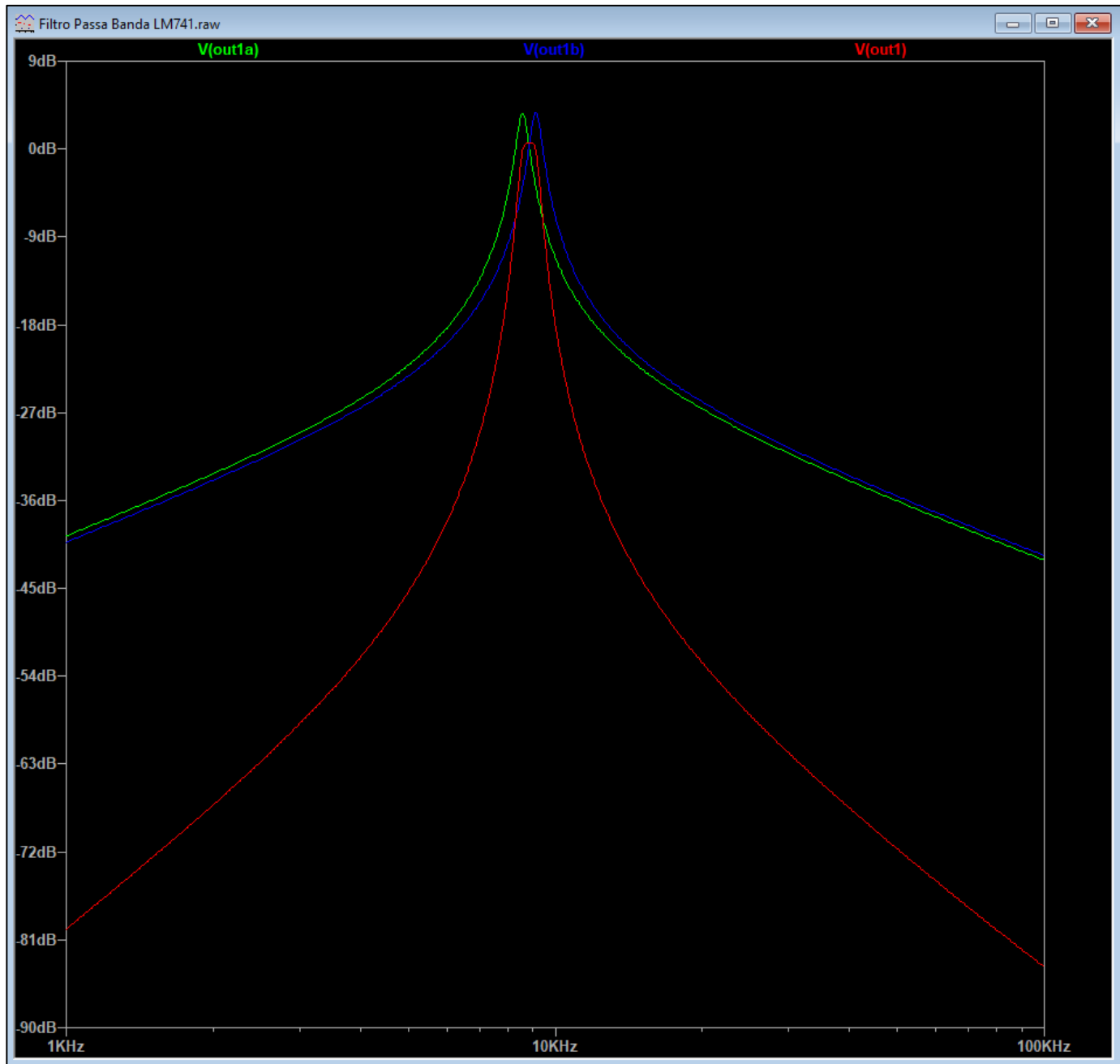




# Filtro Passa Banda (LT1022)

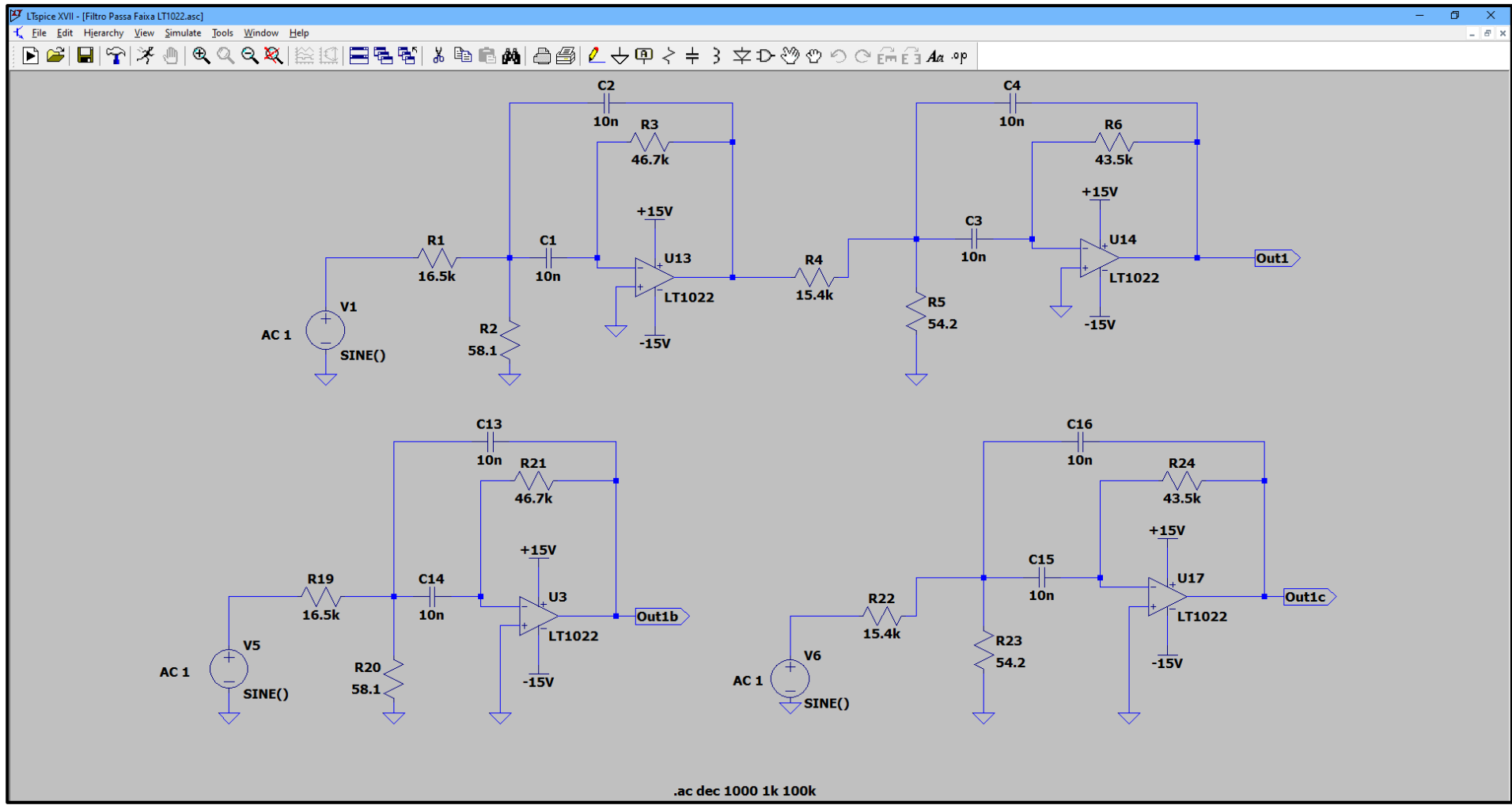


Os valores dos componentes foram medidos !

# Filtro Passa Banda (LT1022)

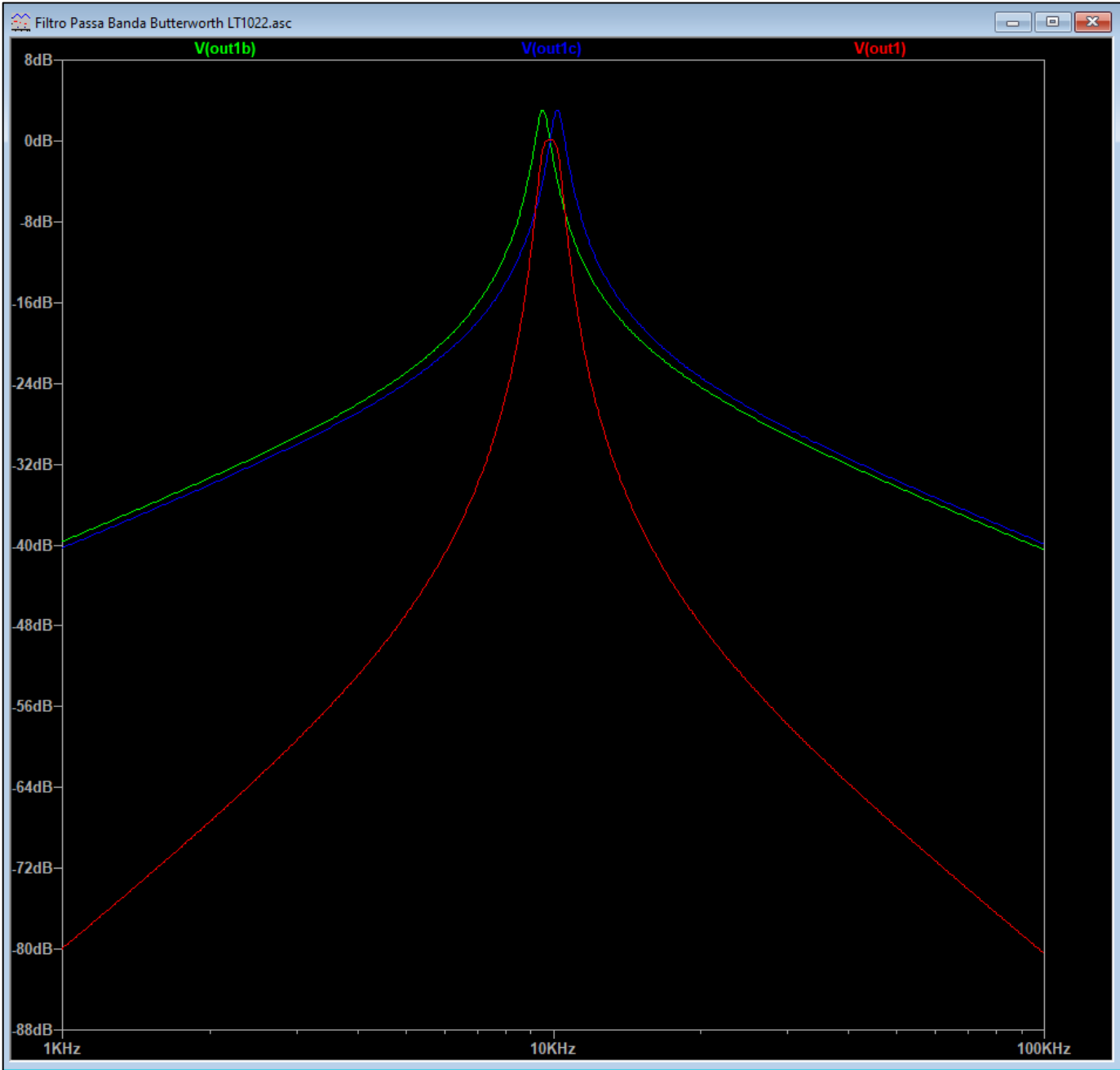
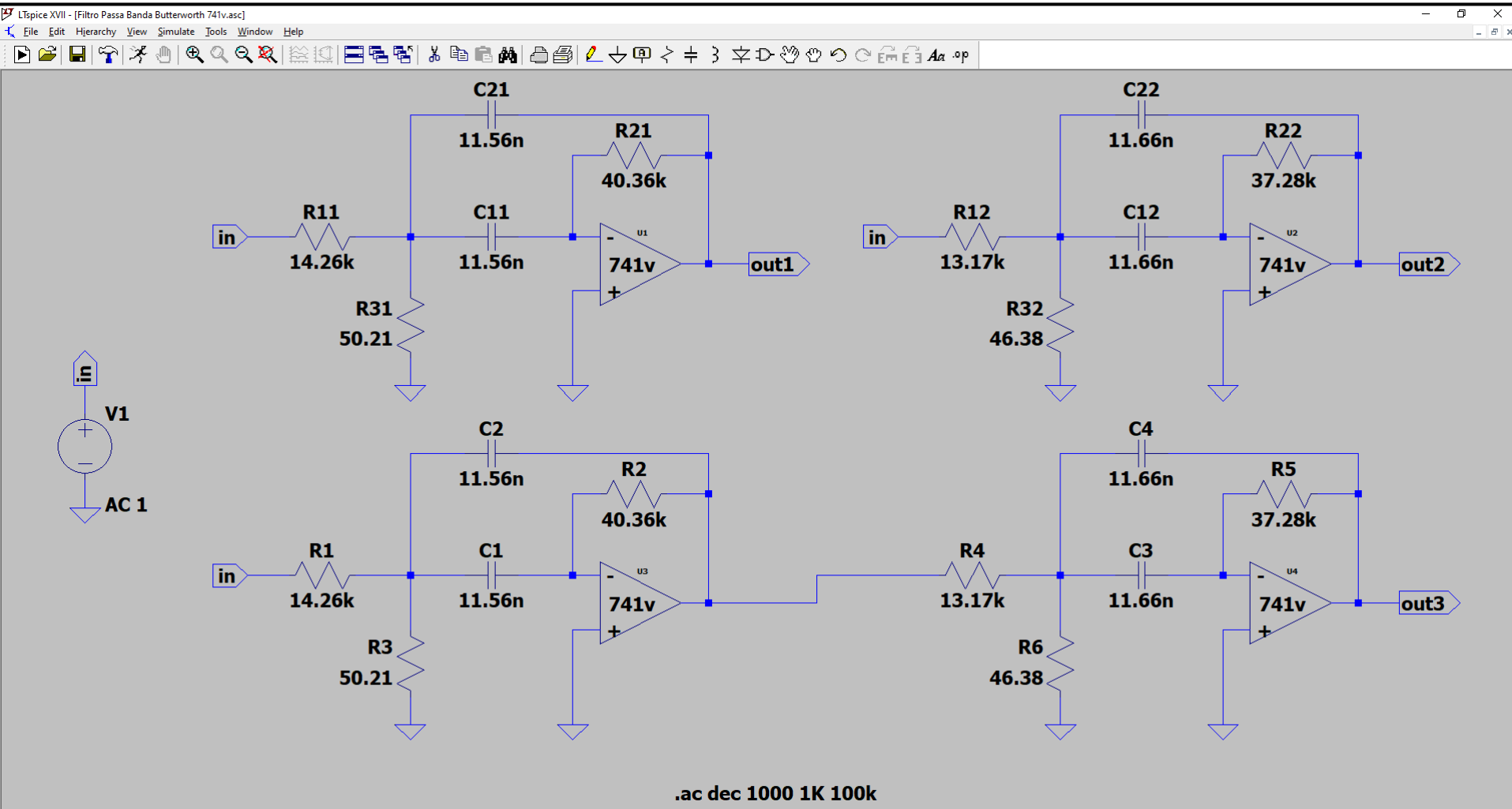
# Filtro Passa Banda (741v) (op amp projetado na disciplina SEL0315)



Os valores dos componentes  
foram medidos !

# Filtro Passa Banda (741v)

