

VIENNA Rectifier & Beyond...

Johann W. Kolar et al.



Swiss Federal Institute of Technology (ETH) Zurich
Power Electronic Systems Laboratory
www.pes.ee.ethz.ch



VIENNA Rectifier & Beyond...



J. W. Kolar, L. Schrittwieser, F. Krismer, M. Antivachis, and D. Bortis



Swiss Federal Institute of Technology (ETH) Zurich
Power Electronic Systems Laboratory
www.pes.ee.ethz.ch



Outline

- ▶ *History*
- ▶ *Vienna Rectifier*
- ▶ *Comparative Evaluation*
- ▶ *... and Beyond*
- ▶ *Future*



Source:
Li-Core

Acknowledgement

H. Ertl
T. Friedli
M. Hartmann
G. Laimer
M. Leibl
J. Miniböck

History

—

*Passive 3- Φ Rectifier
Vienna Rectifier
APEC 1998*

—

History of 3- Φ Rectifiers

- L. Kallir @ Techn. Hochschule Wien (25. Dec. 1898)
- Extension of 1- Φ Graetz/Pollak Rectifier

Zeitschrift für Elektrotechnik.

Organ des Elektrotechnischen Vereines in Wien.

Heft 52. WIEN, 25. December 1898. XVI. Jahrgang.

Gleichrichtung von Wechselströmen durch elektrische Ventile.

Von Ingenieur Ludwig Kallir.

 


Fig. 7.

 


Fig. 8.

- ▶ Electrolytic Cells, Sparc Gaps, Discharge Tubes as „Valves“

Vienna Rectifier

- Patent filed Dec. 23, 1993
- Name Acknowledging



TECHNISCHE
UNIVERSITÄT
WIEN
Vienna University of
Technology



Europäisches Patentamt
European Patent Office
Office européen des brevets



① Veröffentlichungsnummer: **0 660 498 A2**

②

EUROPÄISCHE PATENTANMELDUNG

② Anmeldetag: 20.12.94

③ Priorität: 23.12.93 AT 2612/93

③ Veröffentlichungstag der Anmeldung:
28.06.95 Patentblatt 95/26

② Erfinder: Kolar, Johann W.
Straussengasse 2-10/2/68
A-1050 Wien (AT)

EP 0 660 498 A2


 
 
 


Fig. 1

- ▶ First Demonstrator for *High-Power Telecom Rectifier*

APEC ... 20 years ago

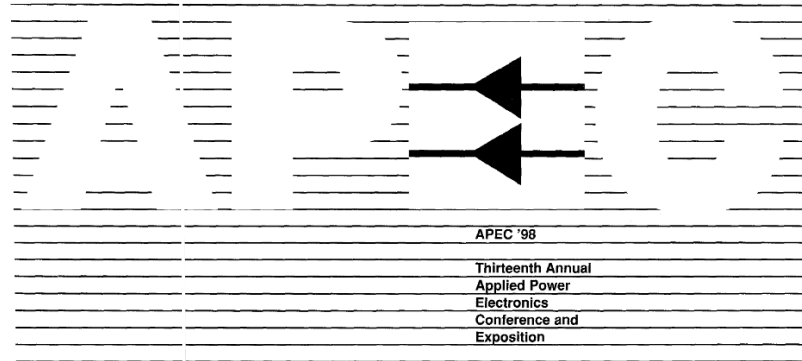


CONTENTS

Volume 1

Monday, February 16 - Grand Ballroom, 1:30 p.m. - 5:00 p.m.


SESSION 1: Plenary Session	1
Chairman: F. Dong Tan, TRW S&EG, Redondo Beach, CA	
1.1 Power Technology Roadmap	3
D. Staffiere, Staffiere Consulting Services, Amherst, NH and J. Sarjeant, State University of New York at Buffalo, Buffalo, NY	
1.2 A Framework for Developing Power Electronics Packaging	9
D. Hopkins, State University of New York, Binghamton, NY, S. Mathuna, University College, Cork, IRELAND, A. Alderman, International Rectifier, El Segundo, CA and J. Flannery, University College, Cork, IRELAND	
1.3 A Checklist of What Can Zap Your Power Electronics	16
A. Brockschmidt, Boeing Defense & Space Group, Seattle, WA	
1.4 Vienna Rectifier II - A Novel Single-Stage High-Frequency Isolated Three-Phase PWM Rectifier System	23
J. Kolar, U. Drofenik and F. Zach, Technical University Vienna, Wien, AUSTRIA	
1.5 High Power Density Electric Drive for an Hybrid Electric Vehicle	34
C. Namuduri and B. Murty, General Motors R&D Center, Warren, MI	
1.6 Intellectual Property: Rich By-Product of Intellectual Capital	41
D. Drinkwater, Digital Equipment Corporation, Maynard, MA	

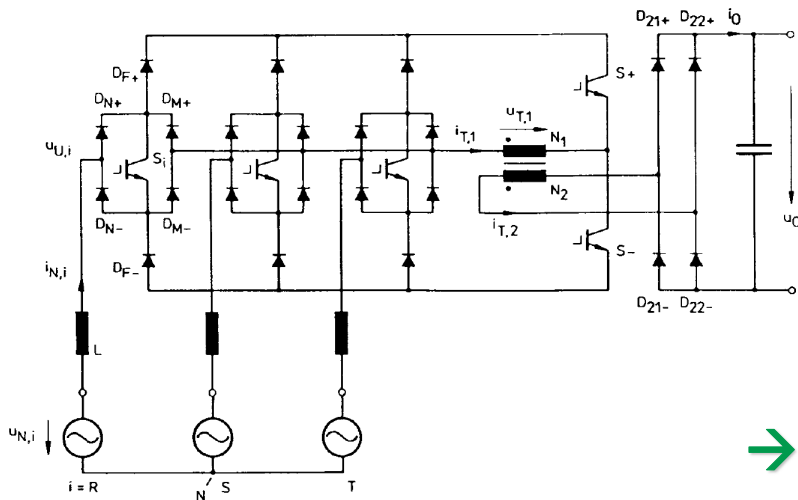

► Plenary Presentation @ APEC 1998



Vienna Rectifier

 Topology Derivation
Basic Function
Hardware Demonstrator



3- Φ Diode Bridge Rectifier

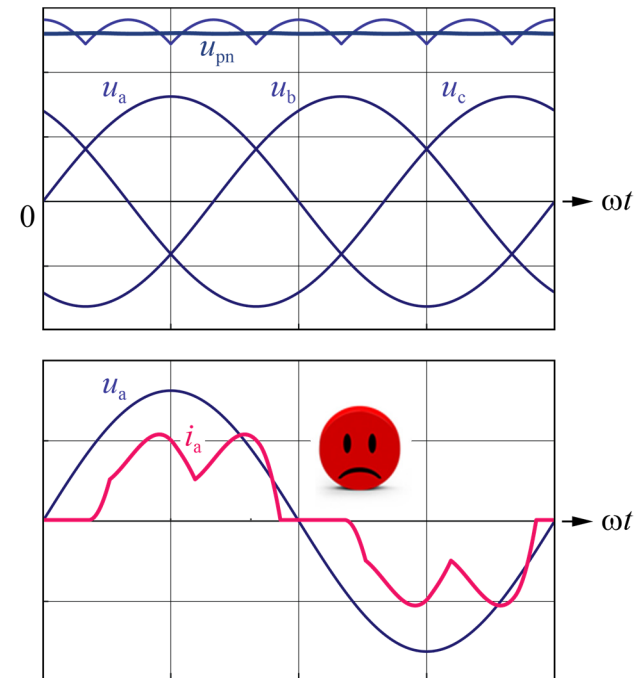 
- Conduction States Defined by *Line-to-Line* Mains Voltages
- Intervals with *Zero Current* / LF Harmonics
- No Output Voltage Control



► Modulation of Diode Bridge Input Voltages

Vienna Rectifier (1)


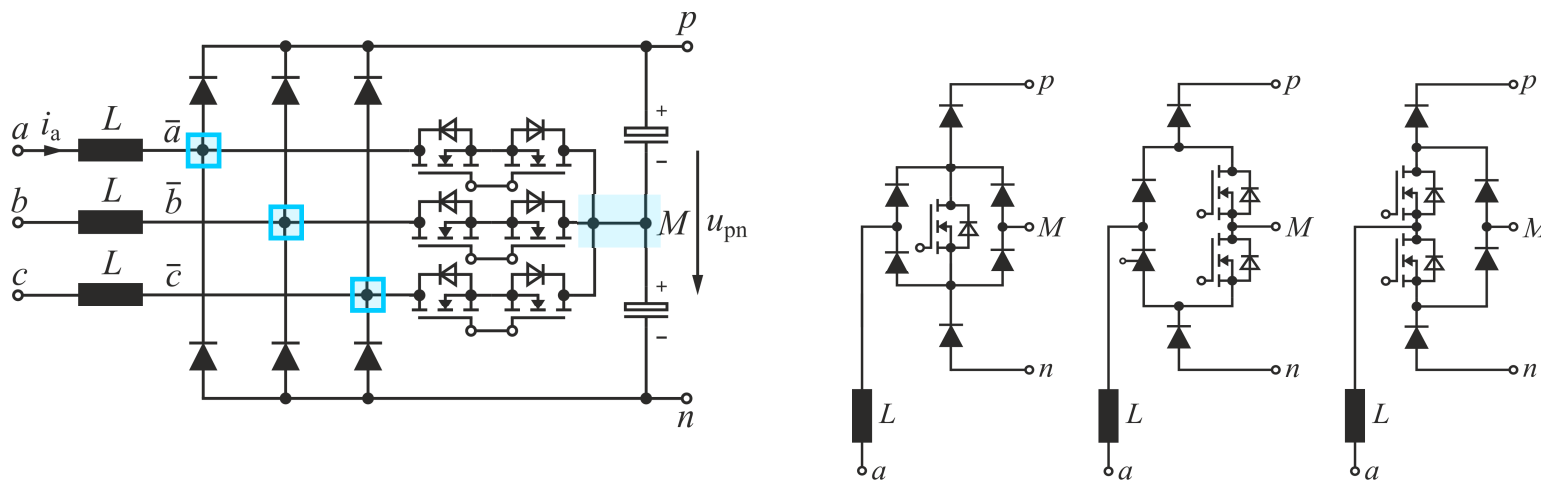
- *Active Control of Diode Bridge Conduction State / Input Voltages*
- Bridge Leg Topologies with Different Voltage Stresses / Cond. Losses
- Phase & Bridge Symmetry !



► Analysis of Input Voltage Formation

Vienna Rectifier (2)

 
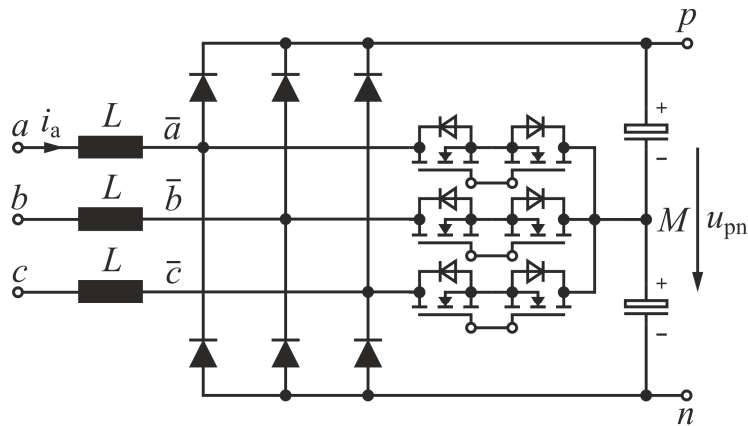
- **Diode Bridge Input Voltage Formation Dependent on Current Direction**
- **Min. Output Voltage Defined by Mains Line-to-Line Voltage Amplitude**
- **Boost-Type**



► Sinusoidal Input Current Shaping

Vienna Rectifier (3)

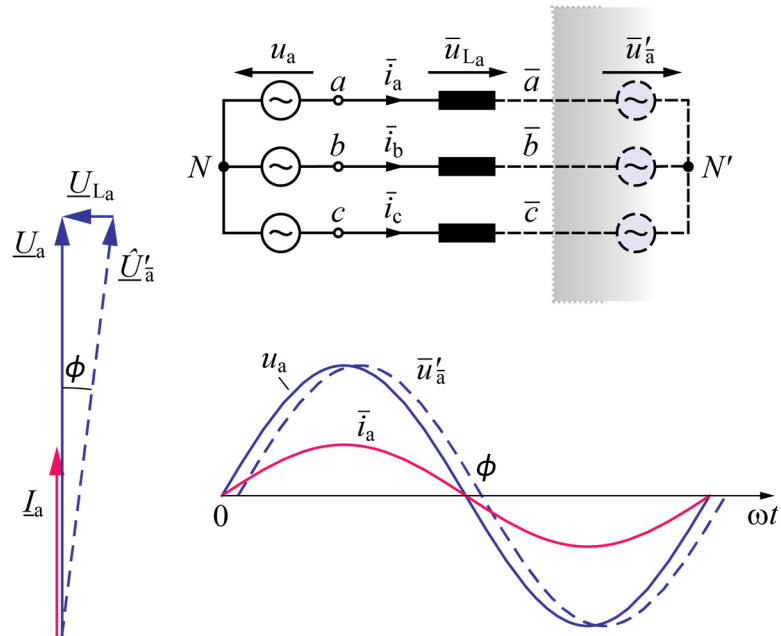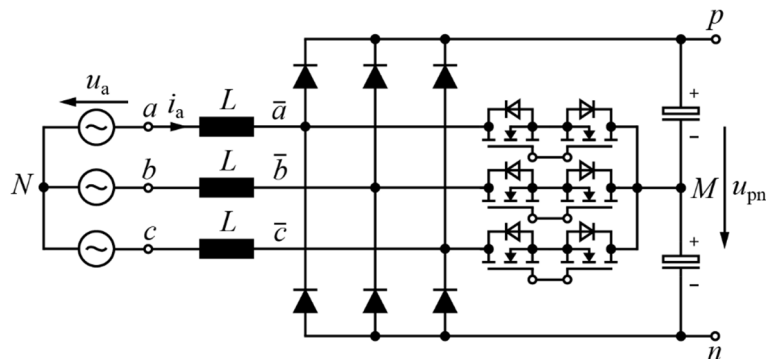
- *Input Current Impressed by Difference of Mains & Diode Bridge Input Voltage*
- $\Phi = (-30^\circ, +30^\circ)$ *Limit Due to Current Dependent Voltage Formation*




► Time Behavior of PWM Voltages


Vienna Rectifier (4)

 - **3-Level Bridge Leg Characteristic / 9-Level Phase Voltage**
- **Low Input Current Ripple / Low Inductance L**
- **Switching Frequency CM Output Voltage**





► **Multi-Loop Control Structure**

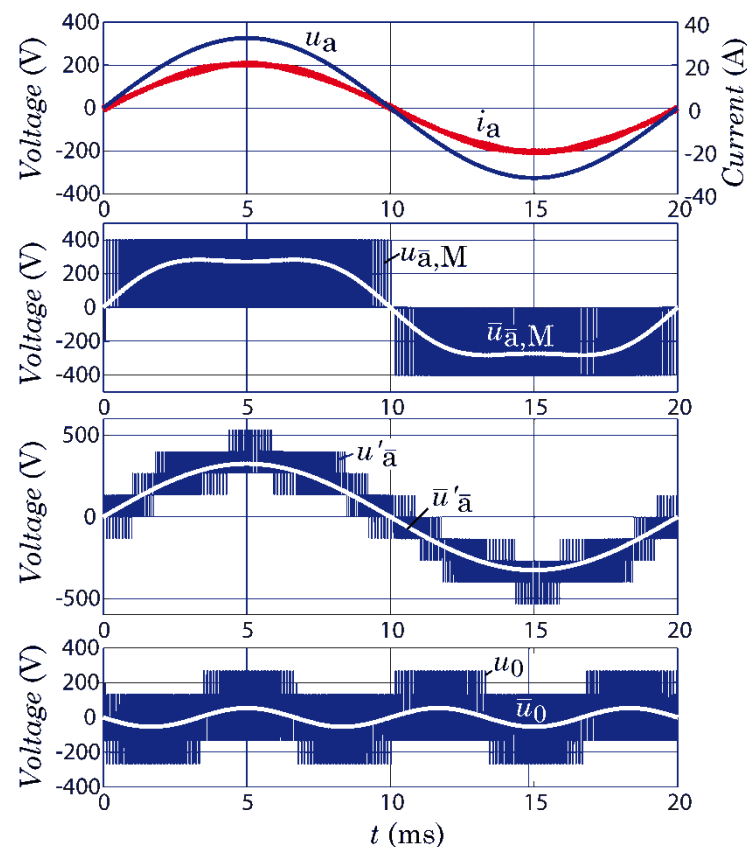

 

Vienna Rectifier (5)

 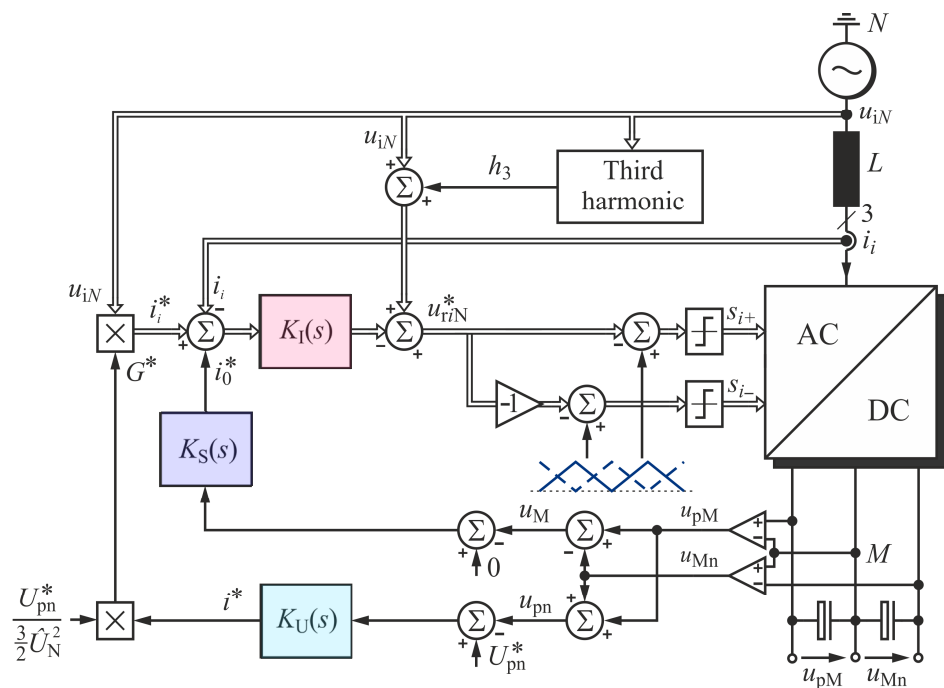
- **Output Voltage Control / Inner Mains Current Control**
- **Add. Control Loop for DC Midpoint Balancing**
- **Redundant Sw. States Utilized for DC Midpoint Balancing**



► **Multi-Stage Diff. Mode & Common Mode EMI Filter**

Vienna Rectifier (6)

 - *CM EMI Filtering Utilizing Internal Cap. Connection to Virtual Star Point*
- No Limit of CM Capacitance by Max. Leakage Current
- CM Filter Stage(s) on DC-Side as Alternative



- ▶ Number of Filter Stages Dependent on Sw. Frequency

Vienna Rectifier (7)



- Highly-Compact Demonstrator System
- CoolMOS & SiC Diodes
- Coldplate Cooling

$P_o = 10 \text{ kW}$
 $U_N = 400\text{V}_{AC} \pm 10\%$
 $f_N = 50\text{Hz or } 360 \dots 800\text{Hz}$
 $U_o = 800\text{V}_{DC}$

$\eta = 96.8\%$

★ $\rho = 10 \text{ kW/dm}^3$

 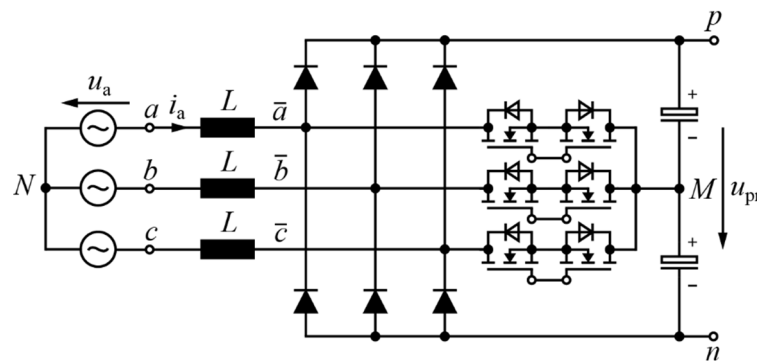► $THD_i = 1.6\% @ f_N = 800\text{Hz} (f_p = 250\text{kHz})$




Vienna Rectifier (8)

- Highly-Compact Demonstrator System
- CoolMOS & SiC Diodes
- Coldplate Cooling


$P_o = 10 \text{ kW}$
 $U_N = 400V_{AC} \pm 10\%$
 $f_N = 50\text{Hz or } 360 \dots 800\text{Hz}$
 $U_o = 800V_{DC}$

$\eta = 96.8\%$
 $\rho = 10 \text{ kW/dm}^3$
 $f_p = 250\text{kHz}$

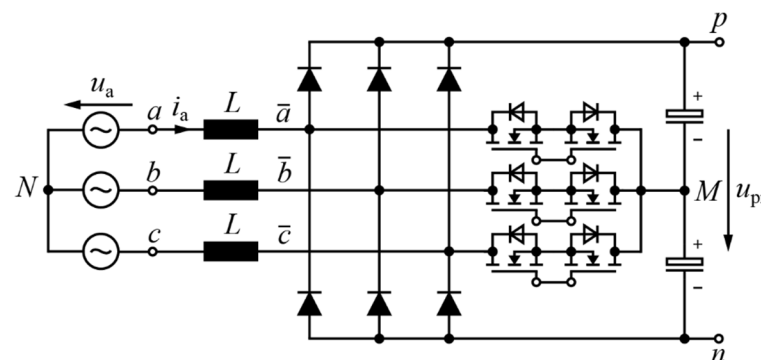- ▶ $THD_i = 1.6\%$ @ $f_N = 800\text{Hz}$
- ▶ System Allows 2- Φ Operation





10A/Div
 200V/Div
 0.5ms/Div

 

Vienna Rectifier (9)

- Dependency of Power Density on Sw. Frequency f_p
- CoolMOS & SiC Diodes
- Coldplate Cooling

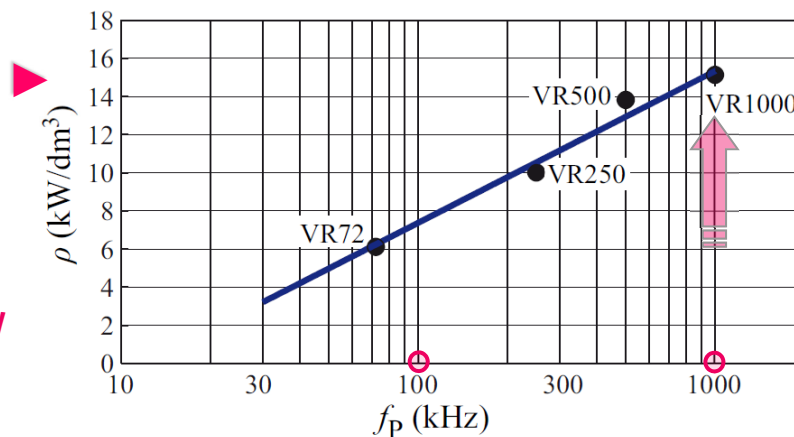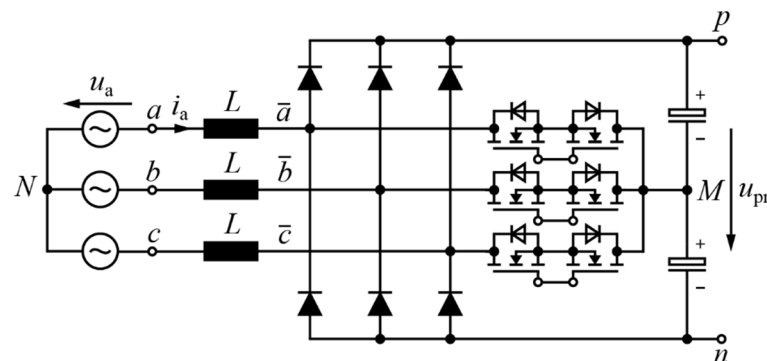$P_o = 10 \text{ kW}$
 $U_N = 230V_{AC} \pm 10\%$
 $f_N = 50\text{Hz or } 360 \dots 800\text{Hz}$
 $U_o = 800V_{DC}$



- ▶ Factor 10 in $f_p \rightarrow$ Factor 2 in Power Density
- ▶ Systems with $f_p = 72/250/500/1000\text{kHz}$



Comparative Evaluation

— *3L-Topology* vs. *2L-Topology* —





Comparative Evaluation (1)

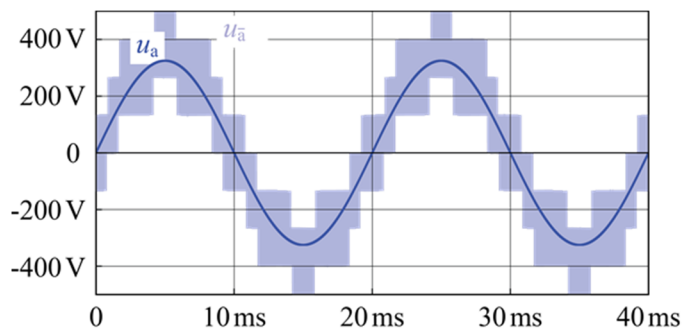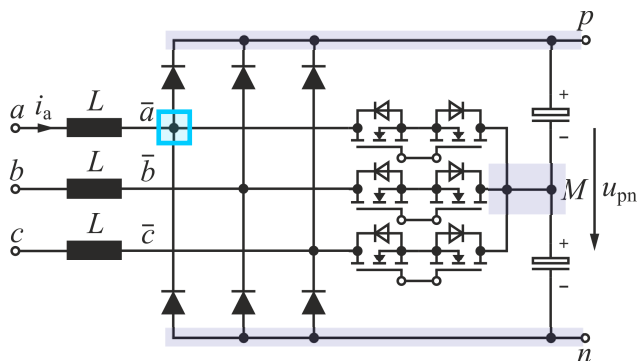- Comparison to Standard 2-Level PWM Rectifier
- 9 vs. 5 Volt. Levels & Factor 2...3 Lower Sw. Losses → Factor 4...6 (!) Lower L





■ Vienna Rectifier

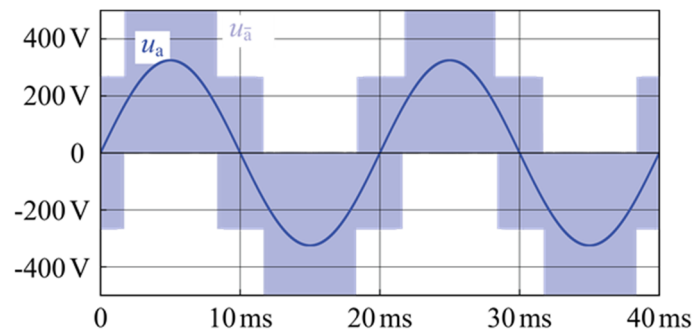 



■ Standard PWM Rectifier

Comparative Evaluation (2)

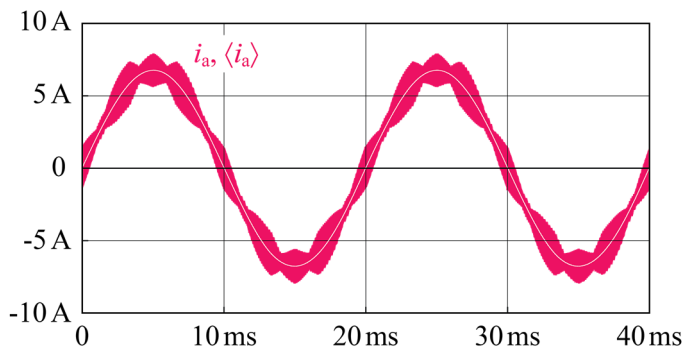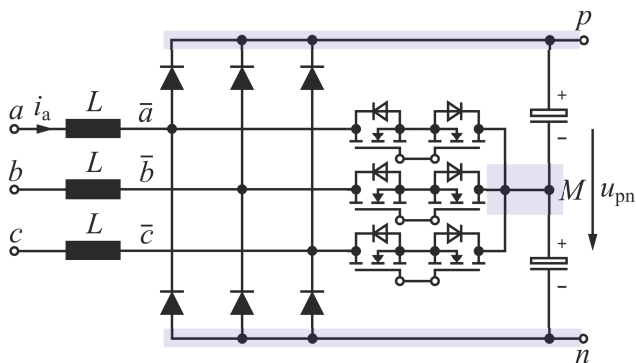- Comparison to Standard 2-Level PWM Rectifier
- 9 vs. 5 Volt. Levels & Factor 2..3 Lower Sw. Losses → 12 kW/dm³ vs. 8 kW/dm³ @ 22kW



■ Vienna Rectifier

 
 


■ Standard PWM Rectifier

Conceptual Limits



 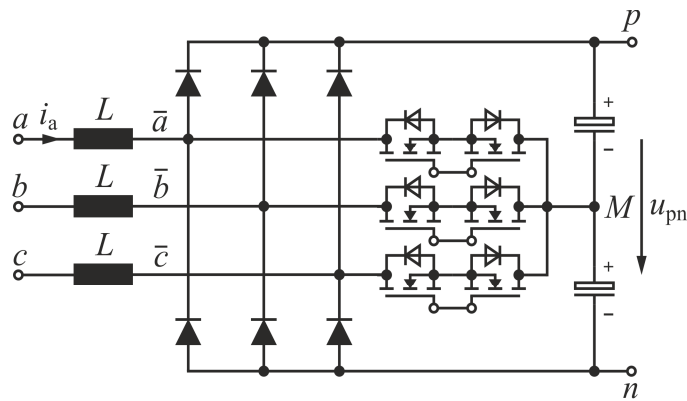- **Boost-Type**
- **No Isolation**
- **Unidirectional (in Basic Form)**




► **Buck-Type & Buck-Boost Topologies / Single-Stage Isolated Systems**

Buck-Type

Integr. Active Filter PFC Rectifier
1-of-3 PWM Rectifier
SWISS Rectifier



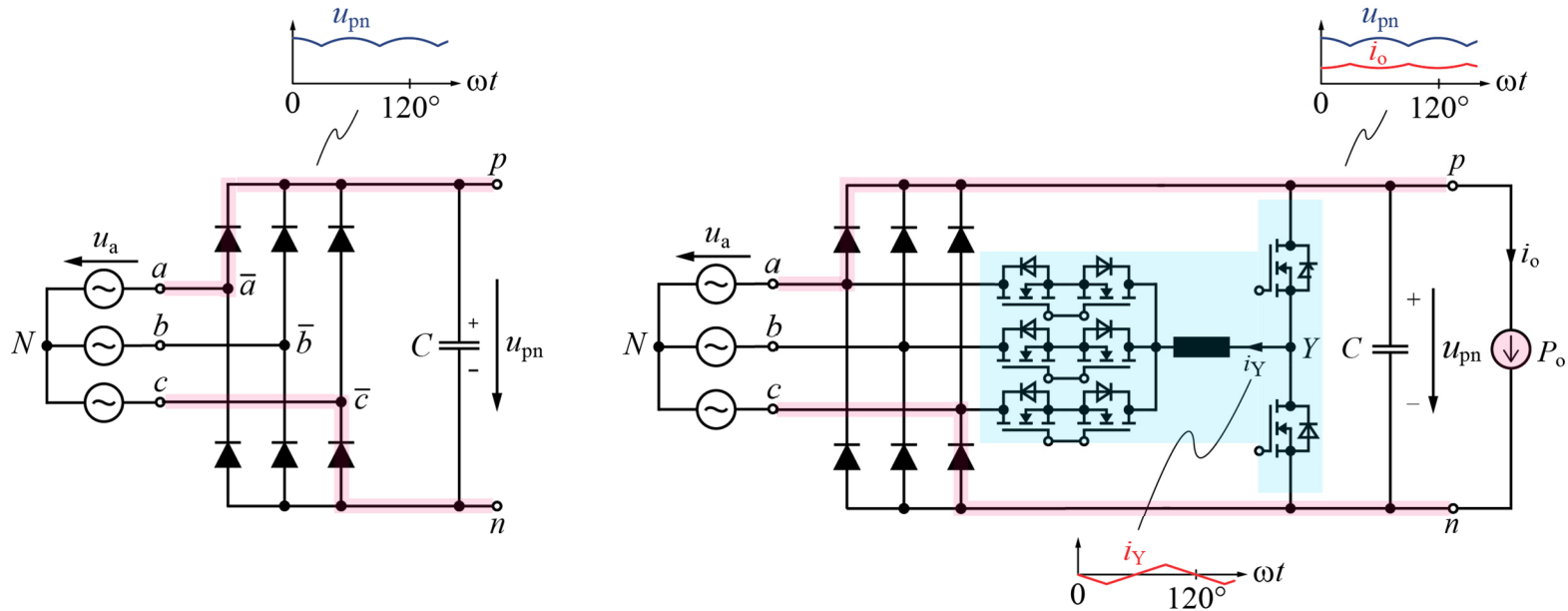Integr. Active Filter (IAF) PFC Rectifier




■ Non-Sinusoidal Mains Current

- $P_o = \text{const.}$ Required
- **NO (!) Output Voltage Control**
- **Basic Idea: M. Jantsch, 1997 (for PV Inv.)**

IAF Rectifier

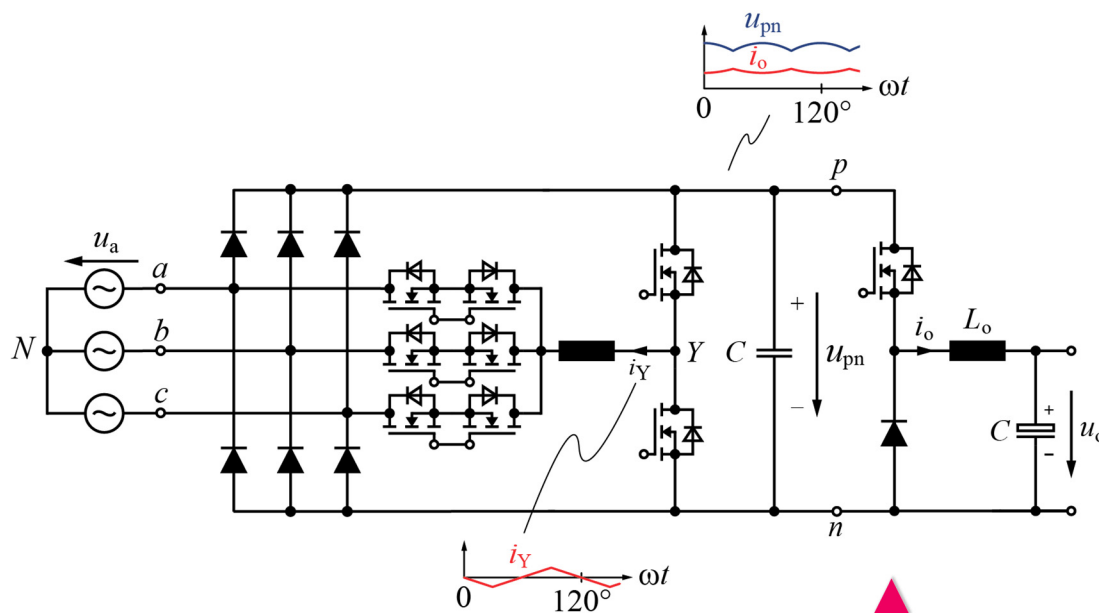- 3rd Harm. Injection into "Middle" Phase
- *Buck-Output Stage for $P_o = \text{const.}$ & *Outp. Voltage Control**
- Sinusoidal Current in All Phases




► Buck-Stage Could be Replaced by *Isol. DC/DC Conv.* or *Inverter*



IAF Rectifier Demonstrator

- Efficiency $\eta > 99.1\%$ @ 60% Rated Load
- Mains Current $THD_I \approx 2\%$ @ Rated Load
- Power Density $\rho \approx 4\text{kW}/\text{dm}^3$

 $P_o = 8\text{ kW}$
 $U_N = 400\text{V}_{AC} \rightarrow U_o = 400\text{V}_{DC}$
 $f_s = 27\text{kHz}$



  
- ▶ SiC Power MOSFETs & Diodes
- ▶ 2 Interleaved Buck Output Stages




—— *1-out-of-3 Rectifier* ——

1-out-of-3 PWM Boost+Buck Rectifier

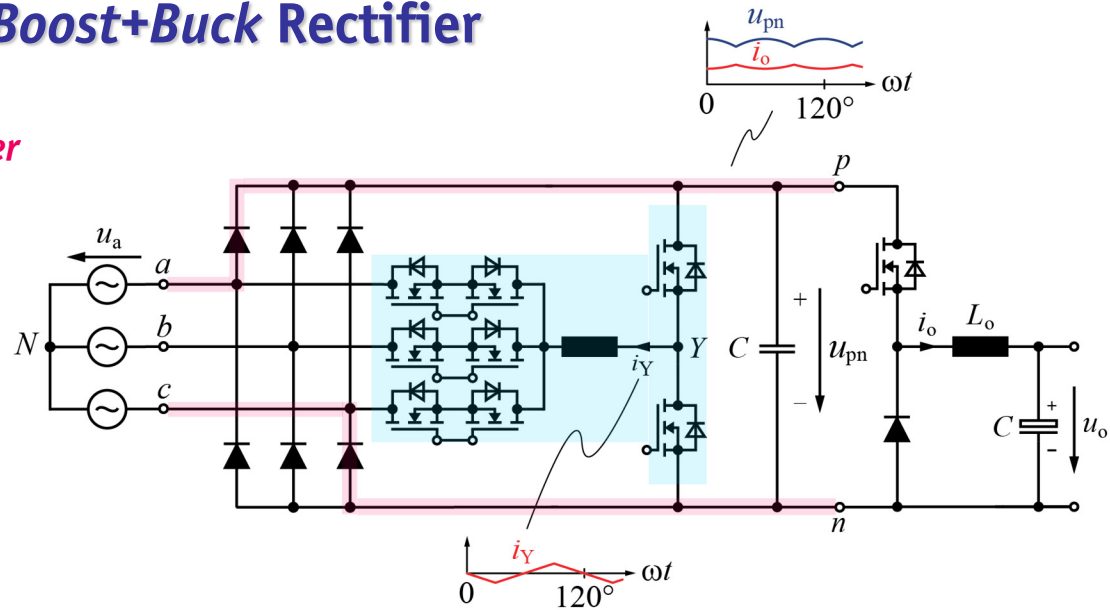- *IAF Buck-Type Rectifier*
- **Unidirectional**





 - *Buck- or Boost+Buck-Type*
- **Bidirectional / Inv. Operation**
- *Similar Concept: D. Neacsu, 2012*



1/3 PWM Boost+Buck Rectifier

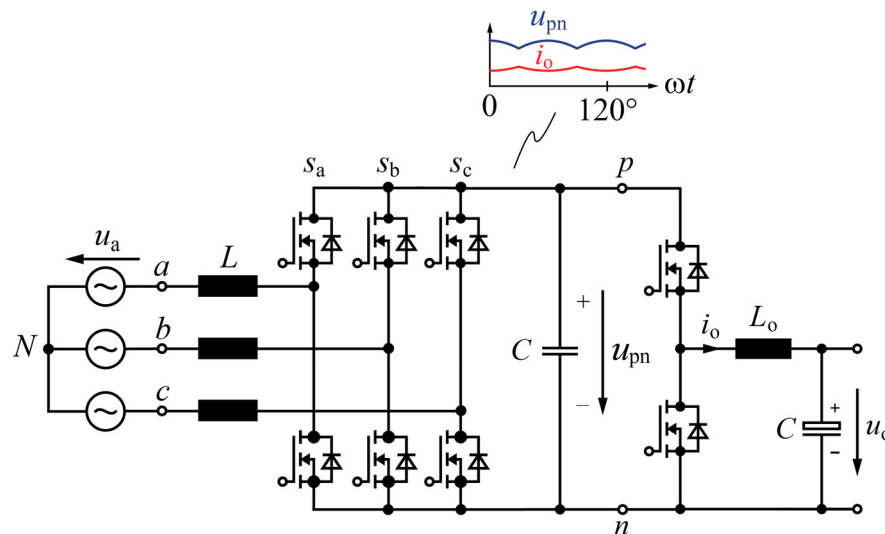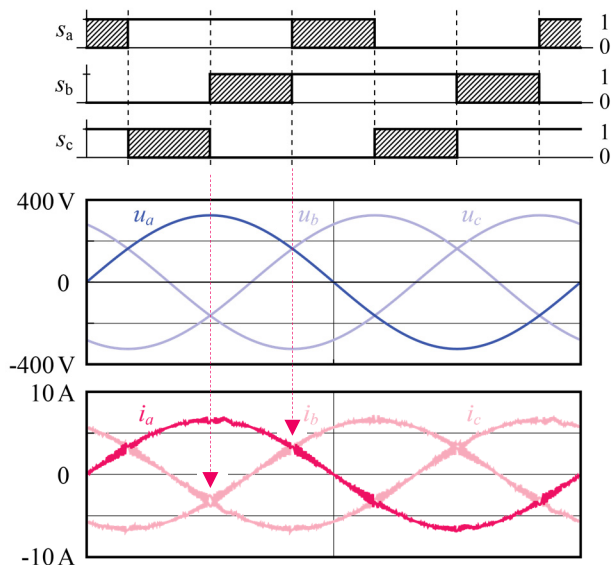- *Buck-Stage Utilized for DC Link Voltage Shaping / Control of 2 Mains Phase Currents*
- *Low Switching Losses / High Efficiency*
- *Cont. Input & Output Currents*





► Option → Operation as *Conv. Boost-Type Const. DC-Link Voltage* PWM Rectifier

—— *SWISS Rectifier* ——



Swiss Rectifier

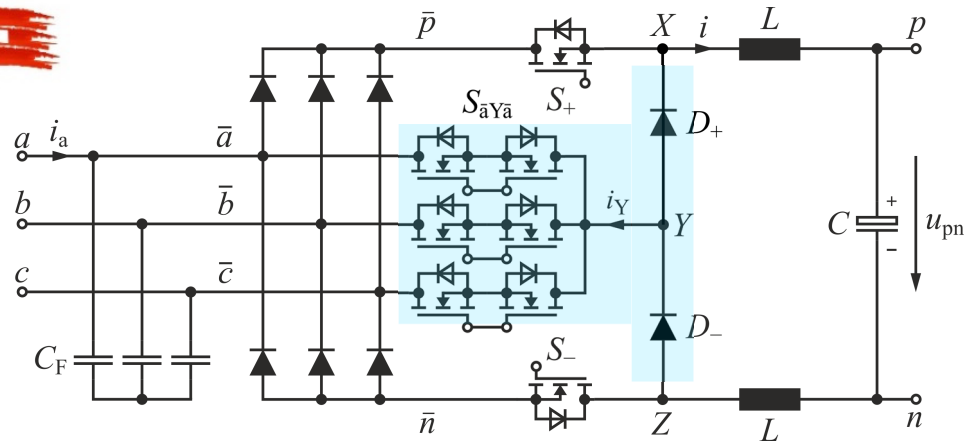 - Controlled Output Voltage
- Sinusoidal Mains Current
- i_y Def. by KCL: E.g. $i_a - i_c$



► Low Complexity


Swiss Rectifier Demonstrator

- Efficiency $\eta = 99.26\%$ @ 60% Rated Load
- Mains Current $THD_I \approx 0.5\%$ @ Rated Load
- Power Density $\rho \approx 4\text{kW}/\text{dm}^3$



$$P_o = 8\text{ kW}$$

$$U_N = 400\text{V}_{AC} \rightarrow U_o = 400\text{V}_{DC}$$

$$f_s = 27\text{kHz}$$

 

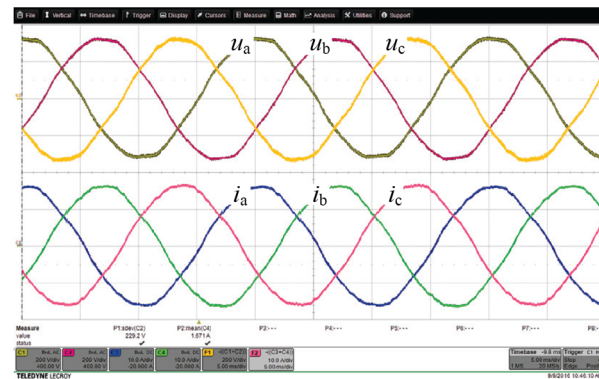 - ▶ SiC Power MOSFETs & Diodes
- ▶ Integr. CM Coupled Output Inductors (ICMCI)







Buck+Boost-Type

Y_3 -Rectifier



Buck+Boost PWM Y_3 -Rectifier

    - Voltage Reference Potential Shifted from DC-Midpoint to **Neg. DC-Link Rail**
- **Front-End Buck-Stage / Phase** → Buck+Boost Operation






► **Bidirectional** & **Wide Input and Output Voltage Range**

Basic Idea: S. Cuk, 1982

Y₃-Rectifier

 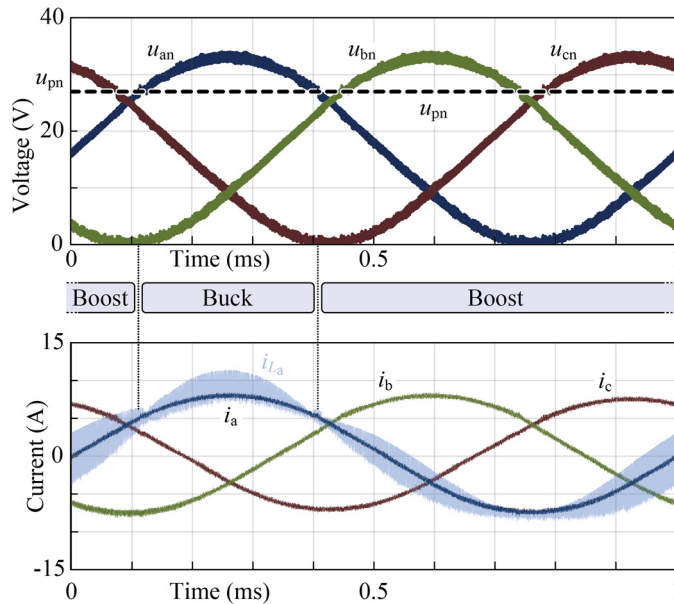 - **Rectifier Operation with Fully Controlled Input Filter**
- **Inverter Operation with Continuous Output Voltage (!)**
- **All-GaN Demonstrator**




→ **Session T32** ← “Grid Applications”, ROOM 217-D, Thursday, 8:30 a.m. – 11:20 a.m.

Isolated Single-Stage



Matrix-Type Rectifier
D3AB-Rectifier




Isolated *Matrix-Type* PFC Rectifier

 

  - **Based on Dual Active Bridge (DAB) Concept**
- **Opt. Modulation ($t_1 \dots t_4$) for Min. Transformer RMS Curr. & ZVS or ZCS**
- **Allows Buck-Boost Operation**



► Equivalent Circuit

 


► Transformer Voltages / Currents



Isolated Matrix-Type PFC Rectifier

- Efficiency $\eta = 98.9\%$ @ 60% Rated Load (ZVS)
- Mains Current $THD_I \approx 4\%$ @ Rated Load
- Power Density $\rho \approx 4\text{kW}/\text{dm}^3$

 $P_o = 8\text{ kW}$
 $U_N = 400\text{V}_{AC} \rightarrow U_o = 400\text{V}_{DC}$
 $f_s = 36\text{kHz}$




 
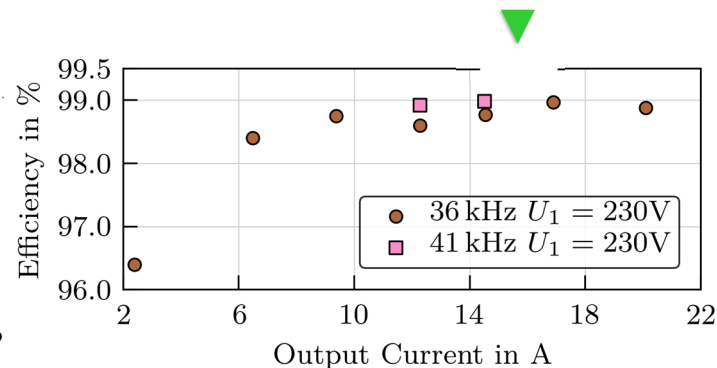
- ▶ 900V / 10mΩ SiC Power MOSFETs
- ▶ Opt. Modulation Based on 3D Look-Up Table



*Isolated
Dual 3- Φ Active Bridge
Rectifier*

Dual 3- Φ Active Bridge PFC Rectifier

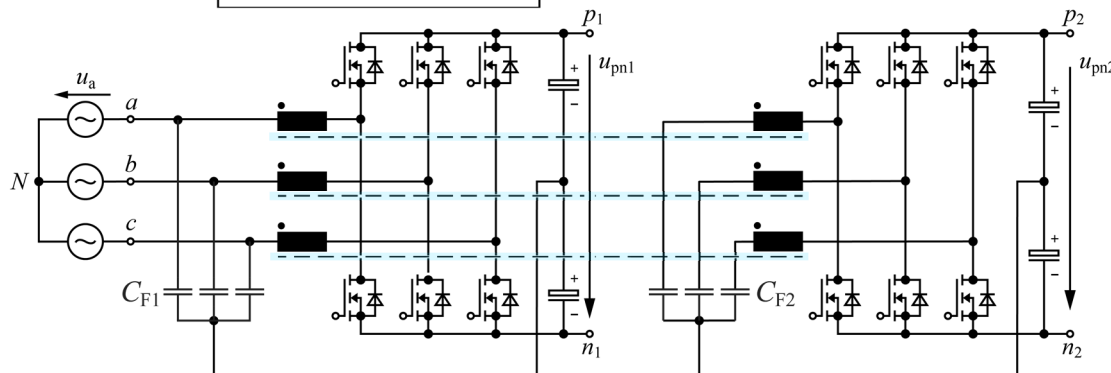  
- *HF-Components of Boost Ind. Voltages Utilized for Power Transfer*
- *Dual Active Bridge Concept*
- *ZVS*




► *Three-Port System* - AC Input / Isol. DC Output / Non-Isol. DC Output

Dual 3- Φ Active Bridge PFC Rectifier

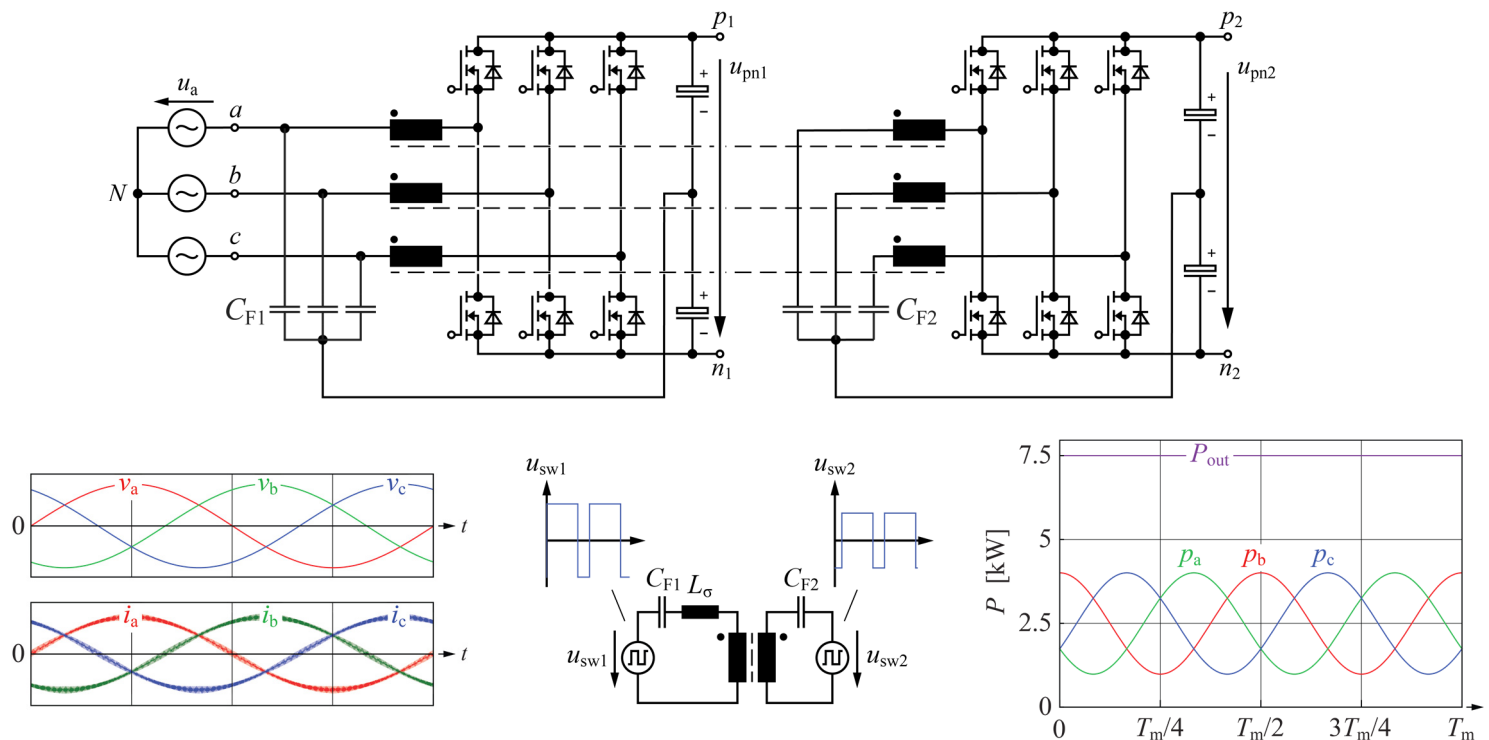- HF-Components of Boost Ind. Voltages Utilized for Power Transfer
- Dual Active Bridge Concept
- ZVS



 ► **Three-Port System** - AC Input / Isol. DC Output / Non-Isol. DC Output



Source: whiskeybehavior.info




Overall Summary

Conclusions

- Several "Black-Belt" PFC Rectifier Topologies
- Highly-Efficiency → 99.5% / 99% Non-Isolated/Isolated
- High Compactness → 10...12kW/dm³

Further Improvements

- Higher Number of Levels (?)

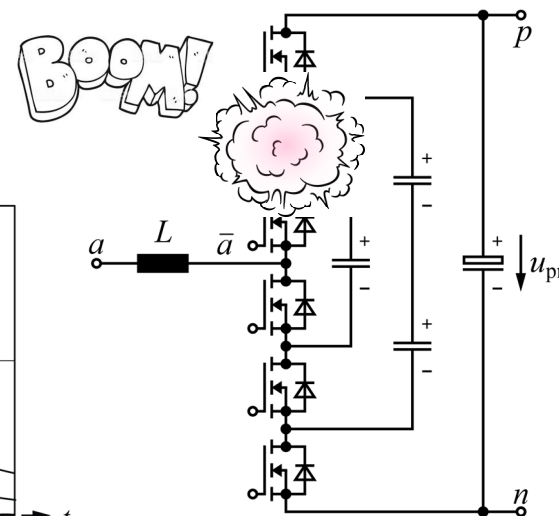  


► Higher Number of Levels → Lower Reliability → Only Fault-Tolerant Topologies Survive!

Further Improvements (cont.)

■ Faster Switching (?)



 Little-Box 2.0
 240 W/in³

  

- ▶ 140W/in³ @ $f_s=250\dots1000\text{kHz}$
- ▶ 240W/in³ @ $f_s=140\text{kHz}$
- ▶ Mapping of Comp. Technologies into Syst. Performance Largely Unclear

■ Faster Design & Development (!)


- ▶ Mutual Coupling of Performance Indices
- ▶ Simulation Tools for Optimal Design / Trade-Offs
- ▶ Design for Manufacturing & Measurement
- ▶ "Digital Twin" – Measurement & Simulation



Future Development 1/2

- Commoditization / Standardization
- Extreme Cost Pressure (!)

 “There is Plenty of Room at the Top” → Medium Voltage/Frequency Solid-State Transformers




Power-Supplies on Chip ← “There is Plenty of Room at the Bottom”

► Key Importance of Technology Partnerships of Academia & Industry

Future Development 2/2

■ Extrapolation of Technology S-Curve

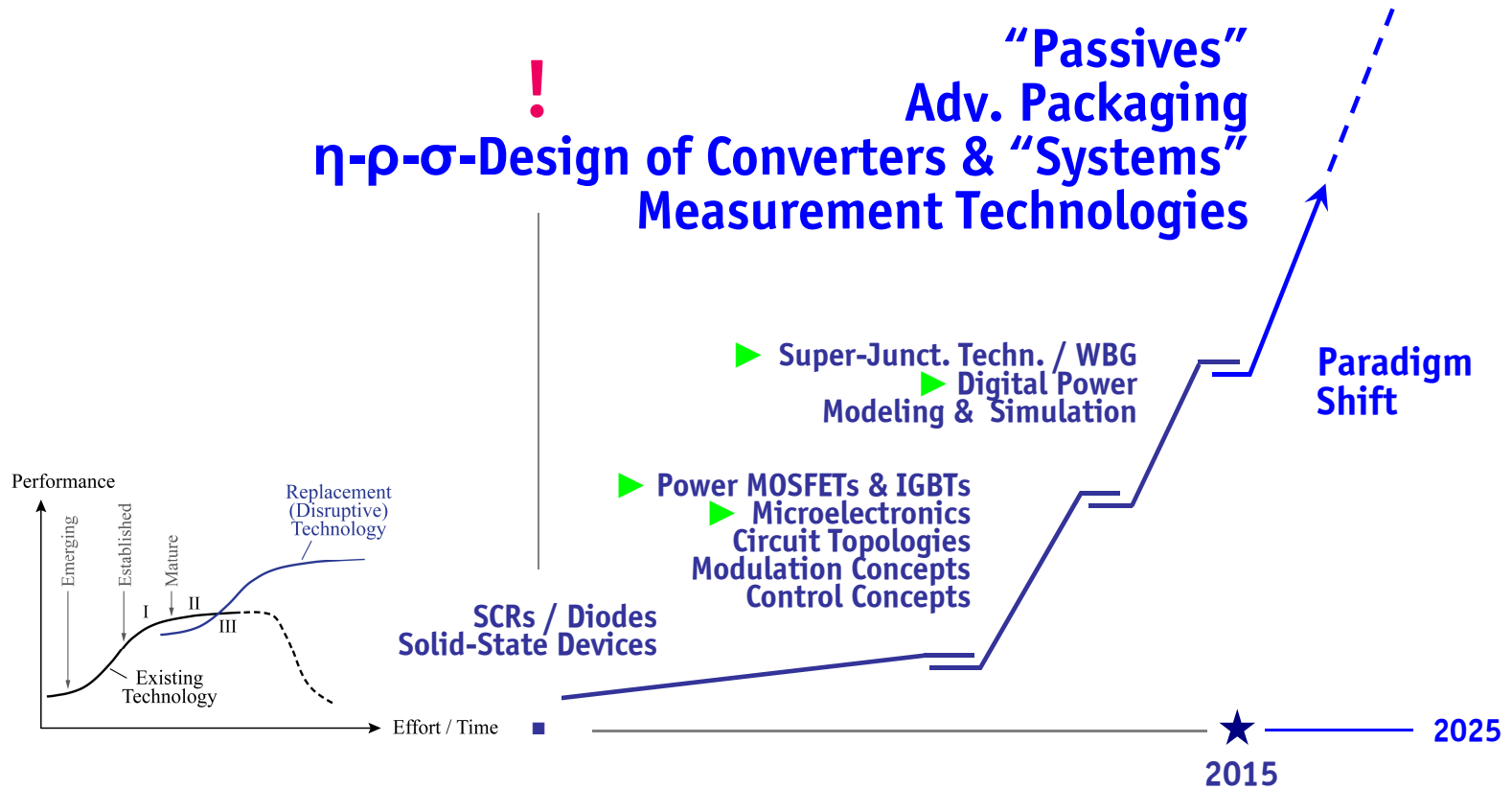


Thank You !






Y-Rectifier Δ-Rectifier


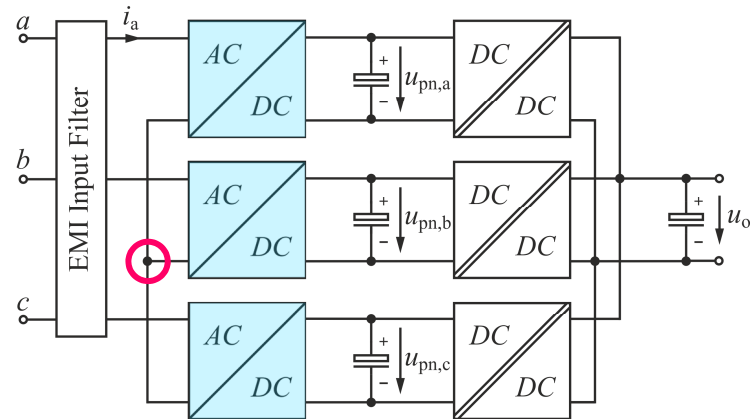


 - Balancing of Phase Modules
- High Semiconductor Voltage Stress



■ Δ-Rectifier Clearly Preferable

Six-Switch *Buck-Type* PFC Rectifier

  


■ Derivation of Rectifier Topology


- ➔ Controllability of Conduction State
- ➔ Phase-Symmetry / Bridge-Symmetry

Technology Progress – *Technology Push*

 - **WBG Semiconductor Technology** → Higher Efficiency, Lower Complexity
- **Microelectronics** → More Computing Power



→ + Advanced Packaging (!)



 


→ Moore's Law

System / Smart Grid Drivers

Metcalfe's Law

   - Moving from Hub-Based Concept to Community Concept Increases Potential Network Value Exponentially ($\sim n(n-1)$ or $\sim n \log(n)$)



Future Development

“Devices”

- Minimize / Avoid Packages → (PCB) Embedding
- Integrate Driver Stage
- Integrate Sensors / Monitoring
- Multiple Use of Isolated Gate Drive Communication Channel
- Offer Test Devices with Integrated Measurement Function
- Facilitate (Double Sided) Heat Extraction

Converters

- Standardized Very Low Cost Building Blocks
- “Application Specific” = Wide Operating Range Standardized Blocks
- Self-Parametrization
- Bidirectional Converters

Systems

- AC and DC Distribution
- Single Converter vs. Combination of Modules / Cells
- Initial Costs / Life Cycle Cost Trade-off
- Grid 4.0

Design


- Minimize Design Time / Fully Computerized
- Maximize Design Flexibility for Appl. Specific Solution (PCB)
- Maximize Design Insight for Trade-off Analysis
- Design for Manufacturing (Planar / PCB Based)

Literature

- More & More “White Noise”





Technology Sensitivity Analysis Based on η - ρ -Pareto Front

 - ▶ Sensitivity to Technology Advancements
- ▶ Trade-off Analysis





Converter Performance Evaluation Based on η - ρ - σ -Pareto Surface

► σ : kW/\$

    

Converter Performance Evaluation Based on η - ρ - σ -Pareto Surface

► 'Technology Node'

  

Technology Node: $(\sigma^*, \eta^*, \rho^*, f_P^*)$