



life.augmented

15kW Bi-directional Vienna PFC

Jeff Halbig

Power Discrete Group – Product Marketing Manager

Agenda

- 1 Demo board Introduction
- 2 Modified Vienna Topology Comparison
- 3 Bidirectional PFC architecture and control
- 4 Demo board summary

15kW 3L T-Type Converter PFC



Main specs

- $P_{out} = 15kW$ @ $V_{in} = 380Vac$ & $V_{out} = 800V$
- $PF > 0.98$ @ 20% load
- $THD < 5\%$ @ 20% load $\eta > 97\%$ @ 20% load
- CCM decoupling current control loop
- Active & Reactive power control
- Grid Connection capability
- Switching frequency = 70kHz
- $I_{ripple} = 2.5A$
- $V_{DC_ripple} = 10V_{pp}$


Key products

- **STM32G474** (32 bit Microcontroller)
- **SCTW40N120G2V** (70m Ω 1200V SiC MOSFET)
- **SCTW35N65G2V** (55m Ω 650V SiC MOSFET)
- **STGAP2S** (Galvanic Isolated Gate Driver)
- **STPS1L30A, STPS2H100A, STTH1L06A, STPS1150A, STPS2L60A** (SiC, Schottky and Ultrafast diodes)
- **STS6NF20V** (N-channel 20 V, STripFET II Power MOSFET)
- **TSV911IDT, TSV912IDT, TSV914IDT** (wide-bandwidth rail to rail Op-Amps)
- **STLM20W87F** (Analog temperature sensor)
- **LD29080DT50R, LD29080S33R**, (LDOs)
- **VIPer26K** (High Voltage Converter)




Industrial On-board Charger System Concept

3-ph Outlet

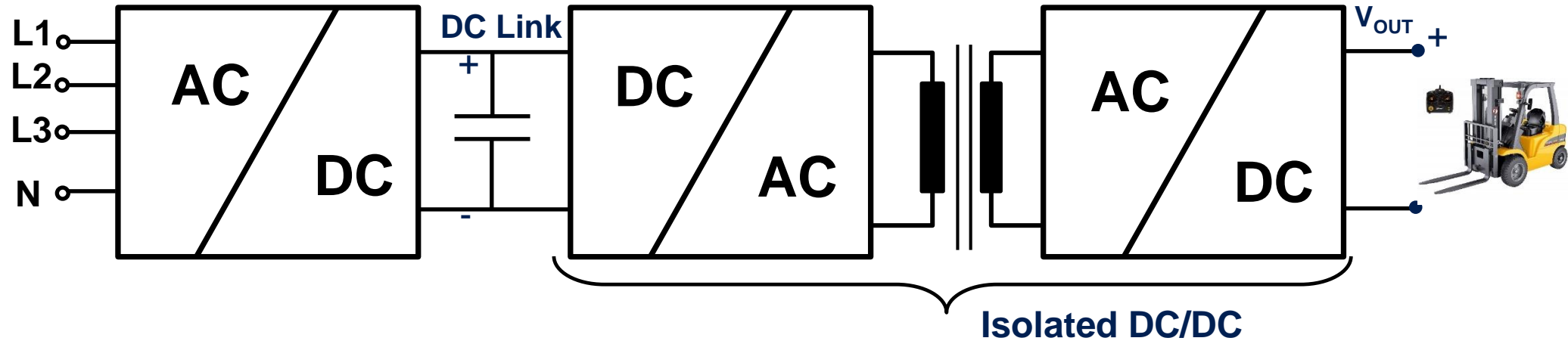


Parameter	Value
Input voltage	$L_x-L_y \rightarrow 400 V_{AC}$ $L_x-N \rightarrow 230 V_{AC}$
DC Link Voltage	400..1000 V
Nominal Power	11..22 kW
Output Voltage	200..500 V_{DC} for 400 V_{DC} Batteries 500..900 V_{DC} for 800 V_{DC} Batteries

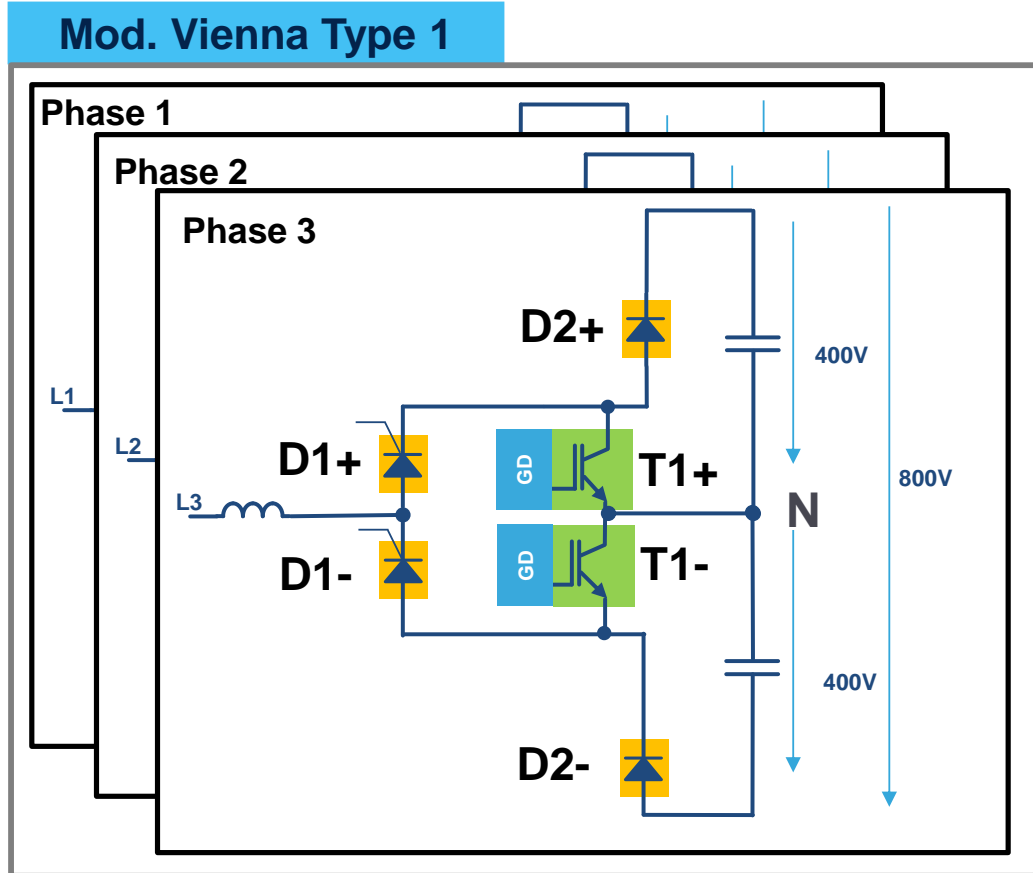Modified Vienna Rectifier Topology Comparison



+ All 650V rated devices
→ lower cost

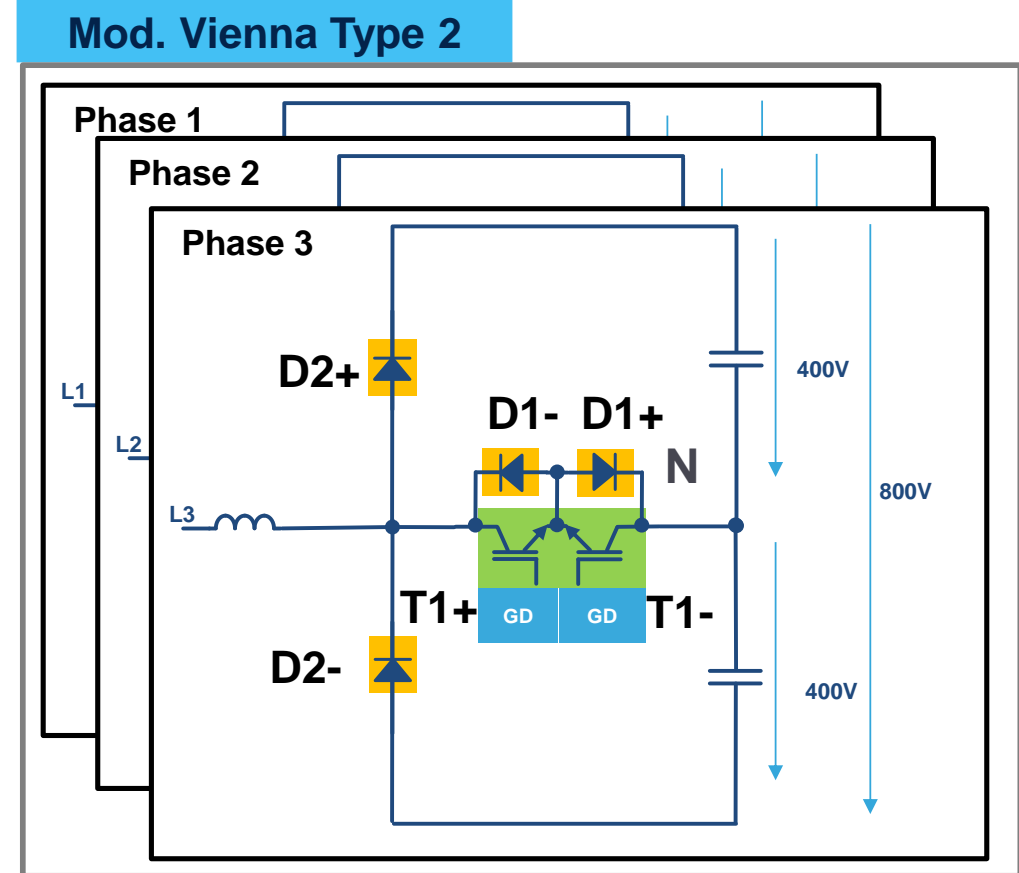- 2 devices in the main current path (D1&D2) → lower efficiency



+ 1 devices in the main current path (D2)
→ Higher efficiency



- Need 1200V diodes (D2), typically SiC.
→ Higher cost

Topology Comparison



Efficiency Comparison @ $P_{out}=20$ kW

Vienna rectifier Type 1

Vienna rectifier Type 2

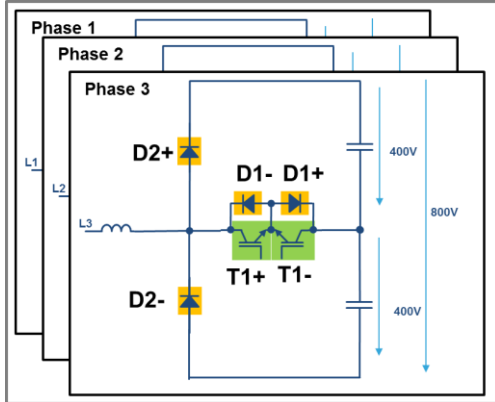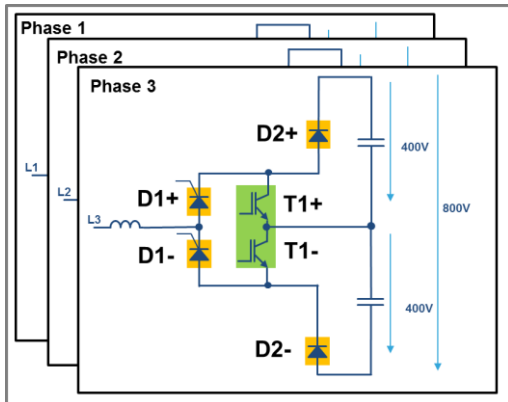


	Mod. Vienna Type 1	Mod. Vienna Type 2
D1	STBR6012W	-----
T1	STGW40H65DFB-4 STW88N65M5-4 SCTW90N65G2V-4	
D2	STPSC40065C	STPSC40H12C

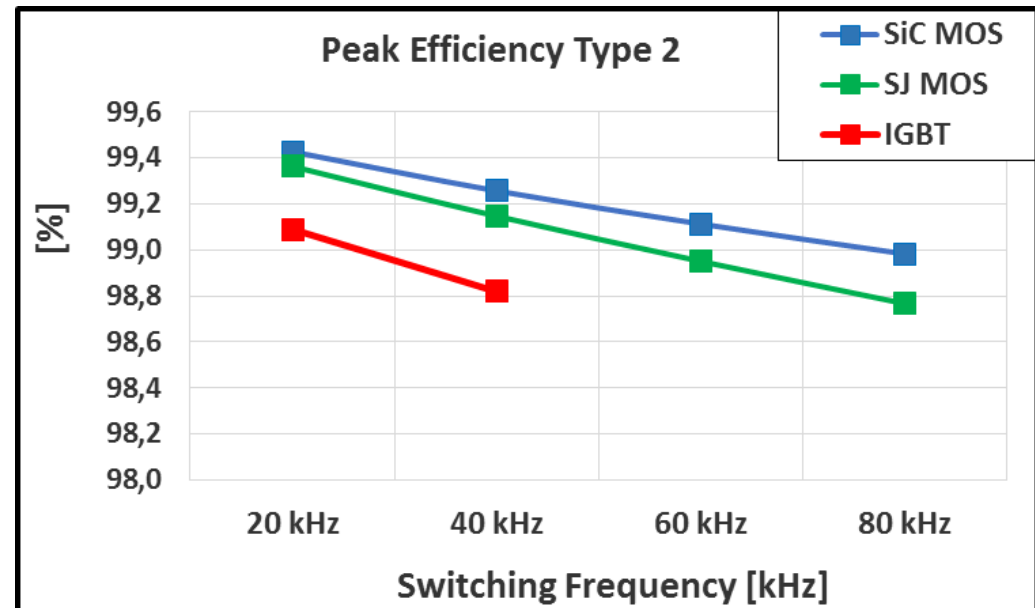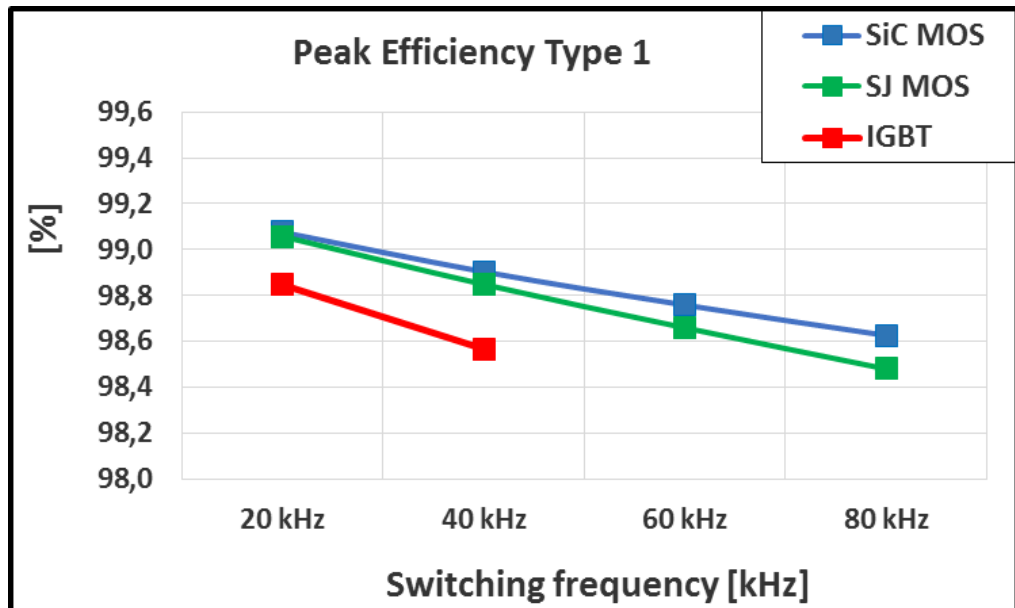

Simulated efficiency @ $T_j = 125^\circ\text{C}$, considering only semiconductor losses.

Modified Vienna Rectifier Topology Comparison


Modified Vienna Type 1

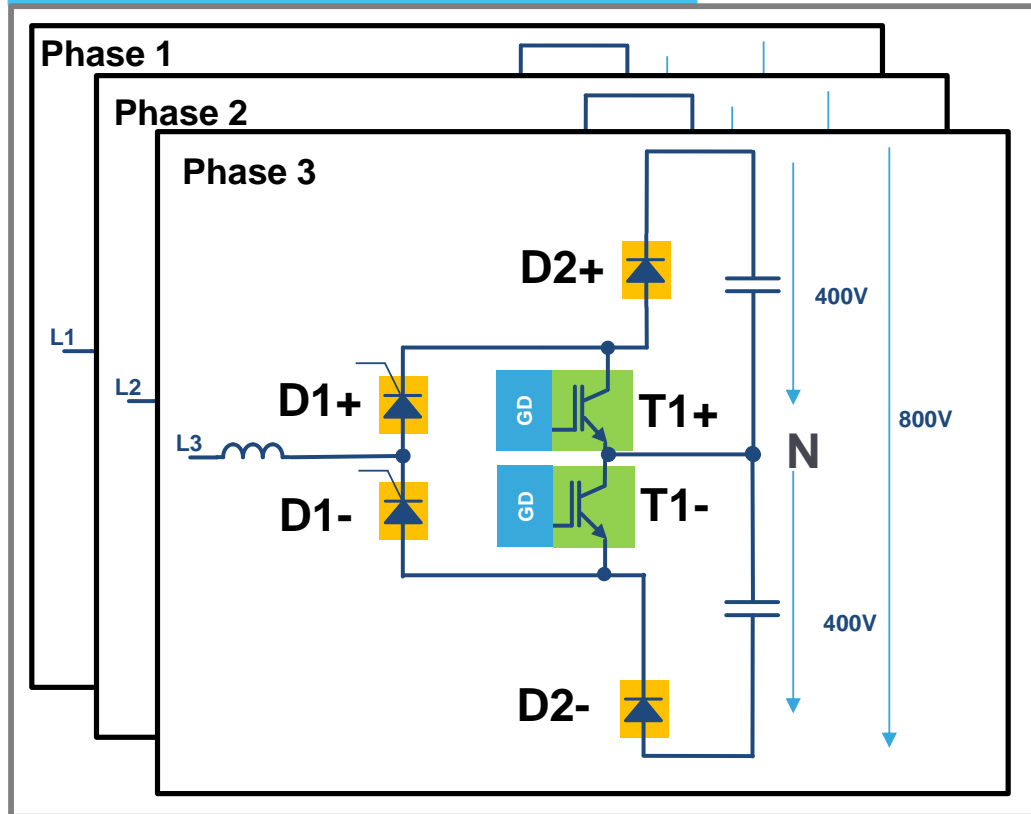

+ All 650V rated devices
→ lower cost

- 2 devices in the main current path (D1&D2) → lower efficiency


Modified Vienna Type 2

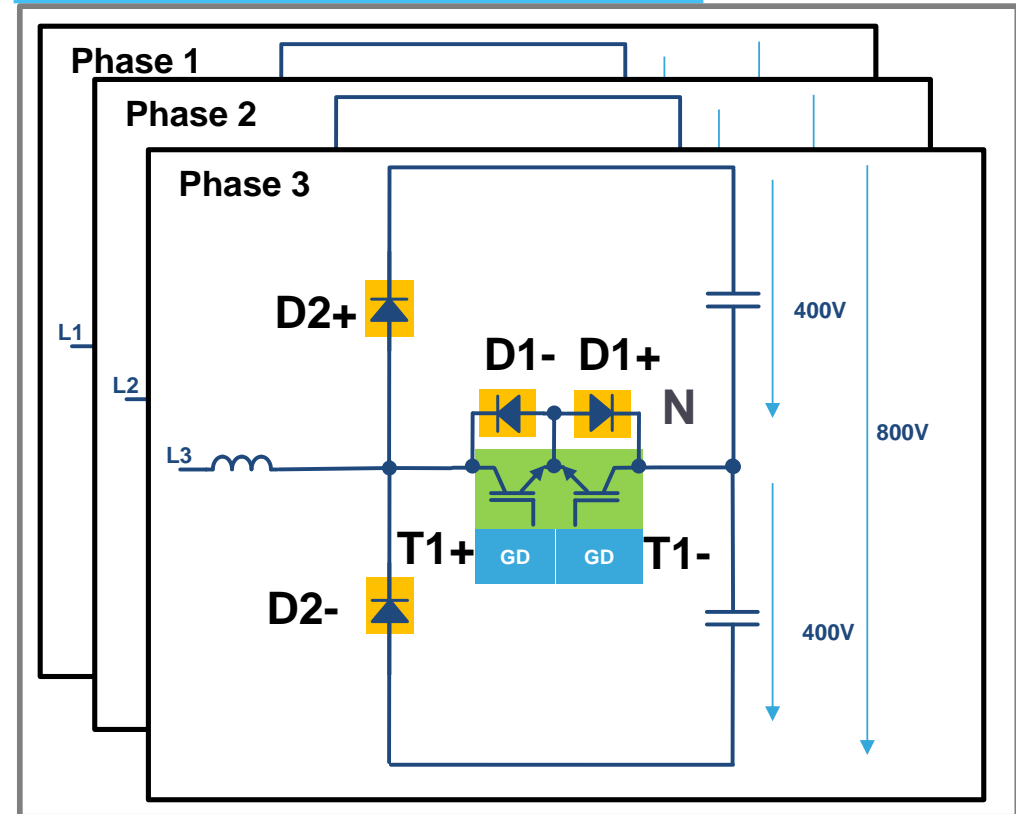

+ 1 devices in the main current path (D2)
→ Higher efficiency


- Need 1200V diodes (D2), typically SiC.
→ Higher cost

Bidirectional PFC - system architecture

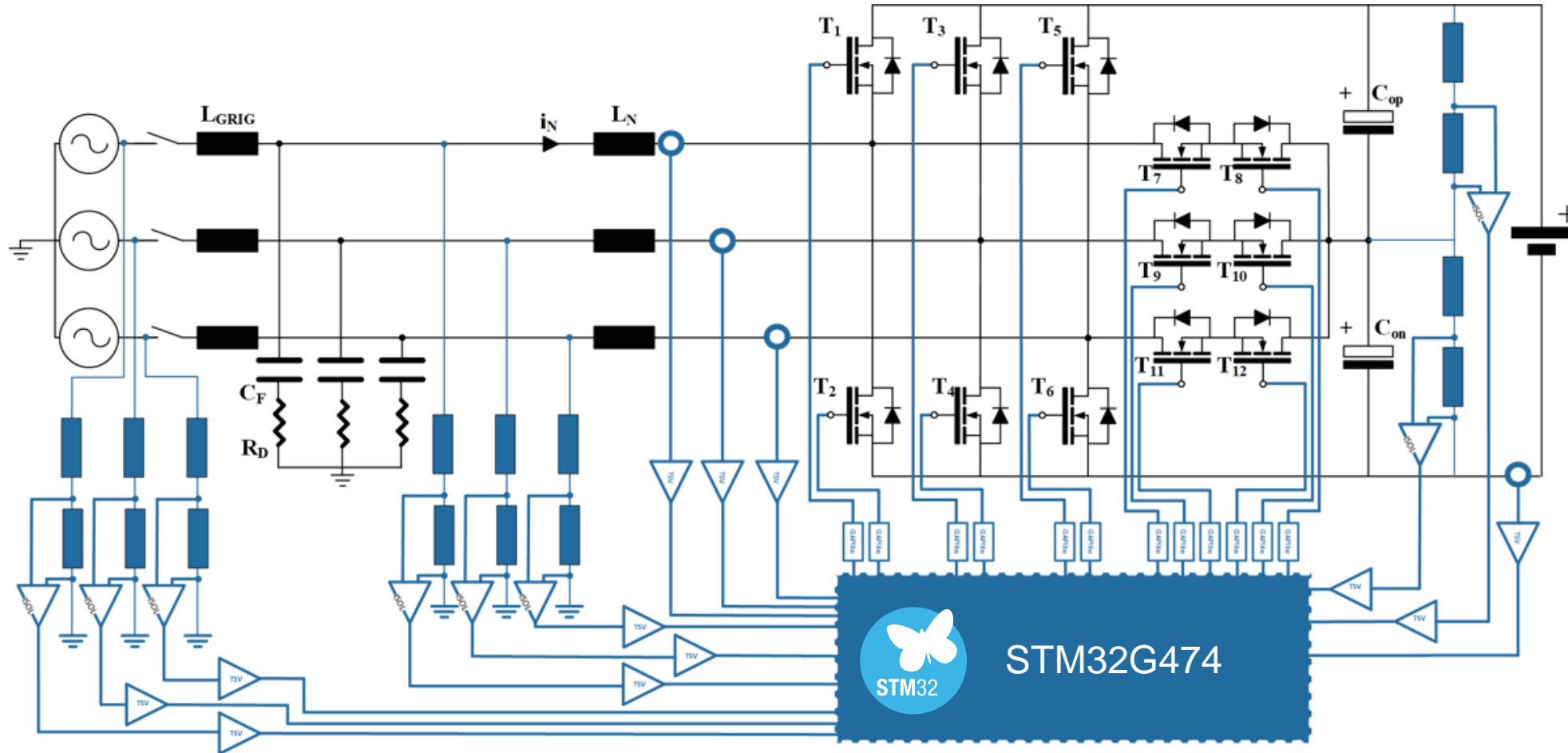


Bidirectional Control

Grid to Battery

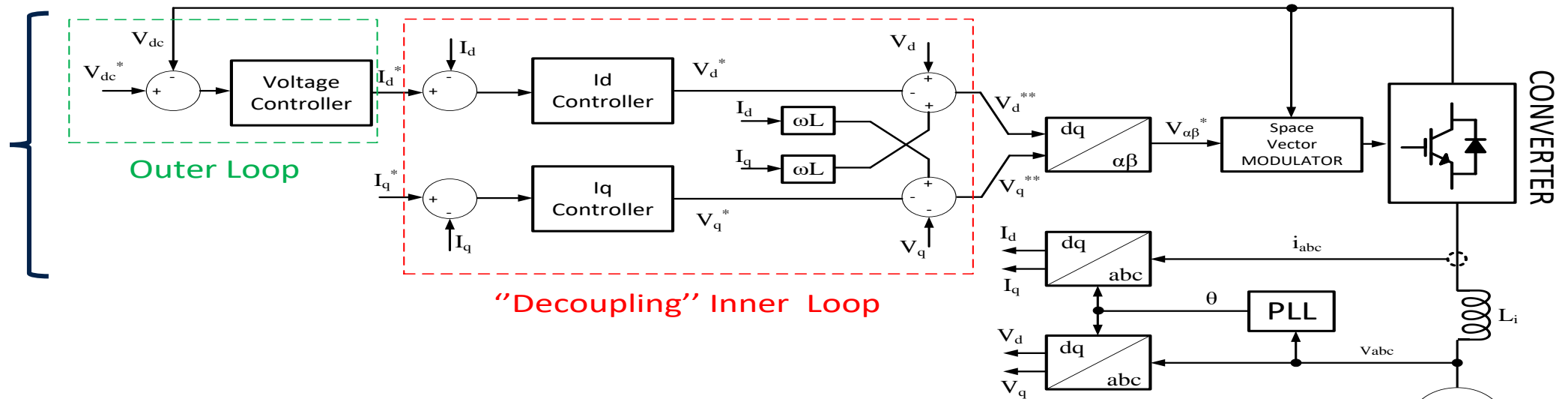

"Decoupling" Inner Loop

Battery to Grid

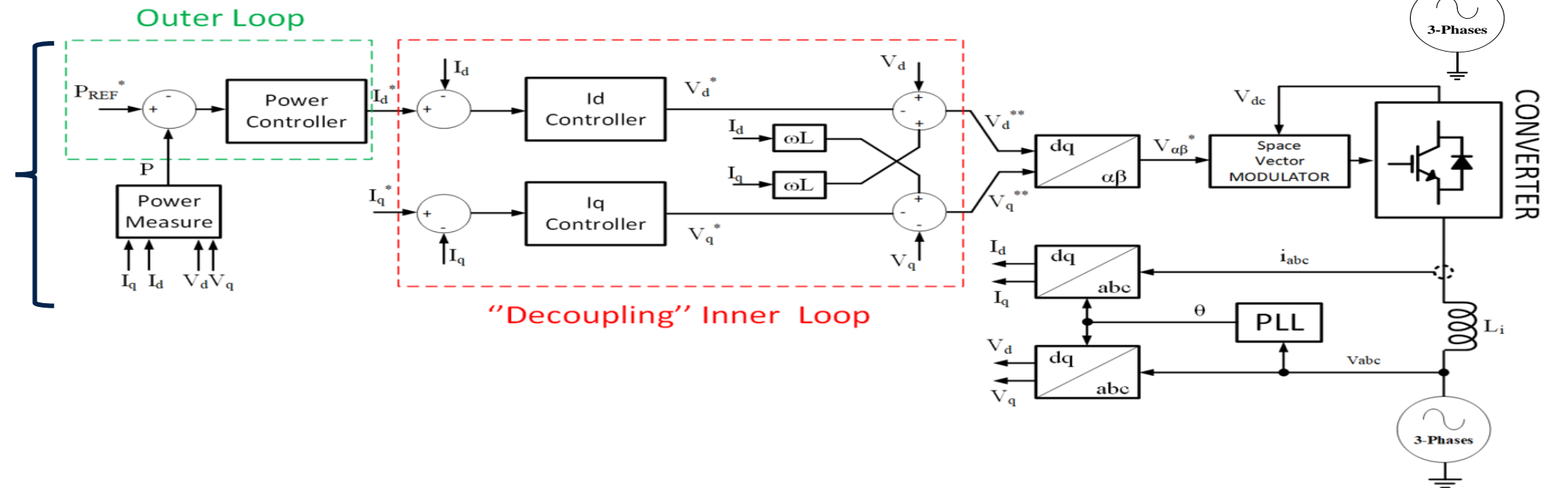

"Decoupling" Inner Loop

15kW 3L T-Type Converter PFC



Main specs

- $P_{out} = 15kW$ @ $V_{in} = 380Vac$ & $V_{out} = 800V$
- $PF > 0.98$ @ 20% load
- $THD < 5\%$ @ 20% load $\eta > 97\%$ @ 20% load
- CCM decoupling current control loop
- Active & Reactive power control
- Grid Connection capability
- Switching frequency = 70kHz
- $I_{ripple} = 2.5A$
- $VDC_{ripple} = 10V_{pp}$

Key products

- **STM32G474** (32 bit Microcontroller)
- **SCTW40N120G2V** (70m Ω 1200V SiC MOSFET)
- **SCTW35N65G2V** (55m Ω 650V SiC MOSFET)
- **STGAP2S** (Galvanic Isolated Gate Driver)
- **STPS1L30A, STPS2H100A, STTH1L06A, STPS1150A, STPS2L60A** (SiC, Schottky and Ultrafast diodes)
- **STS6NF20V** (N-channel 20 V, STripFET II Power MOSFET)
- **TSV911IDT, TSV912IDT, TSV914IDT** (wide-bandwidth rail to rail Op-Amps)
- **STLM20W87F** (Analog temperature sensor)
- **LD29080DT50R, LD29080S33R**, (LDOs)
- **VIPer26K** (High Voltage Converter)

Thank you

© STMicroelectronics - All rights reserved.

The STMicroelectronics corporate logo is a registered trademark of the STMicroelectronics group of companies. All other names are the property of their respective owners.



life.augmented