Instrumentação Virtual

Test and Measurement Solutions for Students in the

Lab and at Home



ADALM2000

Advanced Active Learning Module



- 1. Oscilloscope
- 2. Spectrum Analyzer
- 3. Network Analyzer
- 4. Signal Generator
- 5. Logic Analyzer
- 6. Pattern Generator
- 7. Digital IO
- 8. Voltmeter
- 9. Power Supply









Oscilloscope

Waveform Generator

Power Supplies

Data Logger

Logic Analyzer

Pattern Generator

Static I/O

Spectrum Analyzer

Network Analyzer


Impedance Analyzer

Protocol Analyzer

Script Editor



Simulação de Circuitos (LTSpice)

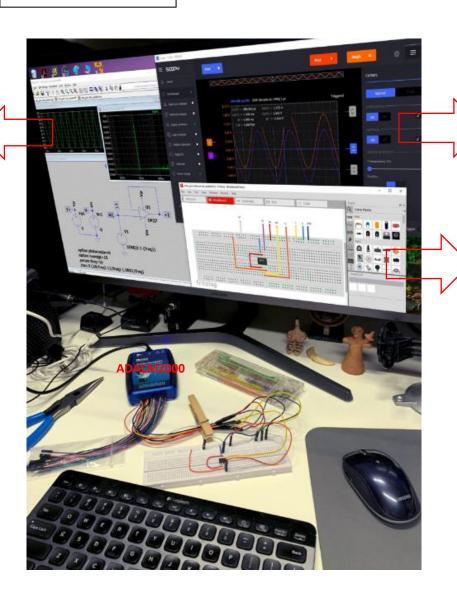



Simulação de um Osciloscópio no ADALM2000 | Software Scopy (Analog Devices | USA)


Simulação de Protoboard (Fritzing)





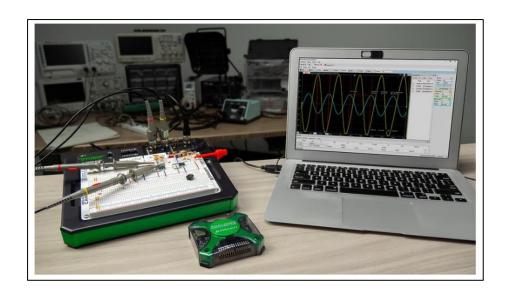

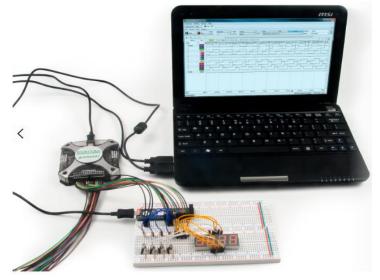

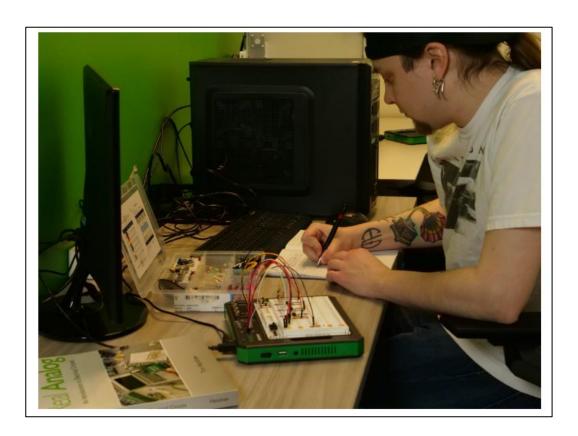


ADALM2000

Osciloscope

≡ SCOPY 500.000 μs/div 8000 Samples at 1 MHz/1 μs OH1 (==) OH2 (==) +

Spectrum Analyzer

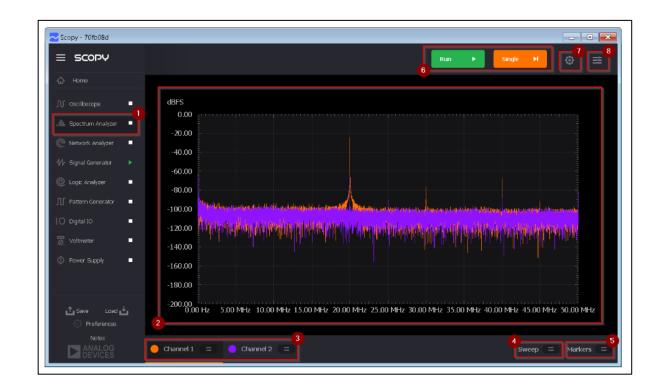







Osciloscope

_ O X W WaveForms (new workspace) Scope 1 🔯 File Control View Window Channel 1 * Condition: C1 C2 8192 samples at 800 kHz | 2016-12-08 15:15:37.278 @ 1 E E W Y 1 ms/div Aud Channel (6) Channel 1 250 mV/div 1 ms 3 ms Status: OK Manual Trigger Discovery2 SN:210321A19E22


Spectrum Analyzer

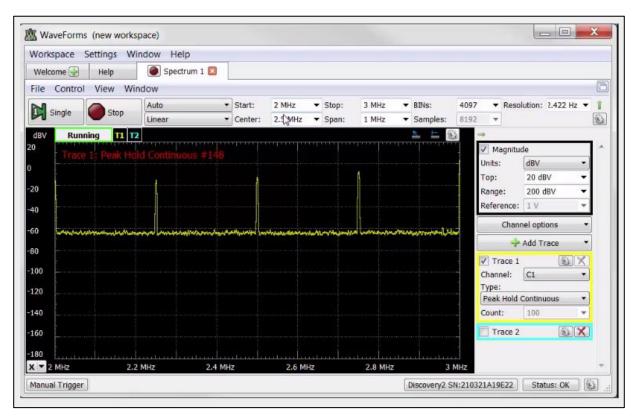

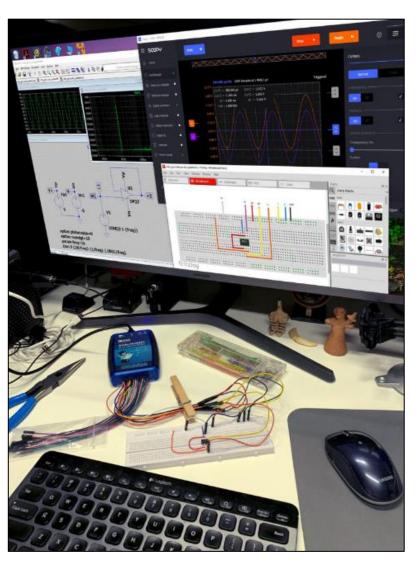




Osciloscópio Virtual (ADALM2000)

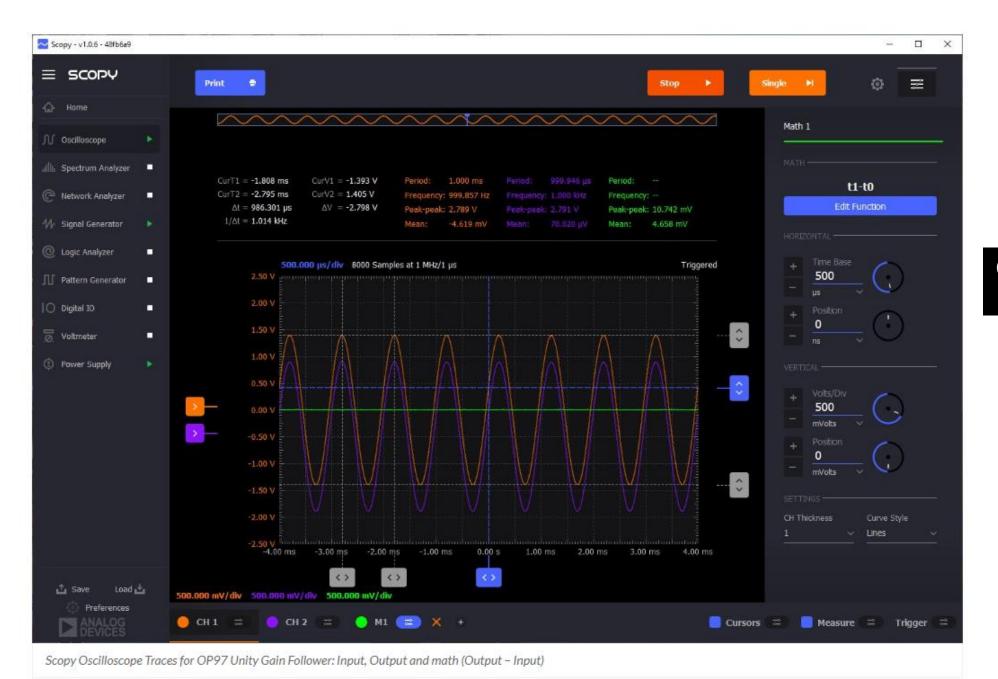


Osciloscópio Virtual (ADALM2000)

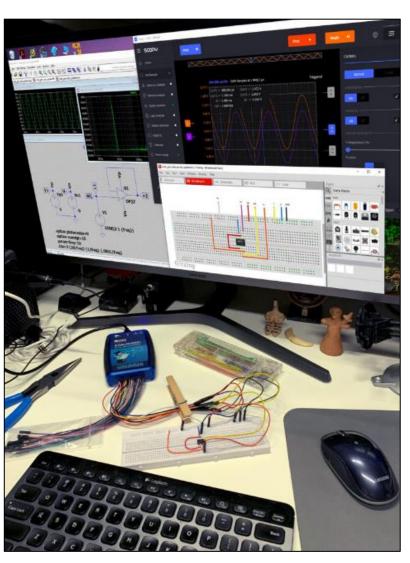




Fritizing

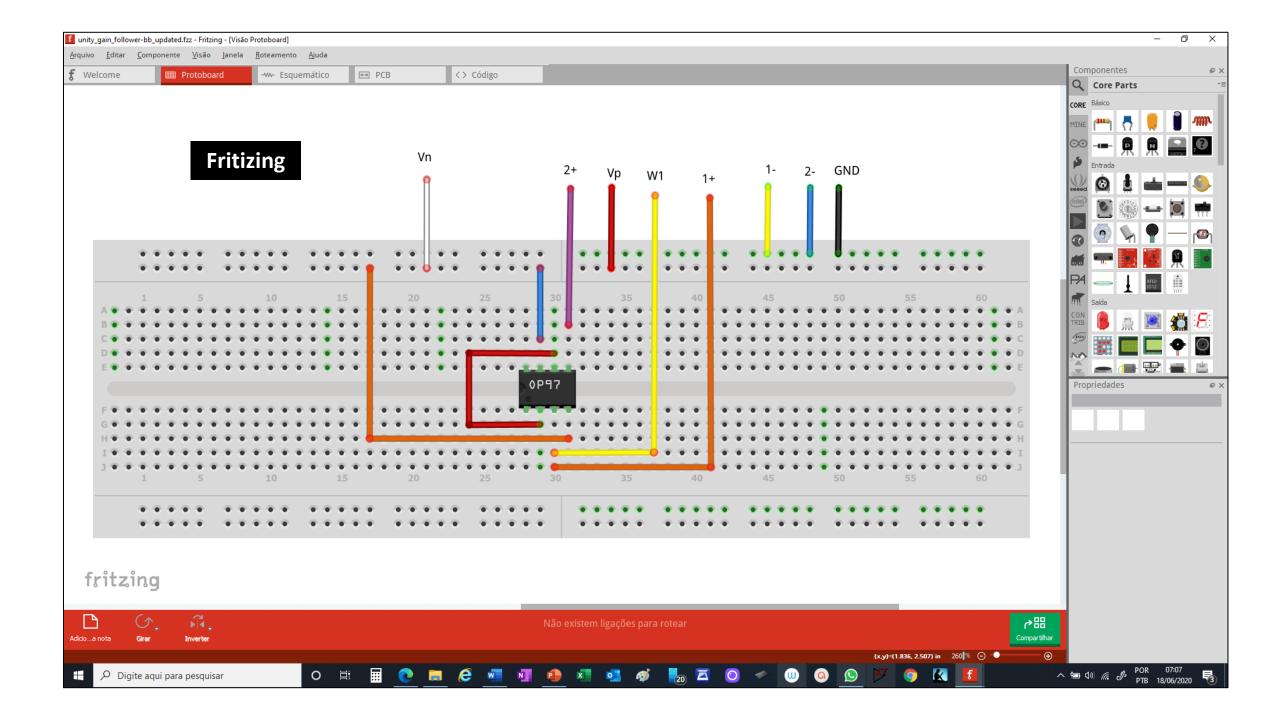


É importante mostrar as conexões entre a instrumentação virtual e o protoboard! O símbolo do Analogic Discovery 2 pode ser inserido na biblioteca de componentes.

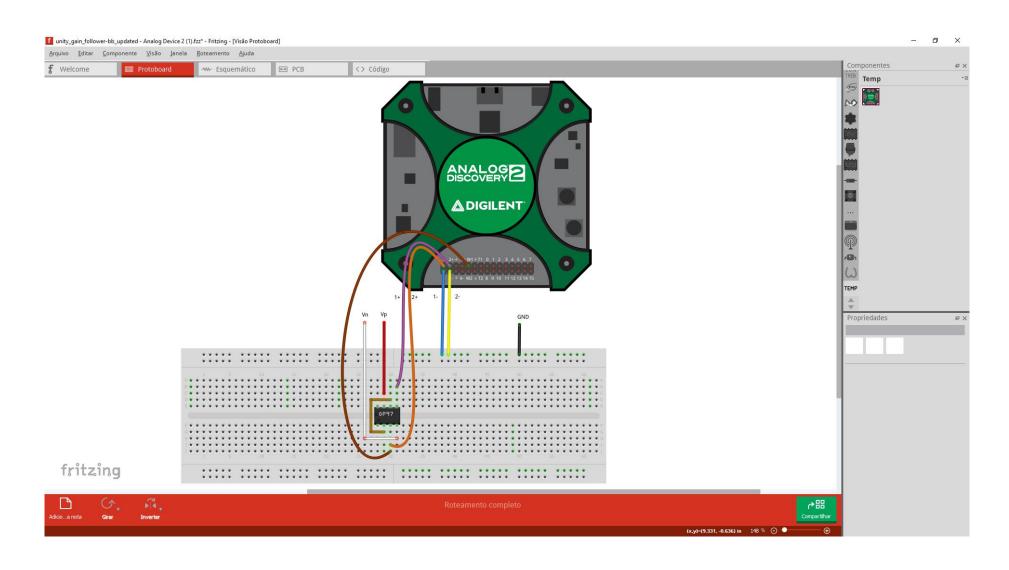


ADALM2000

LTSpice (Simulator Circuit)



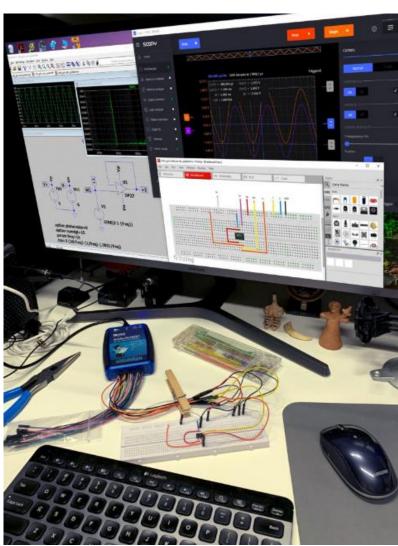

LTSpice (Simulator Circuit)

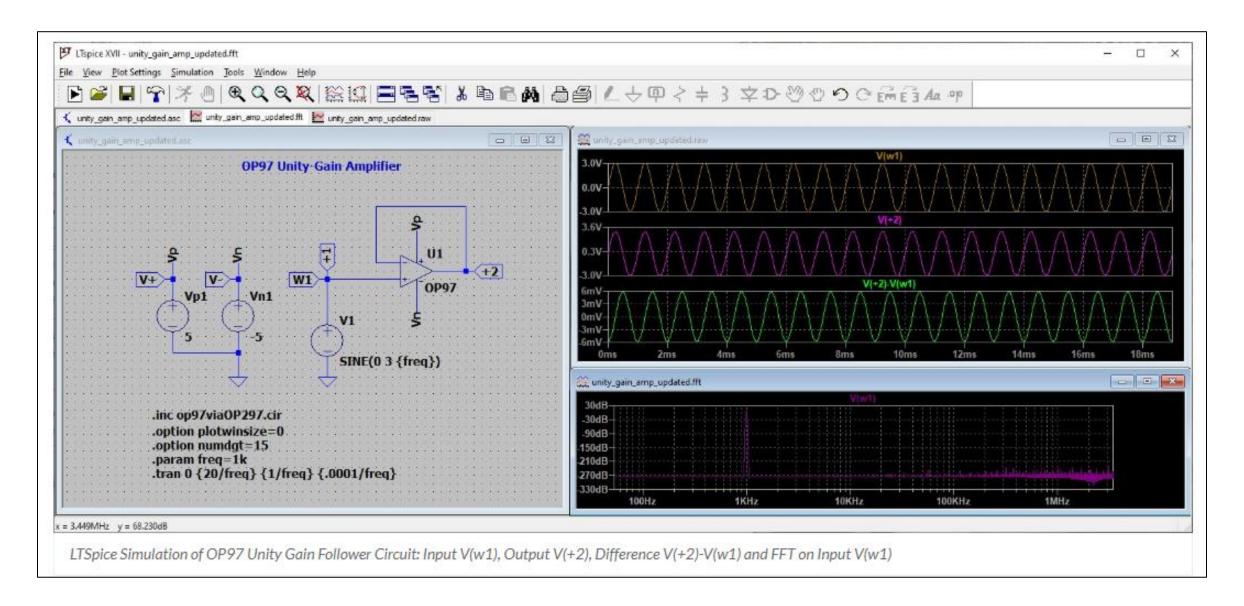



Tutorials

- Analog Electronics
- Mixed Signal Electronics Systems
- Signals and Systems

Analog Electronics

Table of Contents:

Operational Amplifiers:

- 1. Ideal Voltage Feedback (VFB) Op Amp (MT-032)
 - I. Inverting Amplifier (MT-213)
 - II. Inverting Summing Amplifier (MT-214)
 - III. Half Wave Rectifier (MT-212)
 - IV. Full Wave Rectifier (MT-211)
- 2. Current Feedback (CFB) Op Amps (MT-034)
- 3. Voltage Feedback Op Amp Gain and Bandwidth (MT-033)
- 4. Open Loop Gain and Open Loop Gain Nonlinearity (MT-044)
- 5. Bandwidth and Bandwidth Flatness (MT-045)
- 6. Settling Time (MT-046)
- 7. High Speed Voltage Feedback Op Amps (MT-056)
- 8. Input Offset Voltage (MT-037)
- 9. Total Output Offset Voltage Calculations (MT-039)
- 10. Chopper Stabilized (Auto-Zero) Precision Op Amps (MT-055)
- 11. Input Bias Current (MT-038)
- 12. Input Impedance (MT-040)
- 13. Power Supply Rejection Ratio (PSRR) and Supply Voltages (MT-043)
- 14. Input and Output Common-Mode and Differential Voltage Range (MT-041)
- 15. Common-Mode Rejection Ratio (CMRR) (MT-042)
- 16. Outputs, Single-Supply, and Rail-to-Rail Topics (MT-035)
- 17. Output Phase-Reversal and Input Over-Voltage Protection (MT-036)

Instrumentation Amplifiers

- 1. Basic Two Op Amp In-Amp Configuration (MT-062)
- 2. Basic Three Op Amp In-Amp Configuration (MT-063)
- 3. In-Amp DC Error Sources (MT-064)
- 4. Auto-Zero In Amps (MT-067)
- 5. In-Amp Noise (MT-065)
- 6. In-Amp Bridge Circuit Error Budget Analysis (MT-066)
- 7. Difference and Current Sense Amplifiers (MT-068)
- 8. In-Amp Input Overvoltage Protection (MT-069)
- 9. In-Amp Input Radio Frequency Interference Protection (MT-070)
- 10. A Deeper Look into Difference Amplifiers

Variable Gain Amplifiers (VGAs)

- 1. Precision Variable Gain Amplifiers (MT-072)
- 2. High Speed Variable Gain Amplifiers (MT-073)

Comparators

- 1. Comparator Basics (MT-083)
- 2. Op Amps As Comparators (MT-084)
 - Op Amps as Comparators (PowerPoint Slides)

Logarithmic Amplifiers

- 1. Log Amp Basics (MT-077)
- 2. High Frequency Log Amps (MT-078)



Tutorials

- Analog Electronics
- Mixed Signal Electronics Systems
- Signals and Systems

Logarithmic Amplifiers

- 1. Log Amp Basics (MT-077)
- 2. High Frequency Log Amps (MT-078)

Analog Multipliers

- 1. Analog Multipliers Basics (MT-079)
- 2. Mixers and Modulators Overview (MT-080)

Sample / Hold Amplifiers

- 1. Sample-and-Hold Amplifiers (MT-090)
- 2. Applying IC Sample-Hold Amplifiers (AN-270)

Analog Switches and Multiplexing

- 1. Analog Switches and Multiplexers Basics (MT-088)
- 2. Video Multiplexers and Crosspoint Switches (MT-089)

Voltage References:

1. Voltage References (MT-087)

Analog Circuit Simulation

- 1. Analog Circuit Simulation (MT-099)
- 2. SPICE-Compatible Op Amp Macro-Models (AN-138)





Tutorials

